
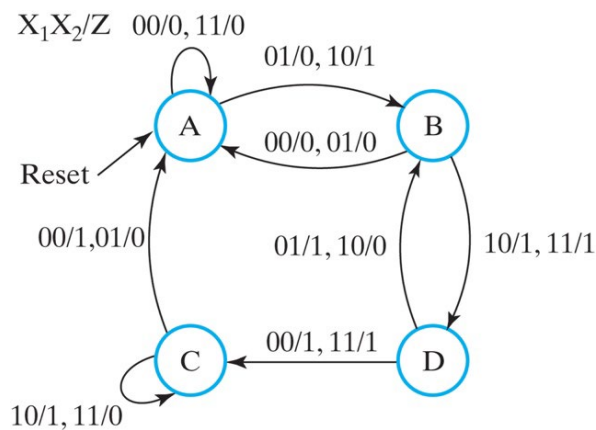


Tutorial Week 7 – Sequential Circuit Design

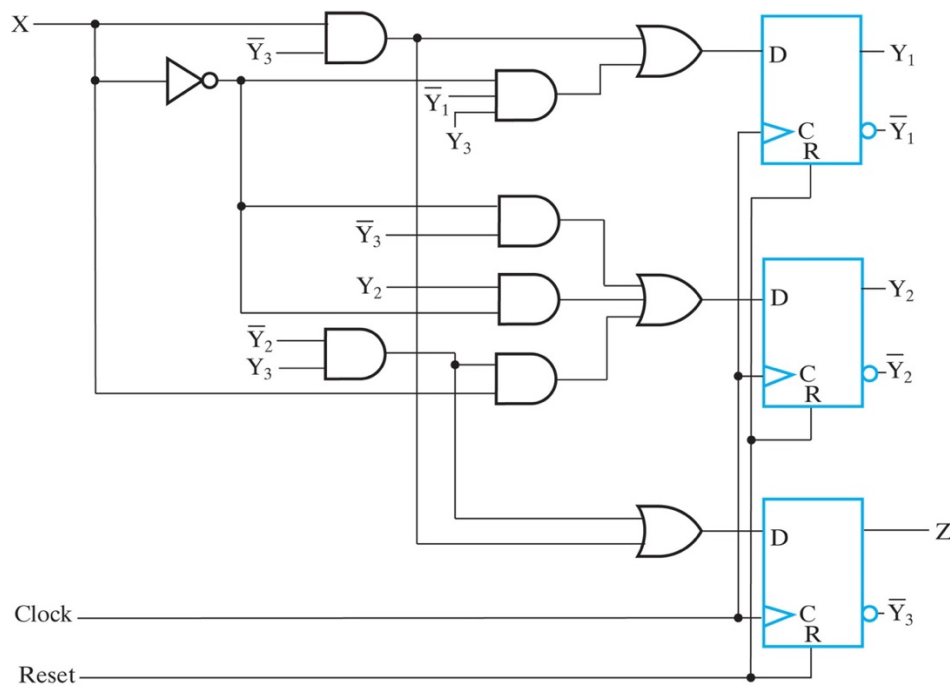
1. **(4-13)** Design a sequential circuit with two D flip-flops *A* and *B* and one input *X*. When $X = 0$, the state of the circuit remains the same. When $X = 1$, the circuit goes through the state transitions from 00 to 10 to 11 to 01, back to 00, and then repeats. Draw the logic diagram for the circuit.
2. **(4-14)** The state diagram of a sequential circuit is shown below



- a. Find the state table for the circuit
 - b. Make a state assignment for the circuit using 2-bit codes and find the encoded state table
 - c. Find an optimized circuit implementation using D flip-flops, NAND gates and inverters
 - d. Repeat parts (b) and (c) using one-hot encoding for the state assignment
3. **(4-16)** The circuit below is to be redesigned to cut its cost.
 - a. Find the state table for the circuit and replace the state codes with single letter identifiers. States 100 and 111 were unused in the original design
 - b. Check for and combine equivalent states
 - c. Make a state assignment such that the output is one of the state variables
 - d. Find the gate input costs of the original circuit and your circuit, assuming that the gate input cost of the D flip-flop is 14. Is the cost of the new circuit reduced?




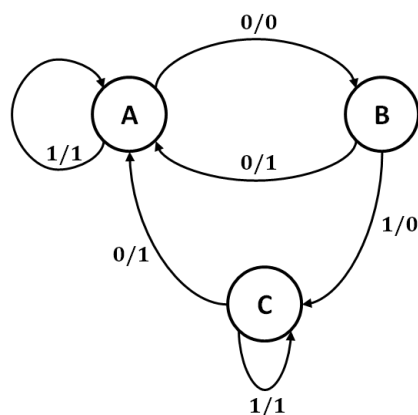4. Design a circuit that implements the following state diagram:



- Using D flip-flops
- Using T flip-flops

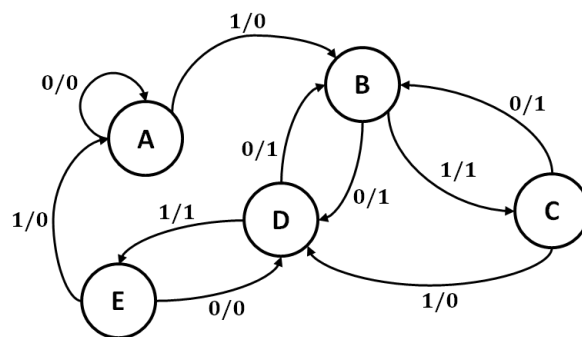5. Design a circuit that implements the following state diagram:



Where referenced, questions are taken from the textbook:

M. Mano, C. R. Kime and T. Martin, *Logic and Computer Design Fundamentals, 5th Edition (Global Edition)*, Pearson, 2016

- a. Using D flip-flops
 - b. Using JK flip-flops
6. Find a minimal state machine equivalent to the state machine whose state table is given below.

Current State	Next State, Output	
	X = 0	X = 1
A	H, 1	A, 0
B	E, 1	H, 1
C	E, 1	D, 1
D	A, 0	G, 0
E	C, 0	E, 1
F	D, 1	F, 0
G	E, 1	H, 1
H	F, 0	B, 0

7. Find a minimal state machine equivalent to the state machine whose state table is:

Current State	Next State		Output Z
	X = 0	X = 1	
A	E	C	0
B	B	C	1
C	A	E	1
D	E	D	0
E	D	B	0

8. **(4-20)** A Universal Serial Bus (USB) communicator link requires a circuit that produces the sequence 00000001. You are to design a synchronous sequential circuit that starts producing this sequence for input $E = 1$. Once the sequence starts, it completes. If $E = 1$, during the last output in the sequence, the sequence repeats. Otherwise, if $E = 0$, the output remains the constant at 1.
- a. Draw the Moore state diagram for the circuit
 - b. Find the state table and make a state assignment
 - c. Design the circuit using D flip-flops and logic gates. A reset should be included to place in the circuit in the appropriate initial state at which E is examined to determine if the sequence of constant 1s is to be produced.
9. **(4-23)** In many communication and networking systems, the signal transmitted on the communication line uses a non-return-to-zero (NRZ) format. USB uses a specific version referred to as non-return-to-zero inverted (NRZI). A circuit that converts any message sequence of 0s and 1s to a sequence in the NRZI format is to be designed. The mapping for such a circuit is as follows:
- a. If the message bit is a 0, then the NRZI format message contains an immediate change from 1 to 0 or from 0 to 1, depending on the current NRZI value.

- b. If the message bit is a 1, then the NRZI format message remains fixed at 0 or 1, depending on the current NRZI value.

This transformation is illustrated by the following example, which assumes that the initial value of the NRZI message is 1:

Message: 10001110011010

NRZI Message: 10100001000110

- a. Find the Mealy model state diagram for the circuit.
- b. Find the state table for the circuit.
- c. Find an implementation of the circuit using D flip-flops and logic gates.
- d. Find an equivalent Moore model implementation of the circuit.