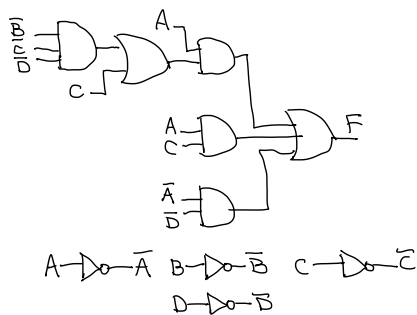


# Question 1 B


Saturday, 7 March 2020 6:20 pm

- a) i) Literals = 9  
Terms = 5  $\rightarrow A(\overline{B}\overline{C}\overline{D} + C) + AC + \overline{A}\overline{D}$   
Complements = 4  
GIC = 18

Students may draw logic diagram to determine the GIC.



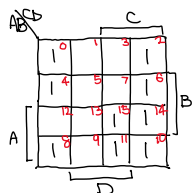- ii) Students can use the K-map to find the minterms for F or use algebraic expansion




OR

$$\begin{aligned} F &= A(\overline{B}\overline{C}\overline{D} + C) + AC + \overline{A}\overline{D} \\ &= \overline{A}\overline{B}\overline{C}\overline{D} + AC + \overline{A}\overline{D} \\ &= \overline{A}\overline{B}\overline{C}\overline{D} + AC(B + \overline{B})(D + \overline{D}) + \overline{A}\overline{D}(B + \overline{B})(C + \overline{C}) \end{aligned}$$

$$F = \Sigma m(0, 2, 4, 6, 8, 10, 11, 14, 15)$$

iii)


A	B	C	D	F	$m_i$
0	0	0	0	1	$m_0$
0	0	0	1	0	$m_1$
0	0	1	0	1	$m_2$
0	0	1	1	0	$m_3$
0	1	0	0	1	$m_4$
0	1	0	1	0	$m_5$
0	1	1	0	1	$m_6$
0	1	1	1	0	$m_7$
1	0	0	0	1	$m_8$
1	0	0	1	0	$m_9$
1	0	1	0	1	$m_{10}$
1	0	1	1	1	$m_{11}$
1	1	0	0	0	$m_{12}$
1	1	0	1	0	$m_{13}$
1	1	1	0	1	$m_{14}$
1	1	1	1	1	$m_{15}$

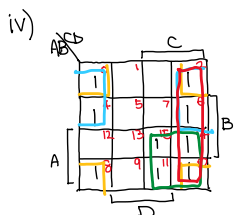

$$F = \overline{B}\overline{D} + \overline{A}\overline{D} + AC \quad \leftarrow \text{SOP}$$

$$\text{PI: } \overline{B}\overline{D}, \overline{A}\overline{D}, AC, C\overline{D}$$
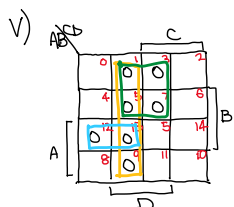
$$\text{EPI: } \overline{B}\overline{D}, \overline{A}\overline{D}, AC$$



$$F = (\overline{A} + \overline{B} + C)(C + \overline{D})(A + \overline{D}) \quad \leftarrow \text{POS}$$


$$\text{PI: } (\overline{A} + \overline{B} + C), (C + \overline{D}), (A + \overline{D})$$

$$\text{EPI: } (\overline{A} + \overline{B} + C), (C + \overline{D}), (A + \overline{D})$$

- vi) Literals = 6  
Terms = 3  
Complements = 3  
GIC = 12

Reduction of 6 GIC after optimisation

vii)  $F = BD + \bar{A}B + AC$

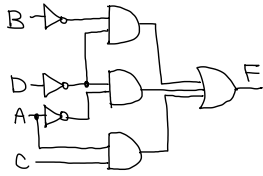

b) binary hexadecimal octal  
110101100.111    1AC.E    654.7

Hex  $\rightarrow$  binary


000 110101100.1110  
 10 12 14  
 ||| ||| |||  
 (1 A C . E)<sub>16</sub>  $\leftarrow$  Hex

Binary  $\rightarrow$  octal

6 5 4 . 7  
 (110101100.111)<sub>2</sub>  $\leftarrow$  Binary

c) A - D latch

B - Positive edge triggered D-flipflop

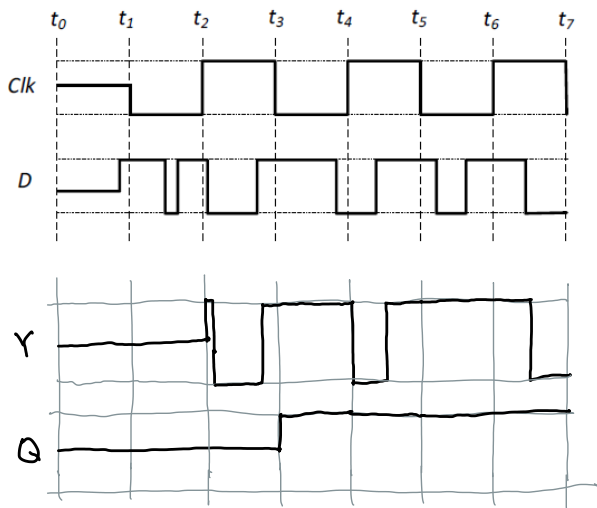


## Question 2 B

Saturday, 7 March 2020 8:31 pm

a) i)  $X+Y = X \oplus Y + XY$   
 $X \oplus Y + XY = X\bar{Y} + \bar{X}Y + XY$   
 $= X\bar{Y} + XY + XY + \bar{X}Y$   
 $= X(\bar{Y}+Y) + Y(X+\bar{X})$   
 $= X+Y$

ii)  $H(A,B,C) = A\bar{B} + AB\bar{C} + \bar{A}B$   
 $= A\bar{B} + AB\bar{C}$   
 $= A\bar{B} \oplus AB\bar{C} + (A\bar{B})(AB\bar{C})$   
 $= A\bar{B} \oplus AB\bar{C} + (\bar{A}\bar{B})(A\bar{B}\bar{C})$   
 $= A\bar{B} \oplus AB\bar{C}$

$$X+Y = X \oplus Y + XY$$

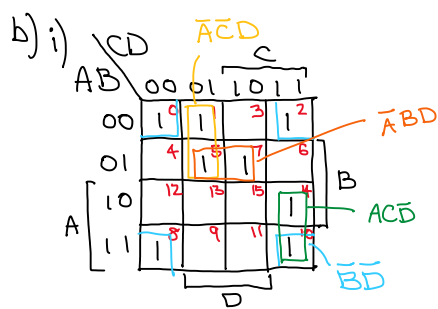

$$G = \sum m(3, 4, 6, 9, 11, 12, 13, 15)$$

$$= \sum m(0, 1, 2, 5, 7, 8, 10, 14)$$



$$= \bar{A}\bar{B}\bar{C}\bar{D} + \bar{A}\bar{B}\bar{C}D + \bar{A}\bar{B}C\bar{D} + \bar{A}\bar{B}CD + \bar{A}B\bar{C}\bar{D} + \bar{A}B\bar{C}D + \bar{A}BC\bar{D} + \bar{A}BCD$$

$$+ A\bar{B}\bar{C}\bar{D} + A\bar{B}\bar{C}D$$

$$= \bar{B}\bar{D}(\bar{A}\bar{C} + \bar{A}C + A\bar{C} + AC) + \bar{A}\bar{C}D(\bar{B} + B) + AC\bar{D}(B + \bar{B}) + \bar{A}BD(C + \bar{C})$$

$$= \bar{B}\bar{D} + \bar{A}\bar{C}D + AC\bar{D} + \bar{A}BD$$

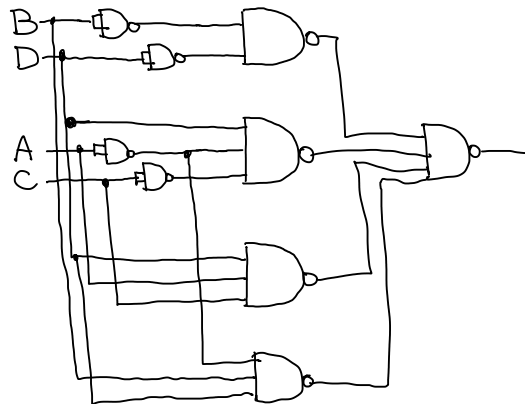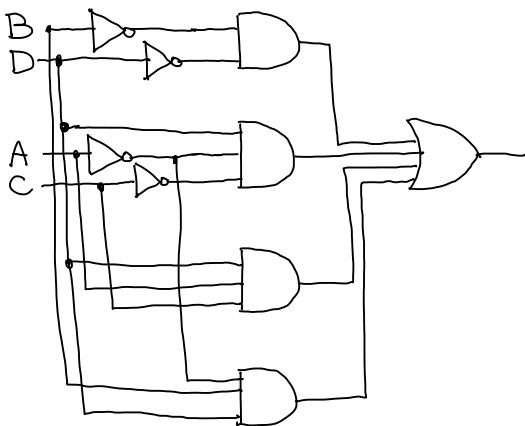ii)  $G = \bar{B}\bar{D} + \bar{A}\bar{C}D + AC\bar{D} + \bar{A}BD$



c) i)


A	B	C	D	Z
0	0	0	0	0
0	0	0	1	1
0	0	1	0	0
0	0	1	1	1
0	1	0	0	0
0	1	0	1	1
0	1	1	0	0
0	1	1	1	1
1	0	0	0	1
1	0	0	1	1
1	0	1	0	0
1	0	1	1	0
1	1	0	0	0
1	1	0	1	0
1	1	1	0	1
1	1	1	1	1

$Z = D$

$Z = D$

$Z = \bar{C}$

$Z = C$

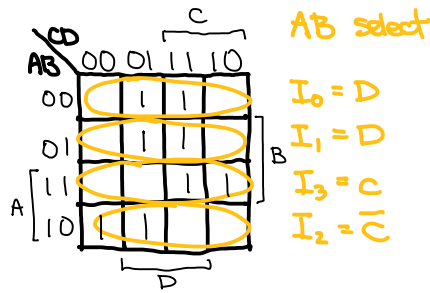


CD select

$I_0 = A\bar{B}$   
 $I_1 = \bar{A} + \bar{B}$   
 $I_2 = AB$   
 $I_3 = \bar{A} + B$



Note: Using CD as select would not give the simplest design.

ii)  $Z = \sum m(1, 3, 5, 7, 8, 9, 14, 15)$


iii)

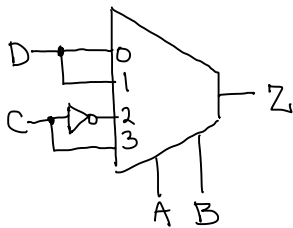


d) Not required

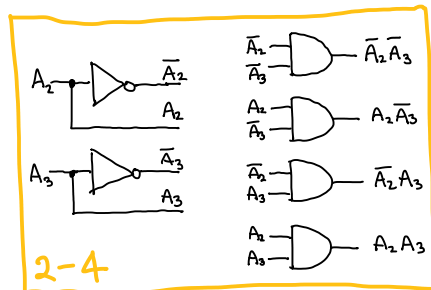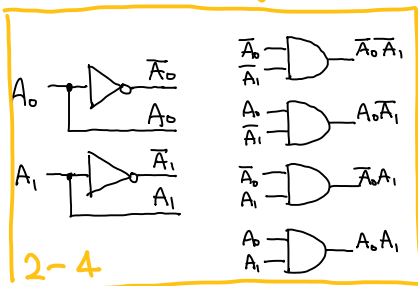

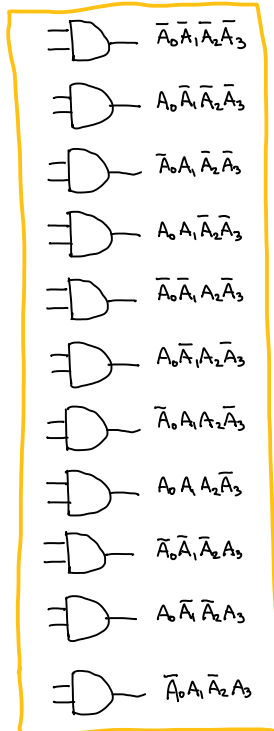$GIC = 4 + 4 \times 2 + 4 \times 2$   
 $+ 11 \times 2$   
 $= 42$



Block diagram

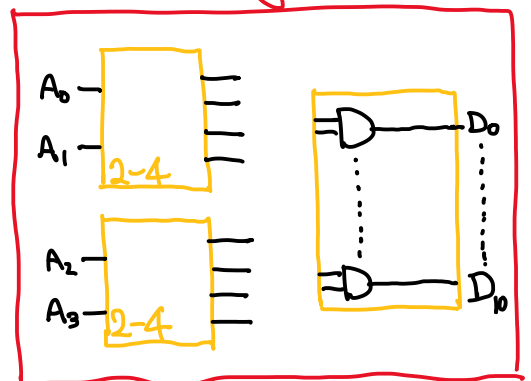

Refer to Week 3 slide 51

- Input n is even,  $n = 4$ .

Use  $2^n$  AND gates driven by two decoders of output size  $2^{n/2} = 4$

Since BCD is only from 0 to X,  $16 - X - 1$  AND gates will be redundant.