

Tutorial 8 – Solutions

1.

```
module decoder_2_to_4_vector(EN, A, D);
    input EN;
    input [1:0] A;
    output [3:0] D;

    wire [1:0] A_n;
    wire [3:0] N;

    not gn0(A_n[0], A[0]);
    not gn1(A_n[1], A[1]);

    and ga3(N[0], A_n[0], A_n[1]);
    and ga4(N[1], A[0], A_n[1]);
    and ga5(N[2], A_n[0], A[1]);
    and ga6(N[3], A[0], A[1]);
    and ga7(D[0], N[0], EN);
    and ga8(D[1], N[1], EN);
    and ga9(D[2], N[2], EN);
    and ga10(D[3], N[3], EN);

endmodule
```

2.

```
module circuit2(A, B, C, D, X, Y);
    input A, B, C, D;
    output X, Y;

    wire n1, n2, n3, n4, n5;


    not gn0(n1, D);
    and ga1(n2, B, C);
    nor gr2(n3, n1, A);
    nand gd3(n4, n1, n3);
    or go4(n5, n1, n2);
    and ga5(X, n4, n5);
    and ga6(Y, n3, n5);

endmodule
```


3.

```
module circuit3(X, F);  
  input [2:0] X;  
  output F;  
  
  wire [1:5] w;  
  
  nand gd1(w[1], X[2], X[1]);  
  nand gd2(w[2], X[2], w[1]);  
  nand gd3(w[3], X[1], w[1]);  
  nand gd4(w[4], w[2], w[3], X[0]);  
  nand gd5(w[5], w[3], X[0]);  
  nand gd6(F, w[4], w[5]);  
  
endmodule
```

4.

 

 5. Use Karnaugh maps to optimize both f and g to two-level logic to obtain:



6.

```

module priority_encoder(D, A, V);
  input [3:0] D;
  output [1:0] A;
  output V;

  assign V = D[0] | D[1] | D[2] | D[3];

  assign A = D[3] ? 2'b11
            : D[2] ? 2'b10
            : D[1] ? 2'b01
            : D[0] ? 2'b00
            : 2'bxx;

endmodule

```

7.

```

module jk_ff_sr(CLK, J, K, S, R, Q);
  input CLK, J, K, S, R;
  output Q;

  reg Q;

  always @(negedge CLK) begin
    if (S) Q <= 1'b1;
    else if (R) Q <= 1'b0;
    else Q <= ((J & ~Q) | (~K & Q));
  end

endmodule

```

8.

```
module mux_case(S, D, Y);
  input[1:0] S;
  input[3:0] D;
  output reg Y;

  always @(S or D)
    case (S)
      2'b00 : Y = D[0];
      2'b01 : Y = D[1];
      2'b10 : Y = D[2];
      2'b11 : Y = D[3];
    endcase

endmodule
```

9.

```
module mux_if(S, D, Y);
  input [1:0] S;
  input [3:0] D;
  output Y;

  reg Y;

  always @(S or D) begin
    if (S == 2'b00) Y = D[0];
    else if (S == 2'b01) Y = D[1];
    else if (S == 2'b10) Y = D[2];
    else Y = D[3];
  end

endmodule
```

10.

```
module state_machine10(CLK,Clear X, Z);
  input CLK, Clear;
  input [1:2] X;
  output reg Z;

  parameter A = 2'b00, B = 2'b01, C = 2'b11, D = 2'b10;

  reg [1:0] state, next_state;

  // Next-state transition
  always @(posedge CLK, negedge Clear)
    if (clear == 0) state <= A;

    else state <= next_state;

  // Next-state inputs
  always @(X or state)
    case (state)
      A: if (X == 2'b01 || X == 2'b10) next_state = B;
         else next_state = A;
      B: if (X == 2'b10 || X == 2'b11) next_state = D;
         else next_state = A;
      C: if (X == 2'b00 || X == 2'b01) next_state = A;
         else next_state = C;
      D: if (X == 2'b00 || X == 2'b11) next_state = C;
         else next_state = B;
    endcase

  // Output function
  always @(X or state)
    case (state)
      A: Z = (X == 2'b10) ? 1'b1 : 1'b0;
      B: Z = (X == 2'b10 || X == 2'b11) ? 1'b1 : 1'b0;
      C: Z = (X == 2'b00 || X == 2'b10) ? 1'b1 : 1'b0;
      D: Z = (X == 2'b11) ? 1'b0 : 1'b1;
    endcase

endmodule
```

11.

```
module state_machine11(CLK,Clear X, Z);
    input CLK,Clear X;
    output reg Z;

    parameter A = 3'b000, B = 3'b001, C = 3'b010,
              D = 3'b011, E = 3'b100, F = 3'b101;

    reg [2:0] state, next_state;

    // Next-state and output transitions
    always @(posedge CLK or negedge Clear)
        if (clear == 0) state <= A;
        else state <= next_state;

    // Next-state inputs
    always @(X or state)
        case (state)
            A: if (X) next_state = D; else next_state = B;
            B: if (X) next_state = C; else next_state = D;
            C: if (X) next_state = F; else next_state = A;
            D: if (X) next_state = C; else next_state = F;
            E: if (X) next_state = E; else next_state = C;
            F: if (X) next_state = F; else next_state = E;
        endcase

    // Next-output function
    always @(state) begin
        case (state)
            A: next_z = 0;
            B: next_z = 0;
            C: next_z = 0;
            D: next_z = 1;
            E: next_z = 1;
            F: next_z = 1;
        endcase
    end

endmodule
```