

1.

$$X \oplus Y$$

$$\begin{aligned} \text{Dual: } X\bar{Y} + \bar{X}Y &= (X + \bar{Y})(\bar{X} + Y) \\ &= \overline{(X + \bar{Y})(\bar{X} + Y)} \\ &= \overline{\bar{X}Y + X\bar{Y}} \\ &= \overline{X \oplus Y} \end{aligned}$$

$$2. F = ABCD + A\bar{D} + \bar{A}D$$

$$= ABCD + A \oplus D$$

$$= A \oplus D + \overline{A \oplus D} \cdot ABCD$$

$$= A \oplus D (ABCD + \overline{ABCD}) + \overline{A \oplus D} \cdot ABCD$$

$$= A \oplus D \cdot ABCD + A \oplus D \cdot \overline{ABCD} + \overline{A \oplus D} \cdot ABCD$$


$$= A \oplus D \cdot \overline{ABCD} + A \oplus D \cdot ABCD$$

$$= (\bar{A}D + A\bar{D}) \cdot ABCD + A \oplus D \cdot ABCD$$


$$= A \oplus D \oplus ABCD$$

$$A+B = A + \bar{A}B$$


3a)

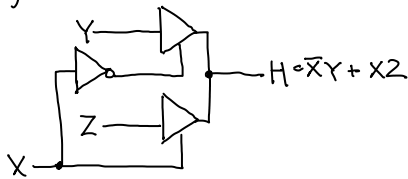

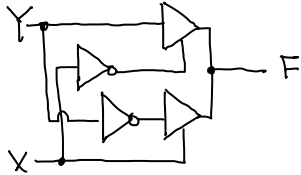b) $F = X \oplus Y = X\bar{Y} + \bar{X}Y$



4. a)

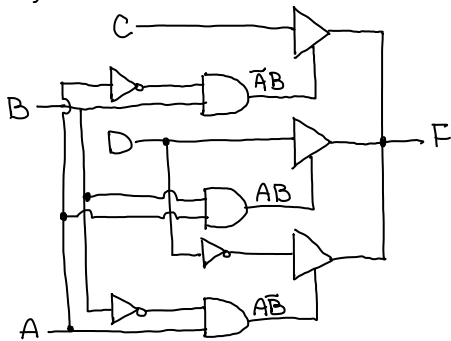

b) No conflicts

5. for the tic-tac-toe grid:

X_1	X_2	X_3
X_4	X_5	X_6
X_7	X_8	X_9

a) for winning combinations:

$$W = X_1X_2X_3 + X_4X_5X_6 + X_7X_8X_9 + \\ X_1X_4X_7 + X_2X_5X_8 + X_3X_6X_9 + \\ X_1X_5X_9 + X_3X_5X_7$$

$$(GIC = 32)$$

$$\text{literals} = 24$$

$$\text{terms} = 8$$




b) $W = X_5(X_4X_6 + X_2X_8 + X_1X_9 + X_3X_7) + \\ X_1(X_2X_3 + X_4X_7) + X_9(X_7X_8 + X_3X_6)$

$$\text{literals} = 21$$

$$\text{term} = 10$$

$$(GIC = 31)$$

A B C D	Decimal	$\sqrt{\text{Decimal}}$	X Y Z
0 0 0 0	0	0	0 0 0
0 0 0 1	1	1	0 0 1
0 0 1 0	2	1.41	0 0 1
0 0 1 1	3	1	0 1 0
0 1 0 0	4	2	0 1 0
0 1 0 1	5	2.24	0 1 0
0 1 1 0	6	2.45	0 1 0
0 1 1 1	7	2.65	0 1 1
1 0 0 0	8	2.83	0 1 1
1 0 0 1	9	3	0 1 1
1 0 1 0	10	3.16	0 1 1
1 0 1 1	11	3.32	0 1 1
1 1 0 0	12	3.46	0 1 1
1 1 0 1	13	3.61	1 0 0
1 1 1 0	14	3.74	1 0 0
1 1 1 1	15	3.87	1 0 0

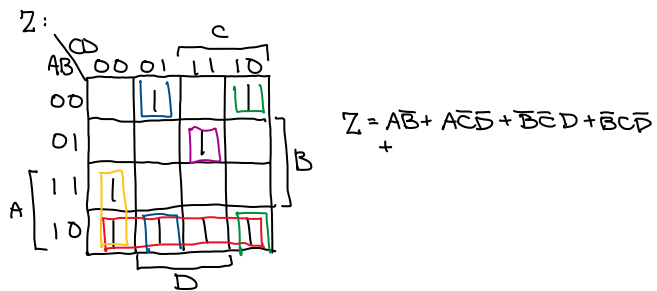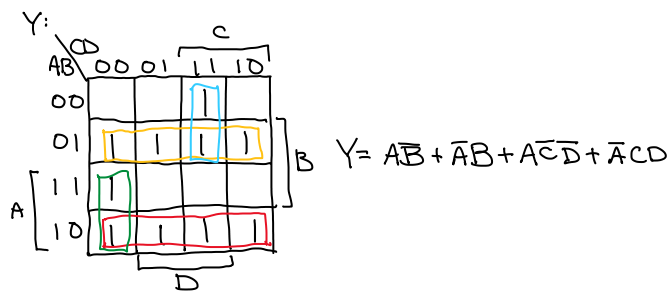
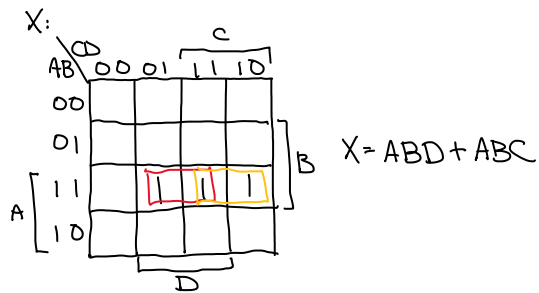


$$\text{Let } F_2 = X\bar{Y} + \bar{X}Y$$

$$\begin{aligned} \bar{F}_2 &= \overline{X\bar{Y} + \bar{X}Y} = (\bar{X} + Y)(X + \bar{Y}) \\ &= \bar{X}X + \bar{X}\bar{Y} + XY + Y\bar{Y} \\ &= \bar{X}\bar{Y} + XY \end{aligned}$$


$$\Rightarrow F_0 = Z\bar{F}_2 + \bar{Z}F_2$$

$$\Rightarrow F_1 = \bar{W}F_2 + WF_2$$

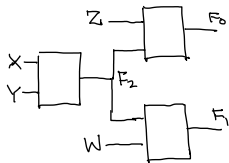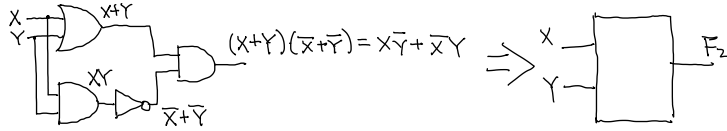


$$\begin{aligned} F_0 &= Z(X\bar{Y} + \bar{X}\bar{Y}) + \bar{Z}(\bar{X}Y + X\bar{Y}) \\ F_1 &= \bar{W}(\bar{X}Y + X\bar{Y}) + W(X\bar{Y} + \bar{X}\bar{Y}) \end{aligned}$$


8.

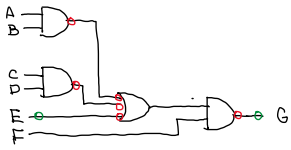


↓ NAND

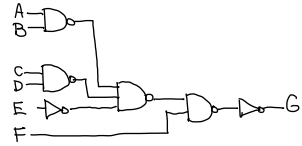






9. Repeat Q8 circuit using NOR gate.

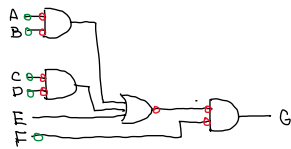

↓ NOR

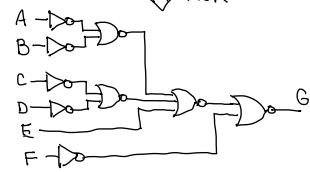


10.

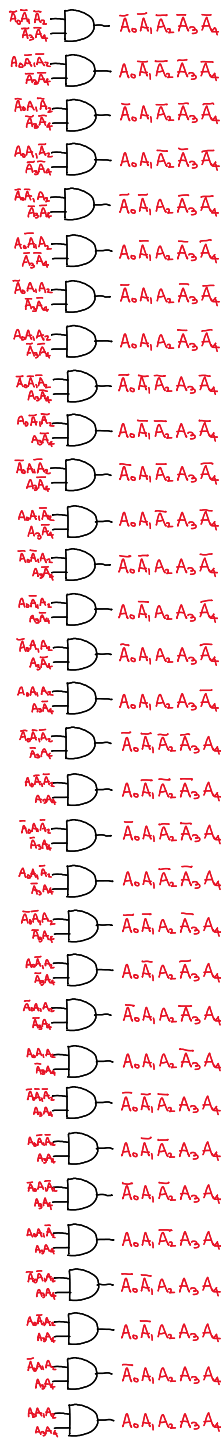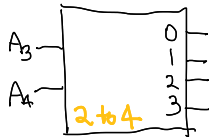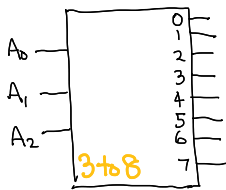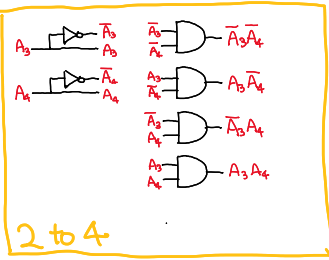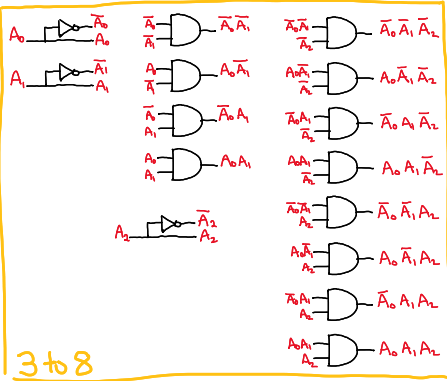





a)

x_2	x_1	x_0	a	b	c	d	e	f	g	
0	0	0	x	x	x	x	x	x	x	m_0
0	0	1	0	0	0	1	0	0	0	m_1
0	1	0	1	0	0	0	0	0	1	m_2
0	1	1	1	0	0	1	0	0	1	m_3
1	0	0	1	1	0	0	0	1	1	m_4
1	0	1	1	1	0	1	0	1	1	m_5
1	1	0	1	1	1	0	1	1	1	m_6
1	1	1	x	x	x	x	x	x	x	m_7

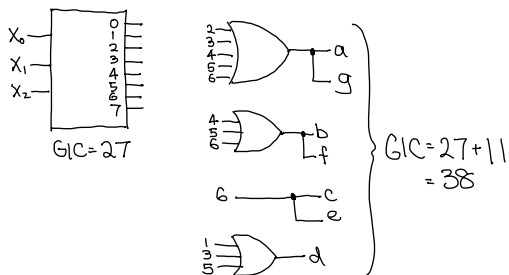Note $a \equiv g$, $b \equiv f$, $c \equiv e$



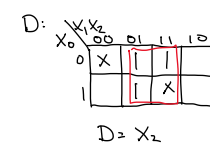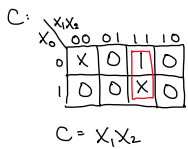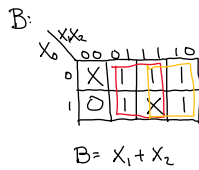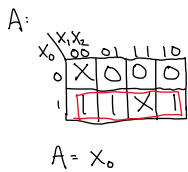- b)
- $A = \{d\}$
 - $B = \{a, g\}$
 - $C = \{c, e\}$
 - $D = \{b, f\}$





GIC=4


12.

D_3	D_2	D_1	D_0	A_1	A_2	V
0	0	0	0	X	X	0
X	X	X	1	0	0	1
X	X	1	0	0	1	1
X	1	0	0	1	0	1
1	0	0	0	1	1	1

$$V = D_0 + D_1 + D_2 + D_3$$

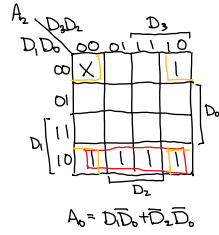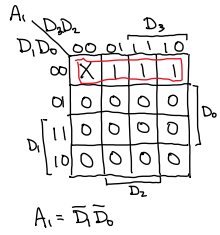

13.

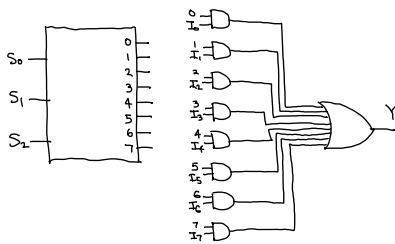


$$F_1 = \sum m(1, 2, 4)$$

$$\begin{aligned} F_2 &= \bar{x}\bar{y}\bar{z} + yz \\ &= \bar{x}\bar{y}\bar{z} + (x+\bar{x})yz \\ &= \bar{x}\bar{y}\bar{z} + xy\bar{z} + \bar{x}yz + x\bar{y}z \\ &= \sum m(0, 3, 7) \end{aligned}$$

$$\begin{aligned} F_3 &= yz + xy \\ &= (x+\bar{x})yz + (z+\bar{z})xy \\ &= xy\bar{z} + \bar{x}yz + x\bar{y}z + x\bar{y}\bar{z} + xy\bar{z} \\ &= \sum m(3, 6, 7) \end{aligned}$$
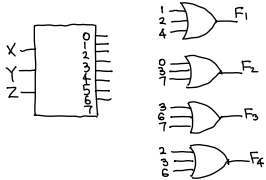
$$\begin{aligned} F_4 &= \bar{x}y + x\bar{y}\bar{z} \\ &= (z+\bar{z})\bar{x}y + x\bar{y}\bar{z} \\ &= \bar{x}yz + \bar{x}y\bar{z} + x\bar{y}\bar{z} \\ &= \sum m(2, 3, 6) \end{aligned}$$



- a) i) Left rear lamp (LR) will be ON and blinking (BL) when left turn switch (LT) or emergency flasher switch (EM) are ON. When break switch (BR) is applied, it will override emergency flasher switch (EM). When left turn switch (LT) is ON, break switch (BR) will be overridden.


$$LR = BL \cdot (LT + EM \cdot \overline{BR}) + BR \cdot \overline{LT}$$

- ii) Right rear lamp (RR) will be ON and blinking (BL) when right turn switch (RT) or emergency flasher switch (EM) are ON. When break switch (BR) is applied, it will override emergency flasher switch (EM). When right turn switch (RT) is ON, break switch (BR) will be overridden.

$$RR = BL \cdot (RT + EM \cdot \overline{BR}) + BR \cdot \overline{RT}$$


b)

	A ₃	A ₂	A ₁	A ₀	
	LJ/RT	EM	BR	BL	LR/RR
	0	0	0	0	0
	0	0	0	1	0
	0	0	1	0	1
	0	0	1	1	1
	0	1	0	0	0
	0	1	0	1	1
	0	1	1	0	0
	0	1	1	1	0
	1	0	0	0	0
	1	0	0	1	1
	1	0	1	0	0
	1	0	1	1	1
	1	1	0	0	0
	1	1	0	1	1
	1	1	1	0	0
	1	1	1	1	1

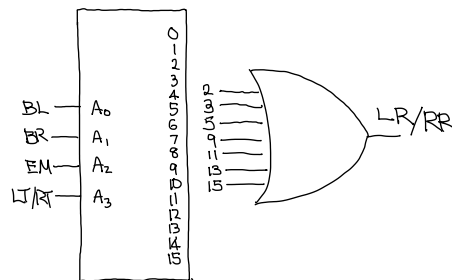

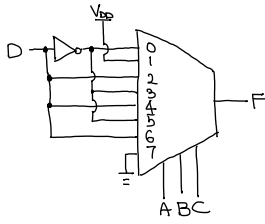16) Using Shannon's expansion, ABC as select

$$\begin{aligned}
 F &= \bar{A}\bar{B}\bar{C}\bar{D} + \bar{A}\bar{B}C\bar{D} + \bar{A}B\bar{C}D + \bar{A}B\bar{C}\bar{D} + \\
 &\quad \bar{A}B\bar{C}\bar{D} + A\bar{B}\bar{C}D + A\bar{B}C\bar{D} + A\bar{B}\bar{C}D \\
 &= \bar{A}\bar{B}\bar{C}(\bar{D}) + \bar{A}\bar{B}C(\bar{D}) + \bar{A}B\bar{C}(D) + \\
 &\quad \bar{A}B\bar{C}(\bar{D}) + A\bar{B}\bar{C}(D) + A\bar{B}C(\bar{D}) + A\bar{B}\bar{C}(D) + \\
 &\quad A\bar{B}C(\bar{D})
 \end{aligned}$$



17)

$$\begin{aligned}
 F &= \bar{A}\bar{B}\bar{C}D + \bar{A}\bar{B}CD + \bar{A}B\bar{C}\bar{D} + \bar{A}B\bar{C}D + \\
 &\quad A\bar{B}\bar{C}\bar{D} + A\bar{B}\bar{C}D + A\bar{B}C\bar{D} + A\bar{B}CD \\
 &= \bar{A}\bar{B}(\bar{C}D + CD) + \bar{A}B(\bar{C}\bar{D}) + A\bar{B}(C\bar{D}) + \\
 &\quad AB(\bar{C}\bar{D} + \bar{C}D + C\bar{D} + CD)
 \end{aligned}$$

