

The University of New South Wales
ELEC2141: Digital Circuit Design
Tutorial Week 10 – Digital IC Logic Families

1. Following are the specifications for the Schottky TTL 74S00 quadruple two-input NAND gates:

Parameter	Name	Value
VCC	Supply Voltage	5V
ICCH	High-level supply current (four gates)	10mA
ICCL	Low-level supply current (four gates)	20mA
VOH	High-level output voltage (min)	2.7V
VOL	Low-level output voltage (max)	0.5V
VIH	High-level input voltage (min)	2V
VIL	Low-level input voltage (max)	0.8V
IOH	High-level output current (max)	1mA
IOL	Low-level output current (max)	20mA
IIH	High level input current(max)	0.05mA
IIL	Low level input current (max)	2mA
tPLH	Low-to-high delay	3ns
tPHL	High-to-low delay	3ns

Calculate the fan-out, power dissipation, propagation delay, and noise margin of the Schottky NAND gate.

- 2.
- Determine the high-level output voltage of the RTL gate for a fan-out of 5.
 - Determine the minimum input voltage required to drive an RTL transistor to saturation when $h_{fe} = 20$.
 - From the results in parts (a) and (b), determine the noise margin of the RTL gate when the input is high and the fan-out is 5.
3. Show that the output transistor of the DTL gate given in Fig. 1 goes into saturation when all inputs are high. Assume that $h_{fe} = 20$.

 


Fig. 1

4. Connect the output Y of the DTL gate (Fig. 1) to N inputs of other, similar gates. Assume that the output transistor is saturated and its base current is 0.44mA. Let $h_{fe} = 20$.
 - a. Calculate the current in the 2-K Ω resistor.
 - b. Calculate the current coming from each input connected to the gate.
 - c. Calculate the total collector current in the output transistor as a function of N.
 - d. Find the value of N that will keep the transistor in saturation.
 - e. What is the fan-out of the gate?
5. Let all inputs in the open-collector TTL gate given in Fig. 2 be in the high state of 3V.
 - a. Determine the voltages in the base, collector, and emitter of all transistors in the circuit.
 - b. Determine the minimum h_{fe} of Q2 which ensures that this transistor saturates.
 - c. Calculate the base current of Q3.
 - d. Assume that the minimum h_{fe} of Q3 is 6.18. What is the maximum current that can be tolerated in the collector to ensure saturation of Q3?
 - e. What is the minimum value of R_L that can be tolerated to ensure saturation of Q3?

 


Fig 2

6. For the following conditions, list the transistors that are off and the transistors that are conducting in the three-state TTL gate of Fig. 3 (for Q1 and Q6, it is necessary to list the states in the base-emitter and base-collector junctions separately):
 - a. When C is low and A is low.
 - b. When C is low and A is high.
 - c. When C is high.

What is the state of the output in each case?

 


Fig. 3

7. Find the logic function realized by the following CMOS circuit in Fig. 4.

 


Fig. 4

8. Derive a CMOS complex gate for each of the following functions:

- a. $F = XY + XZ$
- b. $F = XY + XZ + YZ$
- c. $F = \overline{XY + WZ}$
- d. $F = A \oplus B \oplus C$

9. Find the CMOS complex gate circuit for each of the following functions. In each case, use a minimum number of transistors.

- a. $F(X, Y, Z) = YZ + \bar{X}Z + \bar{X}Y\bar{Z}$
- b. $F(A, B, C, D) = A\bar{D} + A\bar{B} + BD + BC$

10. Find the CMOS complex gate circuit for each of the following functions:

- a. $F(A, B, C, D) = (A + \bar{C})(\bar{A} + C)(B + \bar{D})(\bar{B} + D)$
- b. $F(W, X, Y, Z) = \sum m(4, 7, 9, 11, 12, 13, 14, 15) + d(3, 10)$

11. Construct a 4-to-1-line multiplexer using transmission gates and inverters.