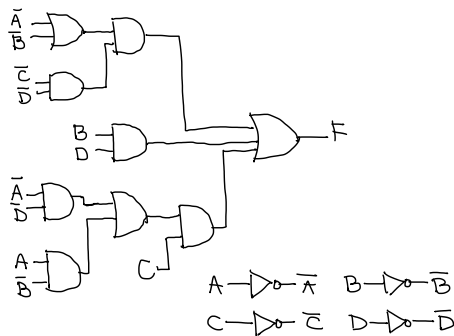


Question 1 F


Saturday, 7 March 2020 6:20 pm

- a) i) Literals = 11
Terms = 8 ← $\overline{C}\overline{D}(\overline{A}+\overline{B}) + BD + C(\overline{A}\overline{D} + A\overline{B})$
Complements = 4
GIC = 23

Students may draw logic diagram to determine GIC



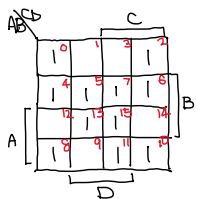- ii) Students can use the K-map to find the minterms for F or use algebraic expansion




OR

$$\begin{aligned} F &= \overline{C}\overline{D}(\overline{A}+\overline{B}) + BD + C(\overline{A}\overline{D} + A\overline{B}) \\ &= \overline{A}\overline{C}\overline{D} + \overline{B}\overline{C}\overline{D} + BD + \overline{A}C\overline{D} + A\overline{B}C \\ &= \overline{A}\overline{C}\overline{D}(B+B) + \overline{B}\overline{C}\overline{D}(A+A) + BD(\overline{A}+A)(\overline{C}+C) + \overline{A}C\overline{D}(\overline{B}+B) + A\overline{B}C(\overline{D}+D) \end{aligned}$$

$$F = \sum m(0, 2, 4, 5, 6, 7, 8, 10, 11, 13, 15)$$

iii)


A	B	C	D	F	m_i
0	0	0	0	1	m_0
0	0	0	1	0	m_1
0	0	1	0	1	m_2
0	0	1	1	0	m_3
0	1	0	0	1	m_4
0	1	0	1	1	m_5
0	1	1	0	1	m_6
0	1	1	1	1	m_7
1	0	0	0	1	m_8
1	0	0	1	0	m_9
1	0	1	0	1	m_{10}
1	0	1	1	1	m_{11}
1	1	0	0	0	m_{12}
1	1	0	1	1	m_{13}
1	1	1	0	0	m_{14}
1	1	1	1	1	m_{15}

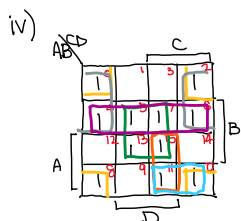

$$\left. \begin{aligned} F &= \overline{B}\overline{D} + BD + \overline{A}\overline{B} + ACD \\ \text{or } F &= \overline{B}\overline{D} + BD + \overline{A}\overline{D} + A\overline{B}C \\ \text{or } F &= \overline{B}\overline{D} + BD + \overline{A}B + ACD \\ \text{or } F &= \overline{B}\overline{D} + BD + \overline{A}B + A\overline{B}C \end{aligned} \right\} \text{SOP any one is correct.}$$

$$\text{PI : } \overline{B}\overline{D}, BD, \overline{A}\overline{B}, ACD, A\overline{B}C, \overline{A}B$$
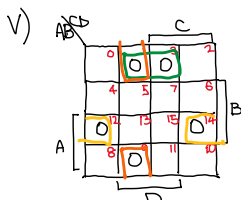
$$\text{EPI : } \overline{B}\overline{D}, BD$$



$$F = (\bar{A} + \bar{B} + D)(B + C + \bar{D})(A + B + \bar{D}) \leftarrow \text{POS}$$


$$\text{PI: } \bar{A} + \bar{B} + D, B + C + \bar{D}, A + B + \bar{D}$$

$$\text{EPI: } \bar{A} + \bar{B} + D, B + C + \bar{D}, A + B + \bar{D}$$

$$\begin{aligned} \text{vi)} \quad & \text{literals} = 9 \\ & \text{terms} = 4 \\ & \text{complements} = 3 \\ & \hline & \text{GIC} = 16 \end{aligned}$$

Reduction of 7 GIC after optimisation
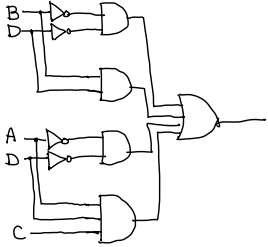
$$\text{vii)} \quad F = \bar{B}\bar{D} + BD + \bar{A}\bar{B} + ACD$$



$$\begin{array}{ccc} \text{b) binary} & \text{hexadecimal} & \text{octal} \\ \hline 11101010.111 & \text{EA.E} & 352.7 \end{array}$$

Hex \rightarrow binary


$$\begin{array}{ccccccc} 1 & 1 & 1 & 0 & 1 & 0 & 1 & 0 & . & 1 & 1 & 1 & 0 \\ \hline & \text{E} & \text{A} & . & \text{E} & & & & & & & & \end{array} \leftarrow \text{Hex}$$

Binary \rightarrow octal

$$\begin{array}{ccccccc} 0 & 1 & 1 & 1 & 0 & 1 & 0 & 1 & 0 & . & 1 & 1 & 1 \\ \hline & 3 & 5 & 2 & . & 7 & & & & & & & \end{array} \leftarrow \text{octal}$$

c) A - D latch

B - Positive edge triggered D flipflop

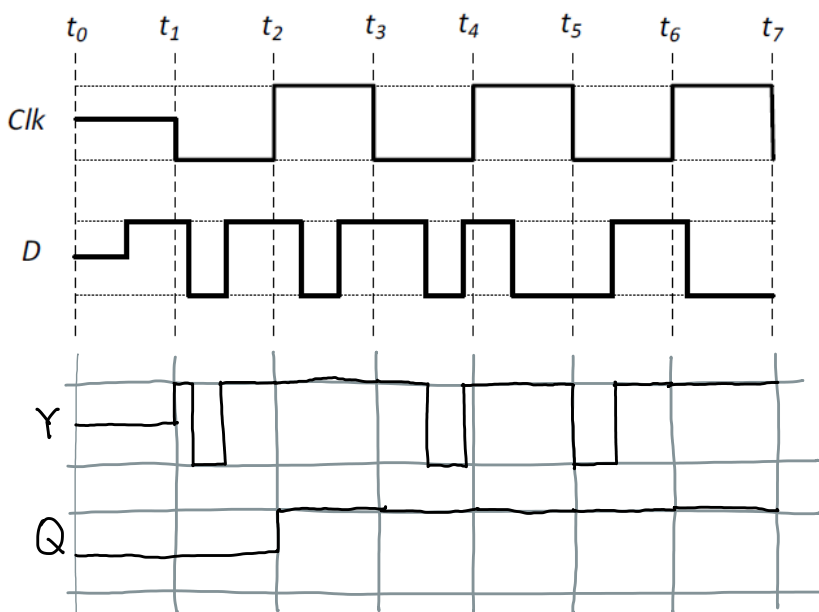

Question 2 F

Saturday, 7 March 2020 8:31 pm


a) i) $X + Y = X \oplus Y + XY$

$$\begin{aligned} X \oplus Y + XY &= X\bar{Y} + \bar{X}Y + XY \\ &= X\bar{Y} + XY + XY + \bar{X}Y \\ &= X(\bar{Y} + Y) + Y(X + \bar{X}) \\ &= X + Y \end{aligned}$$

ii) $H(A, B, C) = A\bar{B} + AB\bar{C} + \bar{A}B$

$$\begin{aligned} &= A\bar{B} + AB\bar{C} \\ &= A\bar{B} \oplus AB\bar{C} + (A\bar{B})(AB\bar{C}) \\ &= A\bar{B} \oplus AB\bar{C} + (\bar{A}\bar{B} + \bar{A}B)(AB\bar{C}) \\ &= A\bar{B} \oplus AB\bar{C} \end{aligned}$$


$$X + Y = X \oplus Y + XY$$

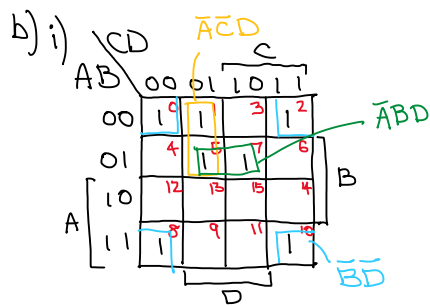

$$G = \sum m(3, 4, 6, 9, 11, 12, 13, 14, 15)$$

$$\begin{aligned} &= \bar{A}\bar{B}\bar{C}\bar{D} + \bar{A}\bar{B}\bar{C}D + \bar{A}\bar{B}C\bar{D} + \bar{A}\bar{B}CD + \bar{A}B\bar{C}\bar{D} + \bar{A}B\bar{C}D + \bar{A}B\bar{C}\bar{D} + \bar{A}B\bar{C}D \\ &+ \bar{A}B\bar{C}\bar{D} \\ &= \bar{A}\bar{B}\bar{D}(\bar{C} + C) + \bar{A}\bar{B}C(\bar{D} + D) + \bar{A}B\bar{D}(\bar{C} + C) + \bar{A}B\bar{C}(\bar{D} + D) \\ &= \bar{A}\bar{B}\bar{D} + \bar{A}\bar{B}C + \bar{A}B\bar{D} + \bar{A}B\bar{C} \\ &= \bar{B}\bar{D}(\bar{A} + A) + \bar{A}\bar{B}C + \bar{A}B\bar{D} \\ &= \bar{B}\bar{D} + \bar{A}\bar{B}C + \bar{A}B\bar{D} \end{aligned}$$

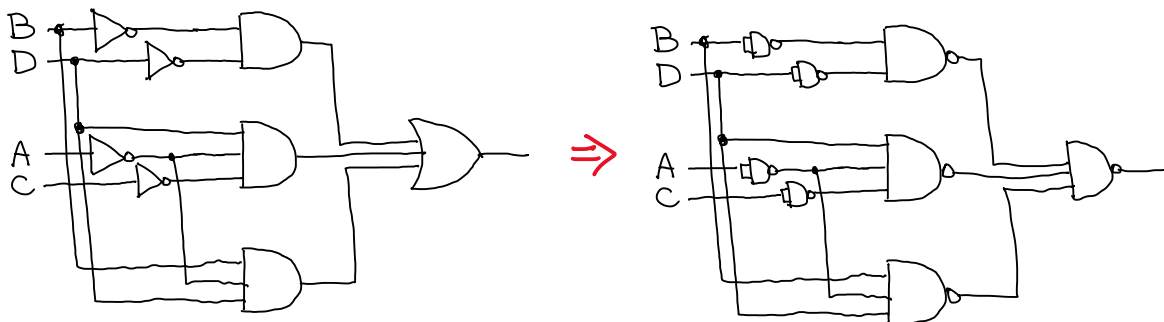ii) $G = \bar{B}\bar{D} + \bar{A}\bar{B}C + \bar{A}B\bar{D}$



c) i)


A	B	C	D	Z
0	0	0	0	0
0	0	0	1	1
0	0	1	0	0
0	0	1	1	1
0	1	0	0	1
0	1	0	1	0
0	1	1	0	1
0	1	1	1	0
1	0	0	0	1
1	0	0	1	0
1	0	1	0	1
1	0	1	1	0
1	1	0	0	1
1	1	0	1	0
1	1	1	0	1
1	1	1	1	0

$Z = D$

$Z = \bar{D}$

$Z = \bar{B}$

$Z = \bar{B}$

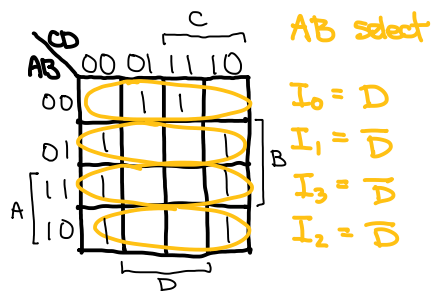


CD select



$I_0 = A+B$
 $I_1 = \bar{A}\bar{B}$
 $I_2 = A+B$
 $I_3 = \bar{A}\bar{B}$

Note: Using CD as select would not give the simplest design.

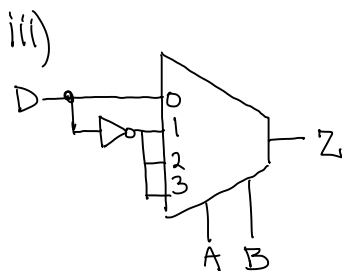
ii) $Z = \sum m(1, 3, 4, 6, 8, 10, 12, 14)$




d) Not required!

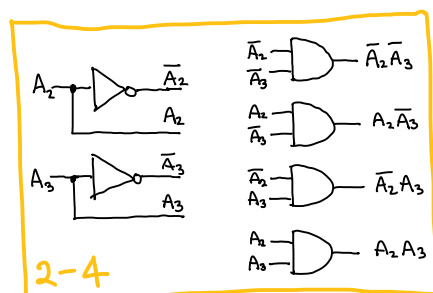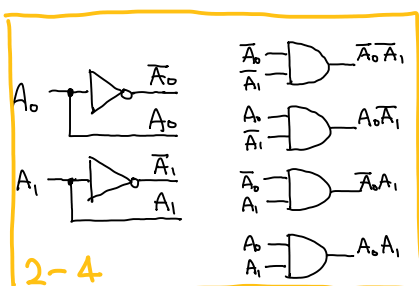

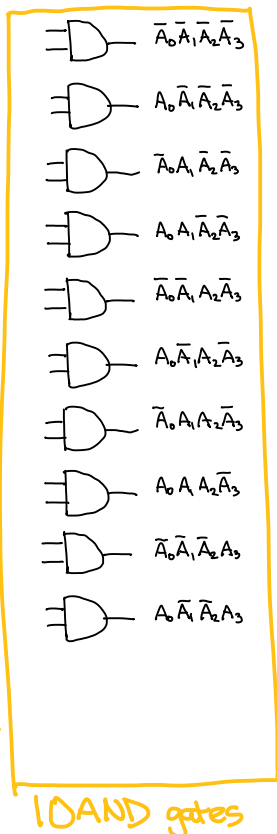GIC = $4 + 4 \times 2 + 4 \times 2 + 10 \times 2$
 $= 40$



Block diagram

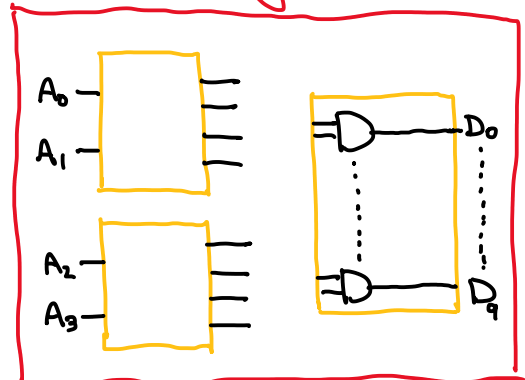

Refer to Week 3 slide 51

- Input n is even, $n=4$.

Use 2^n AND gates driven by two decoders of output size $2^{n/2} = 4$

Since BCD is only from 0 to 9, 16-X-1 AND gates will be redundant.