

Tutorial Week 6 – Sequential Circuits Analysis


1. **(4-5)** A sequential circuit with a D flip-flop A , two inputs X and Y , and one output Z is specified by the following input equations

$$D_A = A\bar{Y} + XY\bar{A} + A\bar{X}, \quad Z = A$$


- a. Draw the logic diagram of the circuit
 - b. Derive the state table
 - c. Derive the state diagram
 - d. Is this a Mealy or Moore machine
2. **(4-6)** A sequential circuit with two D flip-flops A and B , one input X and one output Y is specified by the following input equations:

$$Y = \bar{A} + B, \quad D_A = X + B, \quad D_B = X\bar{A}$$

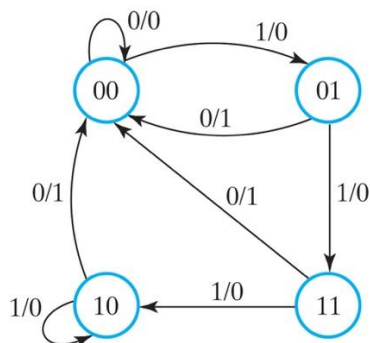- a. Draw the logic diagram of the circuit
 - b. Derive the state table
 - c. Derive the state diagram
 - d. Is this a Mealy or Moore machine
3. **(4-9)** Starting from state 00 in the following state diagram, determine the state transitions and output sequence that will be generated when an input sequence of 10011011110 is applied.



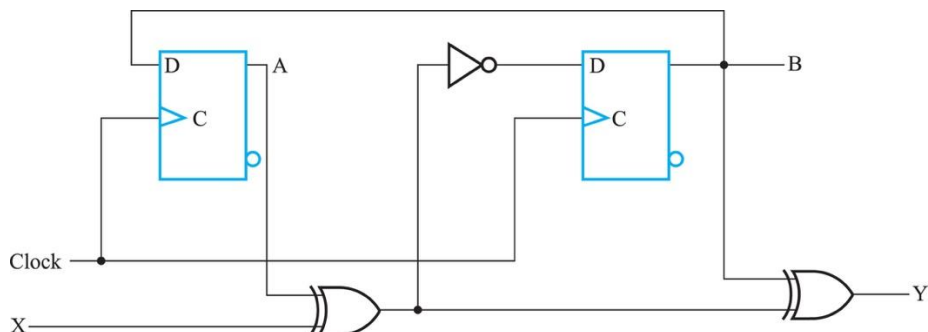4. **(4-11)** A sequential circuit with two D flip-flops A and B , one input X and one output Y . The logic circuit is shown below. Derive the state table and state diagram of the circuit.




Where referenced, questions are taken from the textbook:

M. Mano, C. R. Kime and T. Martin, *Logic and Computer Design Fundamentals, 5th Edition (Global Edition)*, Pearson, 2016

5. **(4-10)** Draw the state diagram of the sequential circuit specified by the state table given below

Present state		Inputs		Next state		Output
A	B	X	Y	A	B	Z
0	0	0	0	1	0	0
0	0	0	1	1	1	1
0	0	1	0	1	1	0
0	0	1	1	1	1	1
0	1	0	0	0	1	1
0	1	0	1	0	0	0
0	1	1	0	0	0	1
0	1	1	1	0	0	0
1	0	0	0	1	1	1
1	0	0	1	0	1	1
1	0	1	0	0	1	0
1	0	1	1	1	0	0
1	1	0	0	0	0	0
1	1	0	1	0	1	0
1	1	1	0	1	0	1
1	1	1	1	1	1	1

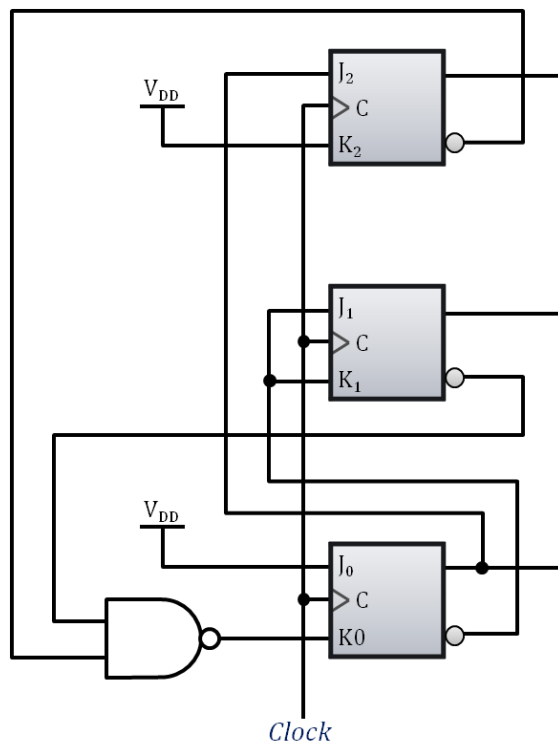6. Construct a state diagram for the counting sequence generated by the follow circuit.



7. Draw the state diagram for the sequential circuit specified by the state table below.

Current State q_1q_0	Next State, Output			
	$XY = 00$ Q_1Q_0, Z	$XY = 01$ Q_1Q_0, Z	$XY = 10$ Q_1Q_0, Z	$XY = 11$ Q_1Q_0, Z
00	00, 0	01, 0	10, 1	11, 1
01	01, 1	10, 1	10, 0	00, 0
10	11, 1	11, 0	11, 1	10, 0
11	00, 0	00, 1	00, 0	01, 0

8. A sequential circuit has two JK flip-flops A and B and one input x . The circuit is described by the following flip-flop input equations:

$$\begin{aligned} J_A &= X & K_A &= \bar{B} \\ J_B &= X & K_B &= A \end{aligned}$$

- Derive the state equations $A(t + 1)$ and $B(t + 1)$ by substituting the input equations for J and K variables
- Draw the state diagram of the circuit
- Obtain the flip-flop input equations for the equivalent sequential circuit using T flip-flops