

Question 1

i)

(3) a)

$$F = (A+B)(A+C+D) + (\bar{A}+B)(B+C+\bar{D})A$$

$$= A + \cancel{AC} + \cancel{AD} + \cancel{AB} + BC + BD + \cancel{AB} + \cancel{ABC} + \cancel{ABD}$$

$$= A + B(C+D)$$

A	B	C	D	F
0	0	0	0	0
0	0	0	1	0
0	0	1	0	0
0	0	1	1	0
0	1	0	0	0
0	1	0	1	1
0	1	1	0	1
0	1	1	1	1
1	0	0	0	1
1	0	0	1	1
1	0	1	0	1
1	0	1	1	1
1	1	0	0	1
1	1	0	1	1
1	1	1	0	1
1	1	1	1	1


(1) b)

$$F = \sum m(5, 6, 7, 8, 9, 10, 11, 12, 13, 14, 15)$$

(1) c)

$$F = \prod M(0, 1, 2, 3, 4)$$

(1) d)

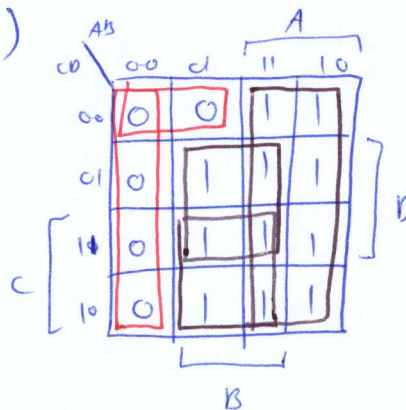

$$F = A + BC + BD$$

(2) e)

$$\bar{F} = \bar{A}\bar{B} + \bar{A}\bar{C}\bar{D}$$

$$F = \overline{\bar{A}\bar{B} + \bar{A}\bar{C}\bar{D}}$$

$$= (A+B)(A+C+D)$$

(2) f)

$$GIC = 19.$$

(i)

(3) a) $x + y = x \oplus y + xy$

\Downarrow

$$x \oplus y + xy = x\bar{y} + \bar{x}y + xy$$

$$= x\bar{y} + xy + xy + \bar{x}y$$

$$= x(\bar{y} + y) + y(x + \bar{x})$$

$$= x + y$$

(4) b)

$$G = A\bar{B} + AB\bar{C} + \bar{A}B$$

$$= \underbrace{A \oplus B}_x + \underbrace{AB\bar{C}}_y$$


$$= A \oplus B \oplus AB\bar{C} + (A \oplus B)(AB\bar{C})$$

$$= A \oplus B \oplus AB\bar{C} + (A\bar{B} + \bar{A}B)(AB\bar{C})$$

$$= A \oplus B \oplus AB\bar{C}$$

$$= A \oplus B \oplus AB(C \oplus 1)$$

(3) c)

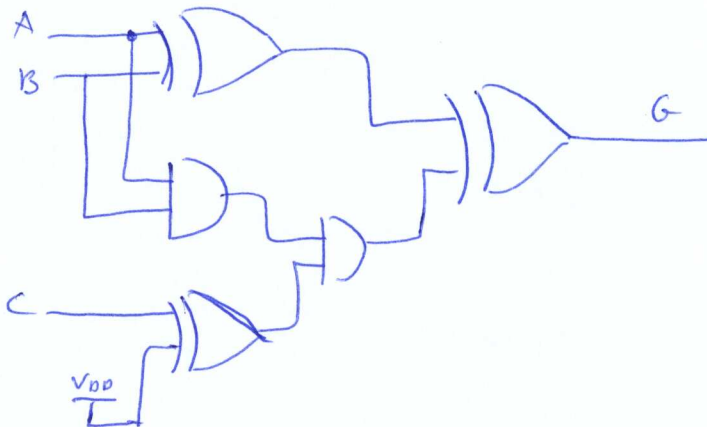

Question 2

③ i)

state	next state, output	
	x=0	x=1
A	B, 1	C, 1
B	E, 0	G, 0
C	C , 1	A, 0
D	D, 0	B, 1
E	F, 1	B , 1
F	H, 0	D, 0
G	G, 0	F, 1
H	F, 1	C, 1

⑤ ii)

B	X						
C	X	X					
D	X	X	X				
E	B~F C~C	X	X	X			
F	X	E~H D~G	X	X	X		
G	X	X	X	D~G B~F	X	X	
H	B~F C~C	X	X	X	F~F C~C	X	X
	A	B	C	D	E	F	G

$A \sim E \sim H$

$B \sim F$

$D \sim G$

state	next, output	
	x=0	x=1
A	B, 1	C, 1
B	A, 0	D, 0
C	C, 1	A, 0
D	D, 0	B, 1

⑤ iii)

state	next state		output
	x=0	x=1	
A	B	C	0
B	A	D	1
C	C	A	1
D	D	B	0

①

iv) one possibility:

	0	1
0	A	C
1	B	D

$A \sim 00$

$B \sim 01$

$C \sim 10$

$D \sim 11$

③

v)

q_1, q_0 state	q_1, q_0 next state		z output
	$x=0$	$x=1$	
00	01	10	0
01	00	11	1
10	10	00	1
11	11	01	0

D_1 :

	q_1, q_0	00	01	11	10
x	0	0	0	1	1
	1	1	1	0	0

D_0 :

	q_1, q_0	00	01	11	10
x	0	1	0	1	0
	1	0	1	1	0

z :

	q_1, q_0	00	01	11	10
q_1	0	0	1	1	0
	1	1	1	0	0

$$D_1 = \bar{x}q_1 + x\bar{q}_1$$

$$= x \oplus q_1$$

$$D_0 = q_1q_0 + xq_0 + \bar{x}\bar{q}_1\bar{q}_0$$


$$= q_1$$

$$z = q_1\bar{q}_0 + \bar{q}_1q_0$$

$$= q_1 \oplus q_0$$

③

vi)

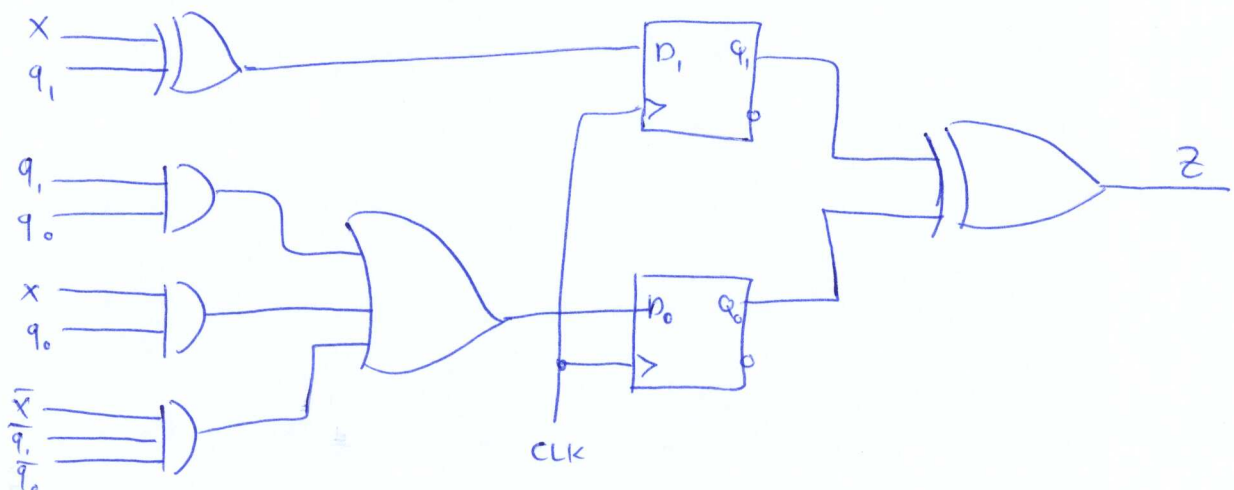

Question 3

(3) i)

$$T_2 = \bar{q}_1$$


$$T_1 = X + q_0 + q_2 q_1$$

$$T_0 = X + \bar{q}_2 \bar{q}_1$$

(10) ii)

		<u>X=0</u>		<u>X=1</u>		<u>X=0</u>		<u>X=1</u>	
	$q_2 q_1 q_0$	$T_2 T_1 T_0$		$T_2 T_1 T_0$		$q_2 q_1 q_0$		$q_2 q_1 q_0$	
S	0 0 0	1 0 1		1 1 ϕ		1 0 1		1 1 1	
T	0 0 1	1 1 1		1 1 ϕ		1 1 0		1 1 0	
E	0 1 0	0 0 0		0 1 ϕ		0 1 0		0 0 1	
R	0 1 1	0 1 0		0 1 ϕ		0 0 1		0 0 0	
A	1 0 0	1 0 0		1 1 ϕ		0 0 0		0 1 1	
W	1 0 1	1 1 0		1 1 1		0 1 1		0 1 0	
-	1 1 0	0 1 0		0 1 1		1 0 0		1 0 1	
!	1 1 1	0 1 0		0 1 1		1 0 1		1 0 0	

(4) iii)

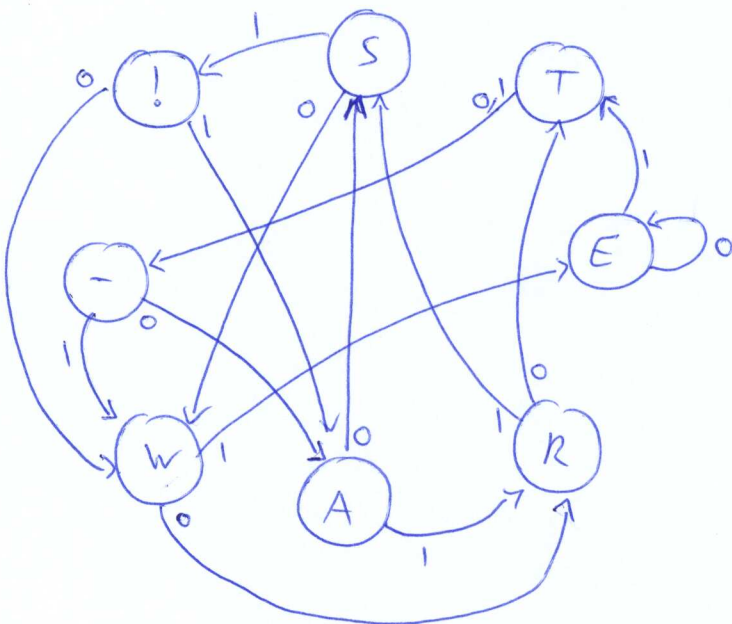

(3) iv)

state	S	W	E	E	T	-	A	S	!
x	0	1	0	1	0	0	0	0	1

Question 4

⑤ i)

$$27 / 2 = 13$$

$$r = 1$$

$$13 / 2 = 6$$

$$1$$

$$6 / 2 = 3$$

$$0$$

$$3 / 2 = 1$$

$$1$$

$$1 / 2 = 0 //$$

$$1$$

$$27_{10} = 11011_2$$

$$0.40625 \times 2 = 0.8125$$

$$I = 0$$

$$0.8125 \times 2 = 1.625$$

$$= 1$$

$$0.625 \times 2 = 1.25$$

$$1$$

$$0.25 \times 2 = 0.5$$

$$0$$

$$0.5 \times 2 = 1.0 //$$

$$1$$

$$0.40625_{10} = 0.01101_2$$

$$27.40625 = 11011.01101_2$$



⑧ ii)

$$F = X + \bar{X}\bar{Y} + \bar{Y}\bar{Z}$$

$$= X + \bar{Y} + \bar{Y}\bar{Z}$$

$$= X + \bar{Y}$$

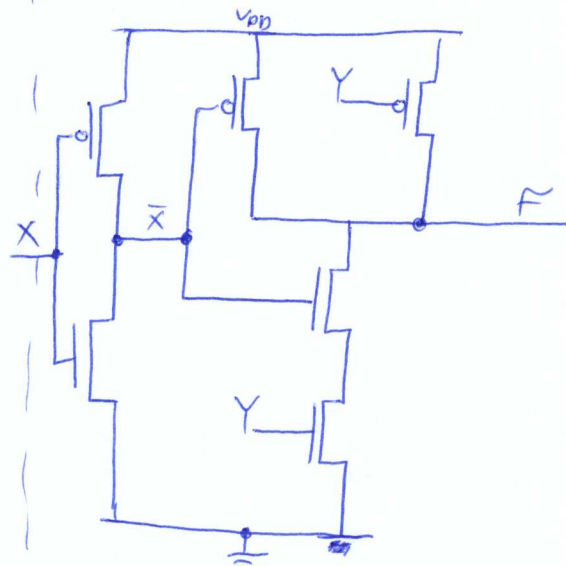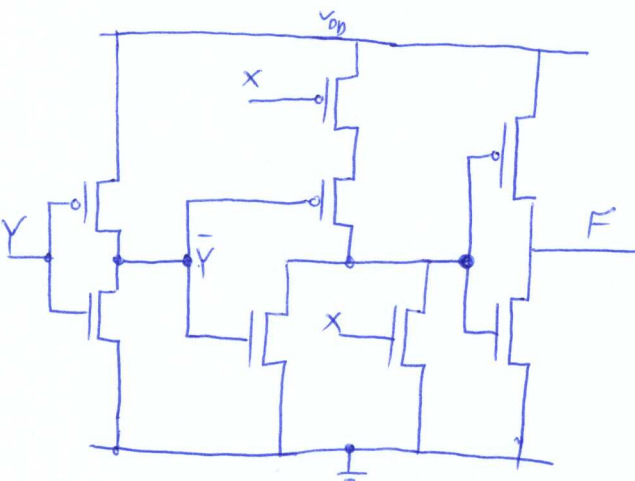Or: $\bar{F} = \overline{X + \bar{Y}} = \bar{X}Y$



7 (ii)

$$\begin{aligned} G = \overline{C(AB+D)} &= \overline{ABC+CD} = (\bar{A} + \bar{B} + \bar{C})(\bar{C} + \bar{D}) \\ &= \bar{A}\bar{C} + \bar{A}\bar{D} + \bar{B}\bar{C} + \bar{B}\bar{D} + \bar{C} + \cancel{\bar{C}\bar{D}} \\ &= \bar{C} + \bar{D}(\bar{A} + \bar{B}) \end{aligned}$$

A	B	C	D	G
0	0	0	0	1
0	0	0	1	1
0	0	1	0	1
0	0	1	1	0
<hr/>				
0	1	0	0	1
0	1	0	1	1
0	1	1	0	1
0	1	1	1	0
<hr/>				
1	0	0	0	1
1	0	0	1	1
1	0	1	0	1
1	0	1	1	0
<hr/>				
1	1	0	0	1
1	1	0	1	1
1	1	1	0	0
1	1	1	1	0

Question 5


⑥
i)

q	Q	D	J	K
0	0	0	0	X
0	1	1	1	X
1	0	0	X	1
1	1	1	X	0


$D(q, J, K)$:

J \ K	q			
	00	01	11	10
0	0	0	1	1
1	1	0	0	1

$$D = \bar{J}\bar{q} + \bar{K}q$$

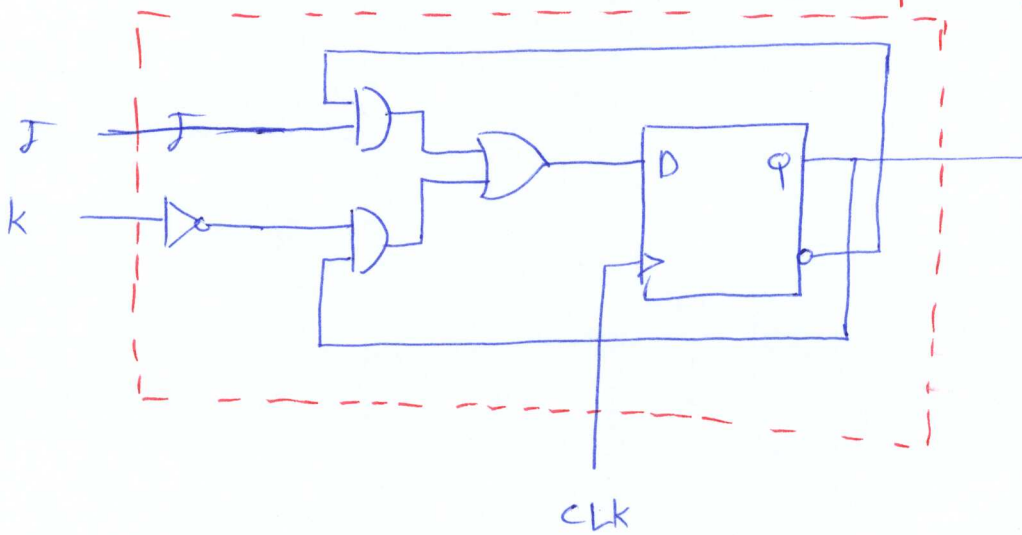

ii) ③
a)

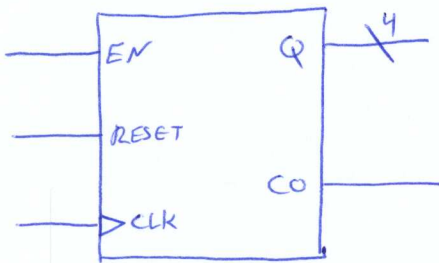

②

b) Four-bit counter with an asynchronous Reset.

5

c)

Inputs:

CLK - A clock signal to synchronize the counter

EN - Enable signal - the counter increments when $EN=1$ and keep steady when $EN=0$.

RESET - Asynchronous signal to reset the counter to 0, only resets on the positive edge of the signal.

Outputs:


Q - The 4-bit counter value.

CO - Carry-out signal. Goes HIGH when the counter is at its highest value (1111) and Low otherwise.

Can be used to cascade two counters.

4

d)

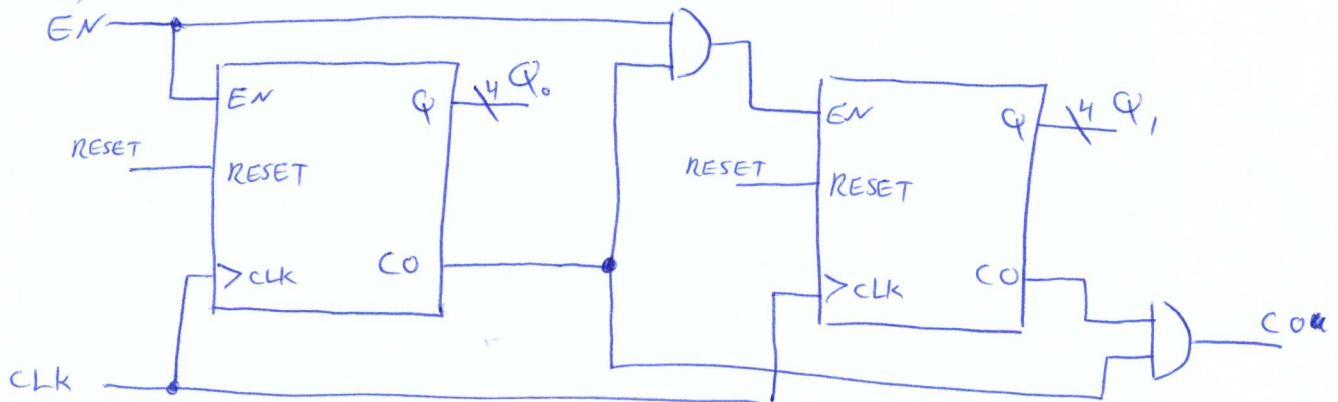

Question 6

8

i)

always @(posedge S) begin

Q <= 1;

end

always @(posedge R) begin

Q <= 0;

end

always @(negedge CLK) begin

Q <= D;

end

(i) 2

a)

$$\begin{array}{r} 01101010 \\ + 00101100 \\ \hline 10010110 \end{array}$$

2

b)

N = 1

C = 0

Z = 0

V = 1

2

c)

No overflow!

(ii) 2

a)

$$\begin{array}{r} 10010001 \\ - 00100100 \\ \hline \end{array}$$

=>

$$\begin{array}{r} 1010001 \\ + 1101100 \\ \hline 01101101 \end{array}$$

2

b)

N = 0

C = 1

Z = 0

V = 1

2

c)

Overflow!