 


1. Rewrite the Verilog description given below (from lectures) for the 2-to-4-line decoder using vector notation for inputs, outputs and wires.

3. Write a structural Verilog description of the circuit given below. Replace X , Y , and Z with `input [2:0] X`.



4. Find a logic diagram that corresponds to the Verilog structural description in the figure below. Note that complemented inputs are not available.

```
// Combinational Circuit 1: Structural Verilog Description

module comb_ckt_1(x1, x2, x3, x4, f);
    input x1, x2, x3, x4;
    output f;

    wire n1, n2, n3, n4, n5, n6;

    not gn0(n1, x1);
    not gn1(n4, n3);

    and ga2(n2, x2, n1);
    and ga3(n3, x2, x3);
    and ga4(n5, x3, x4);
    and ga5(n6, x1, n4);

    or go6(f, n2, n5, n6);

endmodule
```

5. Find a logic diagram representing minimum two-level logic needed to implement the Verilog dataflow description below. Note that complemented inputs are available.


```
// Combinational Circuit 2: Dataflow Verilog Description

module comb_ckt_2(a, b, c, d, a_n, b_n, c_n, d_n, f, g);
  input a, b, c, d, a_n, b_n, c_n, d_n;
  output f, g;

  assign f = b & (a | (a_n & c)) | (b_n & c & d_n);
  assign g = b & (c | (a_n & c_n) | (c_n & d_n));

endmodule
```

 6. Write a dataflow description for the four-input priority encoder, presented in lectures, using the binary decision dataflow concept.
7. Write a Verilog description for a JK negative edge-triggered flip-flop with clock *CLK* and synchronous set (*S*) and reset (*R*) inputs.
8. Write a Verilog description for a 4-to-1-line multiplexer by using a process containing a case statement.
9. Repeat question 8 by using a Verilog process containing if-else statements.
10. Write a Verilog description for the circuit specified by the following state diagram.



11. Write a Verilog description for the circuit specified by the following state diagram.

