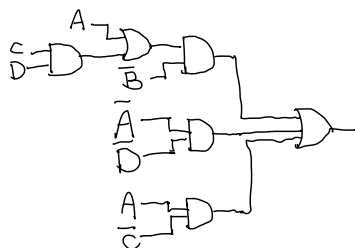


# Question 1 I

Saturday, 7 March 2020 6:20 pm

a) i) Literals = 8  
Terms = 5  
Complements = 4  
GIC = 17


$$\leftarrow \overline{B}(CD+A) + \overline{A}\overline{D} + A\overline{C}$$



Students may draw logic diagram to determine the GIC.

$$A \rightarrow \overline{A} \quad B \rightarrow \overline{B} \quad C \rightarrow \overline{C} \quad D \rightarrow \overline{D}$$

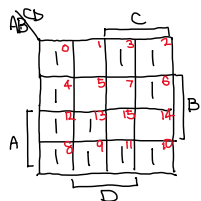ii) Students can use the K-map to find the minterms for F:




OR

$$\begin{aligned} F &= \overline{B}(CD+A) + \overline{A}\overline{D} + A\overline{C} \\ &= \overline{B}CD + \overline{A}\overline{D} + A\overline{B} + A\overline{C} \\ &= \overline{B}CD(A+\overline{A}) + \overline{A}\overline{D}(B+\overline{B})(C+\overline{C}) + A\overline{B}(C+\overline{C})(D+\overline{D}) + A\overline{C}(B+\overline{B})(D+\overline{D}) \end{aligned}$$

$$F = \sum m(0, 2, 3, 4, 6, 8, 9, 10, 11, 12, 13)$$

iii)


A	B	C	D	F	$m_i$
0	0	0	0	1	$m_0$
0	0	0	1	0	$m_1$
0	0	1	0	1	$m_2$
0	0	1	1	1	$m_3$
0	1	0	0	1	$m_4$
0	1	0	1	0	$m_5$
0	1	1	0	1	$m_6$
0	1	1	1	0	$m_7$
1	0	0	0	1	$m_8$
1	0	0	1	1	$m_9$
1	0	1	0	1	$m_{10}$
1	0	1	1	1	$m_{11}$
1	1	0	0	1	$m_{12}$
1	1	0	1	1	$m_{13}$
1	1	1	0	0	$m_{14}$
1	1	1	1	0	$m_{15}$

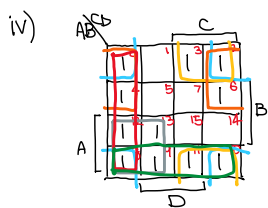

$$F = A\overline{C} + \overline{A}\overline{D} + \overline{B}C$$

$$PI: A\overline{C}, \overline{A}\overline{D}, \overline{B}C, \overline{B}\overline{D}, \overline{C}\overline{D}, A\overline{B}$$
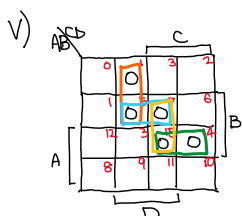
$$EPI: A\overline{C}, \overline{A}\overline{D}, \overline{B}C$$



$$F = (A+C+\overline{D})(A+\overline{B}+\overline{D})(\overline{A}+\overline{B}+\overline{C})$$

OR  $F = (A+C+\overline{D})(\overline{B}+\overline{C}+\overline{D})(\overline{A}+\overline{B}+\overline{C})$


$$\text{Essential Prime Implicants: } (A+C+\overline{D}), (\overline{A}+\overline{B}+\overline{C})$$

$$\text{Prime Implicants: } (A+C+\overline{D}), (\overline{A}+\overline{B}+\overline{C}), (\overline{B}+\overline{C}+\overline{D})$$

vi) literals = 6  
 terms = 3  
 complements = 4  
GIC = 13

Reduction of 4 GIC after optimisation

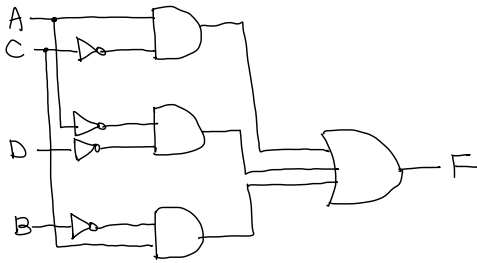vii)  $F = A\bar{C} + \bar{A}\bar{D} + \bar{B}C$




b) binary hexadecimal octal  
11101010011    3A9.8    1651.4

0011101010011000 ← binary  
 3    A    9    8 ← hex

001110101001100 ← binary  
 1    6    5    1    4 ← octal

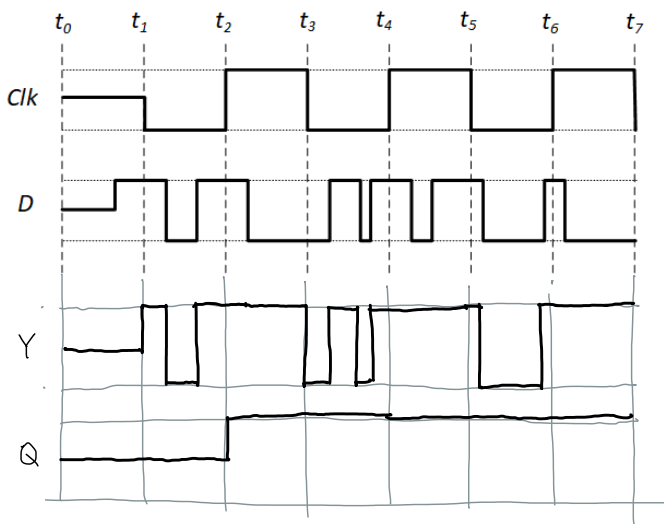c) A - D latch  
 B - Positive edge triggered D Flip-flop



## Question 2 I


Saturday, 7 March 2020 8:31 pm

a) i)  $A+B = A \oplus B + AB$

$$\begin{aligned} A \oplus B + AB &= A\bar{B} + \bar{A}B + AB \\ &= A\bar{B} + AB + AB + \bar{A}B \\ &= A(\bar{B}+B) + B(A+\bar{A}) \\ &= A+B \end{aligned}$$

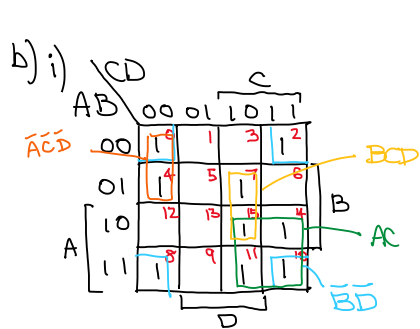ii)  $H(A,B,C) = A\bar{B} + AB\bar{C} + \bar{A}B$

$$\begin{aligned} &= A \oplus B + AB\bar{C} \\ &= A \oplus B \oplus AB\bar{C} + (A \oplus B)(AB\bar{C}) \\ &= A \oplus B \oplus AB\bar{C} + (\bar{A}\bar{B} + AB)(AB\bar{C}) \\ &= A \oplus B \oplus AB\bar{C} \end{aligned}$$





$$\begin{aligned} G &= \Pi M(1, 3, 5, 6, 9, 12, 13) \\ &= \Sigma m(0, 2, 4, 7, 8, 10, 11, 14, 15) \end{aligned}$$

$$\begin{aligned} &= \bar{A}\bar{B}\bar{C}\bar{D} + \bar{A}\bar{B}C\bar{D} + \bar{A}B\bar{C}\bar{D} + \bar{A}BCD + A\bar{B}\bar{C}\bar{D} + A\bar{B}C\bar{D} + A\bar{B}C\bar{D} + ABCD \\ &\quad + A\bar{B}C\bar{D} + \bar{A}\bar{B}C\bar{D} + ABCD \end{aligned}$$

$$\begin{aligned} &= \bar{B}\bar{D}(\bar{A}\bar{C} + \bar{A}C + A\bar{C} + AC) + AC(\bar{B}D + B\bar{D} + B\bar{D} + \bar{B}D) + \bar{A}\bar{C}\bar{D}(B + \bar{B}) + BCD(\bar{A} + A) \\ &= \bar{B}\bar{D} + AC + \bar{A}\bar{C}\bar{D} + BCD \end{aligned}$$

ii)

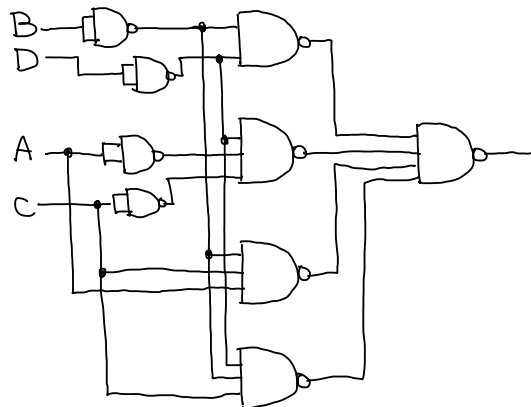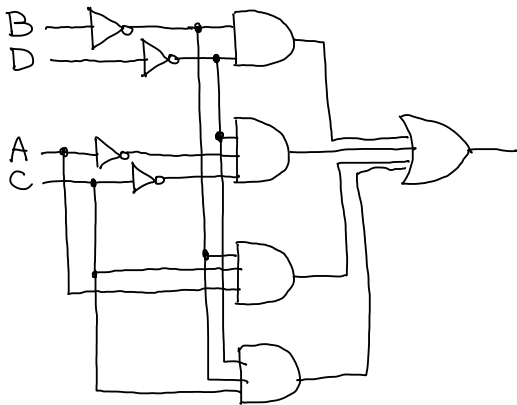

NAND only

9) i)


A	B	C	D	Z
0	0	0	0	1
0	0	0	1	0
0	0	1	0	1
0	0	1	1	0
0	1	0	0	1
0	1	0	1	0
0	1	1	0	1
0	1	1	1	0
1	0	0	0	1
1	0	0	1	1
1	0	1	0	1
1	0	1	1	1
1	1	0	0	0
1	1	0	1	0
1	1	1	0	0
1	1	1	1	0

$Z = \bar{D}$

$Z = \bar{D}$

$Z = 1$

$Z = 0$

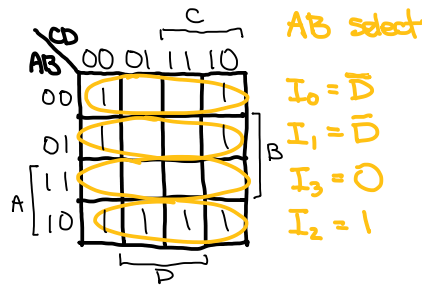

CD select

$$I_0 = \bar{A} + \bar{B}$$

$$I_1 = A\bar{B}$$


$$I_2 = \bar{A} + B$$

$$I_3 = A\bar{B}$$

Note: Using CD as select would not give the simplest design.



ii)  $Z = \sum m(0, 2, 4, 6, 8, 9, 10, 11)$

iii)

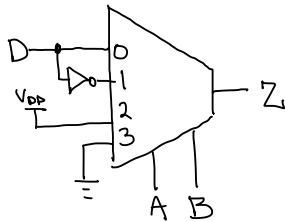


d)


Not required!

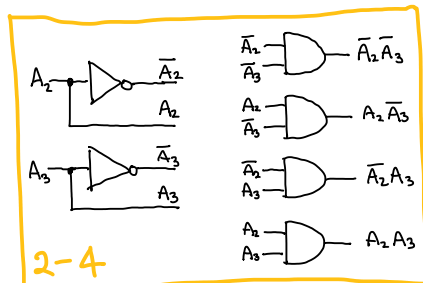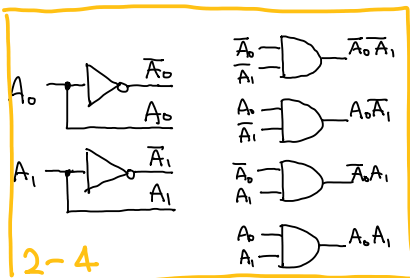
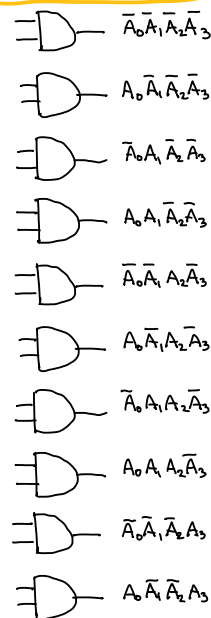
$$GIC = 4 + 4 \times 2 + 4 \times 2 + 11 \times 2 = 42$$



Block diagram

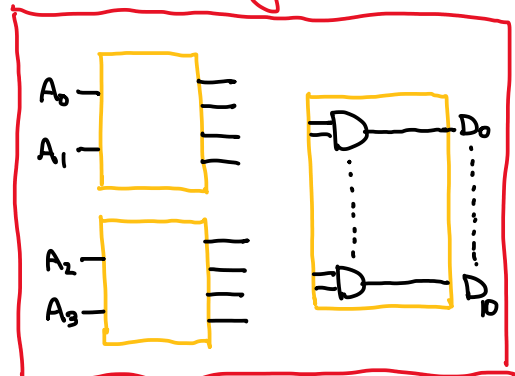

Refer to Week 3 slide 51

- Input n is even,  $n=4$ .

Use  $2^n$  AND gates driven by two decoders of output size  $2^{n/2} = 4$

Since BCD is only from 0 to X, 16-X-1 AND gates will be redundant.