


Question 1 A

Saturday, 7 March 2020 6:20 pm

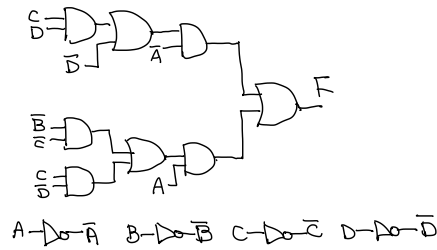
a) i) Literals = 9
Terms = 7
Complements = 4
GIC = 20

$$\rightarrow \overline{A}(CD + \overline{D}) + A(\overline{B}\overline{C} + C\overline{D})$$

Students may draw logic diagram to determine the GIC.



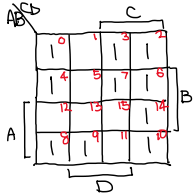ii) Students can use the K-map to find the minterms for F or use algebraic expansion




OR

$$\begin{aligned} F &= \overline{A}(CD + \overline{D}) + A(\overline{B}\overline{C} + C\overline{D}) \\ &= \overline{A}CD + \overline{A}\overline{D} + A\overline{B}\overline{C} + AC\overline{D} \\ &= \overline{A}CD(B + \overline{B}) + \overline{A}\overline{D}(B + \overline{B})(C + \overline{C}) + A\overline{B}\overline{C}(D + \overline{D}) + AC\overline{D}(B + \overline{B}) \end{aligned}$$

$$F = \sum m(0, 2, 3, 4, 6, 7, 8, 9, 10, 14)$$

iii)


A	B	C	D	F	m_i
0	0	0	0	1	m_0
0	0	0	1	0	m_1
0	0	1	0	1	m_2
0	0	1	1	1	m_3
0	1	0	0	1	m_4
0	1	0	1	0	m_5
0	1	1	0	1	m_6
0	1	1	1	1	m_7
1	0	0	0	1	m_8
1	0	0	1	1	m_9
1	0	1	0	1	m_{10}
1	0	1	1	0	m_{11}
1	1	0	0	0	m_{12}
1	1	0	1	0	m_{13}
1	1	1	0	1	m_{14}
1	1	1	1	0	m_{15}

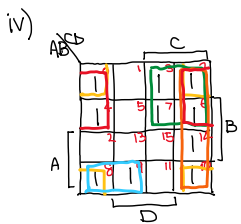

$$F = \overline{A}\overline{D} + \overline{A}C + C\overline{D} + A\overline{B}\overline{C} \quad \leftarrow \text{SOP}$$

$$\text{PI: } \overline{B}\overline{D}, \overline{A}\overline{D}, \overline{A}C, C\overline{D}, A\overline{B}\overline{C}$$
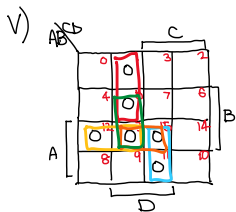
$$\text{EPI: } \overline{A}\overline{D}, \overline{A}C, C\overline{D}, A\overline{B}\overline{C}$$



$$F = (A + C + \overline{D})(\overline{A} + \overline{B} + C)(\overline{A} + \overline{C} + \overline{D}) \quad \leftarrow \text{POS}$$


$$\text{PI} = (\overline{A} + C + \overline{D}), (\overline{B} + C + \overline{D}), (\overline{A} + \overline{B} + C),$$

$$\text{EPI} = (A + C + \overline{D}), (\overline{A} + \overline{B} + C), (\overline{A} + \overline{C} + \overline{D})$$

vi) Literals = 9
Terms = 4
Complements = 4
GIC = 17

Reduction of 3 GIC after optimisation

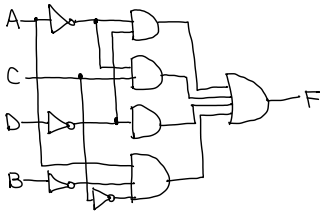vii) $F = \bar{A}\bar{B} + \bar{A}C + C\bar{D}, \bar{A}\bar{B}C$



b) binary hexadecimal octal
110101100111 1AC.E 65A.7


Octal \rightarrow Binary

6 5 4 . 7
 (110101100.111)₂ \leftarrow Binary

Binary \rightarrow Hexadecimal

000 110101100 . 1110
 10 12 14
 A C E
 (1 A C . E)₁₆ \leftarrow Hex

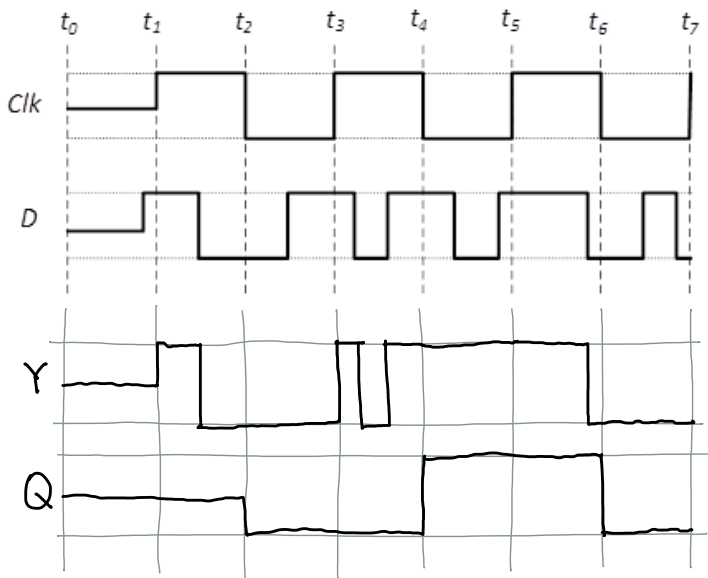c) A - D latch
 B - Positive edge triggered D-flip flop



Question 2 A

Saturday, 7 March 2020 8:31 pm


a) i) $X + Y = X \oplus Y + XY$

$$\begin{aligned} X \oplus Y + XY &= X\bar{Y} + \bar{X}Y + XY \\ &= X\bar{Y} + XY + XY + \bar{X}Y \\ &= X(\bar{Y} + Y) + Y(X + \bar{X}) \\ &= X + Y \end{aligned}$$

ii) $H(A, B, C) = A\bar{B} + AB\bar{C} + \bar{A}B$

$$\begin{aligned} &= A\bar{B} + AB\bar{C} \\ &= A\bar{B} \oplus AB\bar{C} + (A\bar{B})(AB\bar{C}) \\ &= A\bar{B} \oplus AB\bar{C} + (\bar{A}\bar{B})(AB\bar{C}) \\ &= A\bar{B} \oplus AB\bar{C} \end{aligned}$$

$$X + Y = X \oplus Y + XY$$


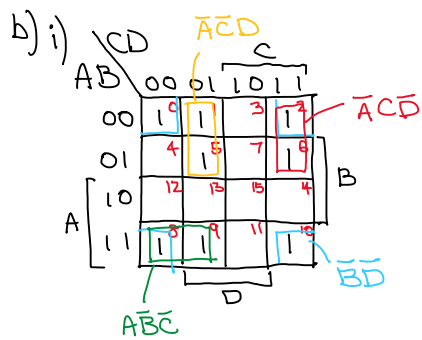


$$G = \sum m(3, 4, 7, 11, 12, 13, 14, 15)$$

$$= \sum (0, 1, 2, 5, 6, 8, 9, 10)$$

$$\begin{aligned} &= \bar{A}\bar{B}\bar{C}\bar{D} + \bar{A}\bar{B}\bar{C}D + \bar{A}\bar{B}C\bar{D} + \bar{A}\bar{B}CD + \bar{A}B\bar{C}\bar{D} + \bar{A}B\bar{C}D + \bar{A}B\bar{C}\bar{D} + \bar{A}B\bar{C}D \\ &+ \bar{A}B\bar{C}\bar{D} + \bar{A}B\bar{C}D \\ &= \bar{B}\bar{D}(\bar{A}\bar{C} + \bar{A}C + A\bar{C} + AC) + \bar{A}\bar{C}\bar{D}(\bar{B} + B) + \bar{A}\bar{C}D(\bar{B} + B) + \bar{A}C\bar{D}(\bar{B} + B) \\ &= \bar{B}\bar{D} + \bar{A}\bar{C}\bar{D} + \bar{A}B\bar{C}\bar{D} + \bar{A}C\bar{D} \end{aligned}$$

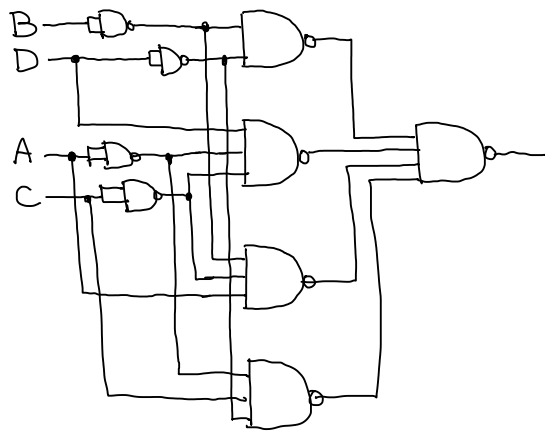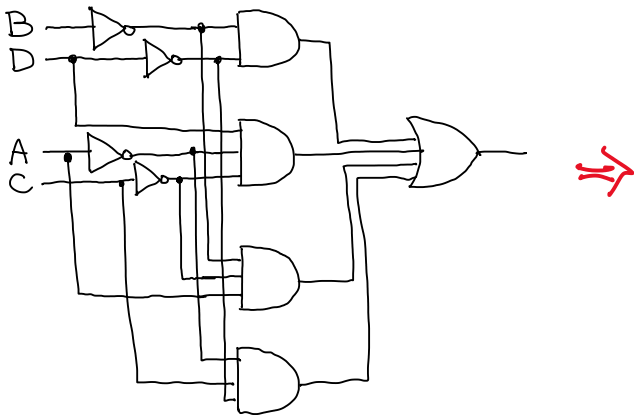ii) $G = \bar{B}\bar{D} + \bar{A}\bar{C}\bar{D} + \bar{A}B\bar{C}\bar{D} + \bar{A}C\bar{D}$



c) i)


A	B	C	D	Z
0	0	0	0	0
0	0	0	1	1
0	0	1	0	0
0	0	1	1	1
0	1	0	0	0
0	1	0	1	1
0	1	1	0	0
0	1	1	1	1
1	0	0	0	0
1	0	0	1	0
1	0	1	0	1
1	0	1	1	1
1	1	0	0	1
1	1	0	1	1
1	1	1	0	0
1	1	1	1	0

$Z = D$

$Z = D$

$Z = C$

$Z = \bar{C}$

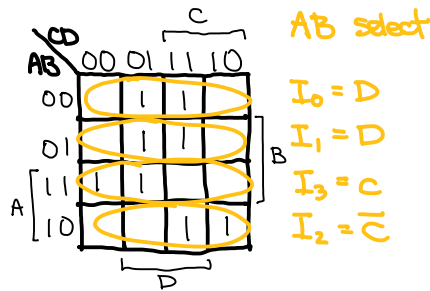

CD select

$I_0 = AB$

$I_1 = \bar{A} + B$


$I_2 = A\bar{B}$

$I_3 = \bar{A} + \bar{B}$



Note: Using CD as select would not give the simplest design.

ii) $Z = \sum m(1, 3, 5, 7, 10, 11, 12, 13)$


iii)

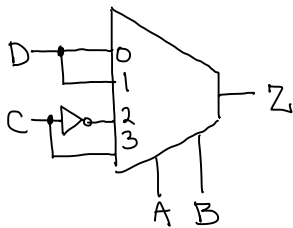

d) Not required!

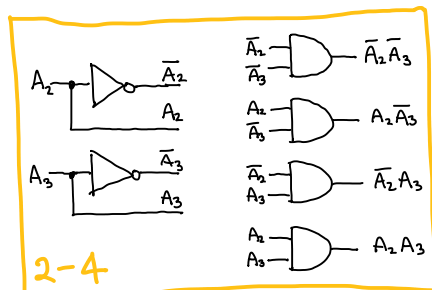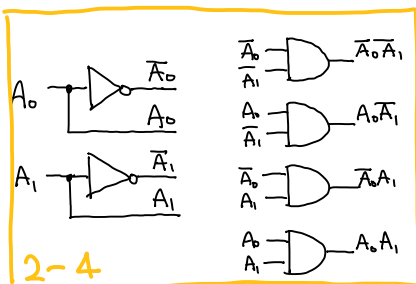


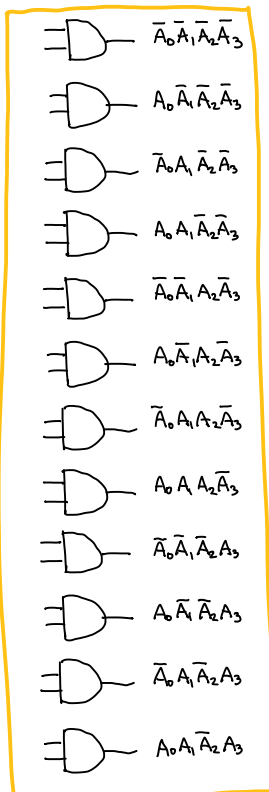GIC = $4 + 4 \times 2 + 4 \times 2 + 12 \times 2$
 $= 44$



12 AND gates

Block diagram

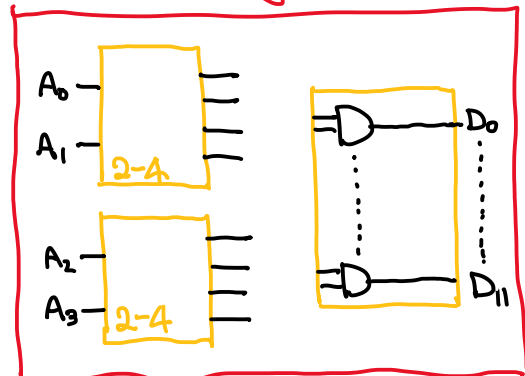

Refer to Week 3 slide 51

- Input n is even, $n = 4$.

Use 2^n AND gates driven by two decoders of output size $2^{n/2} = 4$

Since BCD is only from 0 to X, $16 - X - 1$ AND gates will be redundant.