

# MIDTERM EXAM T1 2019 SOLUTION

$$1a) F(A, B, C, D) = \underbrace{\bar{C}D}_1 + \underbrace{AB\bar{C}}_1 + \underbrace{AB\bar{D}}_1 + \underbrace{\bar{A}BD}_1 \rightarrow \text{terms}$$

$$(1) GIC = 11 (\text{literals}) + 4 (\text{terms}) + 4 (\text{complements})$$

= 19      (1)      (1)      (1)

(H) Can be done algebraically or with truth table

Algebraic Method

$$\bar{C}D = \bar{C}D(A + \bar{A})(B + \bar{B}) = \bar{C}D(AB + \bar{A}B + A\bar{B} + \bar{A}\bar{B})$$

$$= \bar{A}\bar{B}\bar{C}D + \bar{A}B\bar{C}D + A\bar{B}\bar{C}D + \bar{A}\bar{B}\bar{C}D$$

1                      5                      9                      1                      (minterms)

$$AB\bar{C}(D + \bar{D}) = AB\bar{C}D + AB\bar{C}\bar{D}$$

13                      12

(2)

$$AB\bar{D}(C + \bar{C}) = ABC\bar{D} + AB\bar{C}\bar{D} \Rightarrow F = \sum m(1, 3, 5, 9, 12, 13, 14)$$

14                      12

$$\bar{A}BD(C + \bar{C}) = \bar{A}BCD + \bar{A}\bar{B}CD$$

3                      1

Truth table

A	B	C	D	$\bar{C}D$	$AB\bar{C}$	$AB\bar{D}$	$\bar{A}BD$	F
0	0	0	0	0	0	0	0	0
0	0	0	1	1	0	0	1	1
0	0	1	0	0	0	0	0	0
0	0	1	1	0	0	0	1	1
0	1	0	0	0	0	0	0	0
0	1	0	1	1	0	0	0	1
0	1	1	0	0	0	0	0	0
0	1	1	1	0	0	0	0	0
1	0	0	0	0	0	0	0	0
1	0	0	1	1	0	0	0	1
1	0	1	0	0	0	0	0	0
1	0	1	1	0	0	0	0	0
1	1	0	0	0	1	1	0	1
1	1	0	1	1	1	0	0	1
1	1	1	0	0	0	1	0	1
1	1	1	1	0	0	0	0	0

(2) - Method

(iii)

AB \ CD	00	01	11	10
00		1	1	0
01		1		0
11	1	1		1
10		1		

most will have 0's in empty spaces here

OR

(2)

CD \ AB	00	01	11	10
00			1	
01		1	1	1
11		1		
10			1	

Prime implicants:  $\bar{C}D$ ,  $AB\bar{D}$ ,  $AB\bar{C}$ ,  $\bar{A}\bar{B}D$  (3)

Essential PIs:  $\bar{C}D$ ,  $AB\bar{D}$ ,  $\bar{A}\bar{B}D$  (1, 5)

$$F = \bar{C}D + AB\bar{D} + \bar{A}\bar{B}D \quad (1.5)$$

(iv)

AB \ CD	00	01	11	10
00	0			0
01	0		0	0
11			0	
10	0		0	0

OR

CD \ AB	00	01	11	10
00	0	0		0
01			0	0
11		0	0	0
10	0	0		0

Prime implicants: (4)

$A+D$ ,  $B+D$ ,  $A+\bar{B}+\bar{C}$ ,  $\bar{B}+\bar{C}+\bar{D}$ ,  $\bar{A}+\bar{C}+\bar{D}$ ,  $\bar{A}+B+\bar{C}$

Essential PIs

$A+D$ ,  $B+D$  (2)

$$F = (A+D)(B+D)(\bar{B}+\bar{C}+\bar{D})(\bar{A}+\bar{C}+\bar{D})$$

OR

$$F = (A+D)(B+D)(A+\bar{B}+\bar{C})(\bar{A}+\bar{C}+\bar{D}) \quad (2)$$

OR

$$F = (A+D)(B+D)(\bar{B}+\bar{C}+\bar{D})(\bar{A}+B+\bar{C})$$

(v)

$$\text{new GIC} = 8 \text{ (literals)} + 3 \text{ (terms)} + 4 \text{ (comp.)}$$

$$= 15 \quad (1) \quad (1) \quad (1)$$

$$\text{Reduction} = 19 - 15 = 4.$$



1b)

Solution 2;

$$X = Y \Rightarrow EQ = 1; \quad X > Y \Rightarrow GT = 1$$

$$X < Y \Rightarrow LE = 1; \quad NULL = 0$$


$X_3$	$X_2$	$X_1$	$X_0$	$EQ$	$GT$	$LE$	
0	0	0	0	1	0	0	
0	0	0	1	0	0	1	$S_1, S_0$ F
0	0	1	0	0	0	1	0 0 NULL
0	0	1	1	0	0	1	0 1 LE
0	1	0	0	0	1	0	1 0 EQ (2)
0	1	0	1	1	0	0	1 1 GT
0	1	1	0	0	0	1	
0	1	1	1	0	0	1	
1	0	0	0	0	1	0	
1	0	0	1	0	1	0	
1	0	1	0	1	0	0	
1	0	1	1	0	0	1	
1	1	0	0	0	1	0	
1	1	0	1	0	1	0	
1	1	1	0	0	1	0	
1	1	1	1	1	0	0	

$$EQ = \sum m(0, 5, 10, 15)$$

$$GT = \sum m(4, 8, 9, 12, 13, 14)$$

$$LE = \sum m(1, 2, 3, 6, 7, 11)$$

(6)

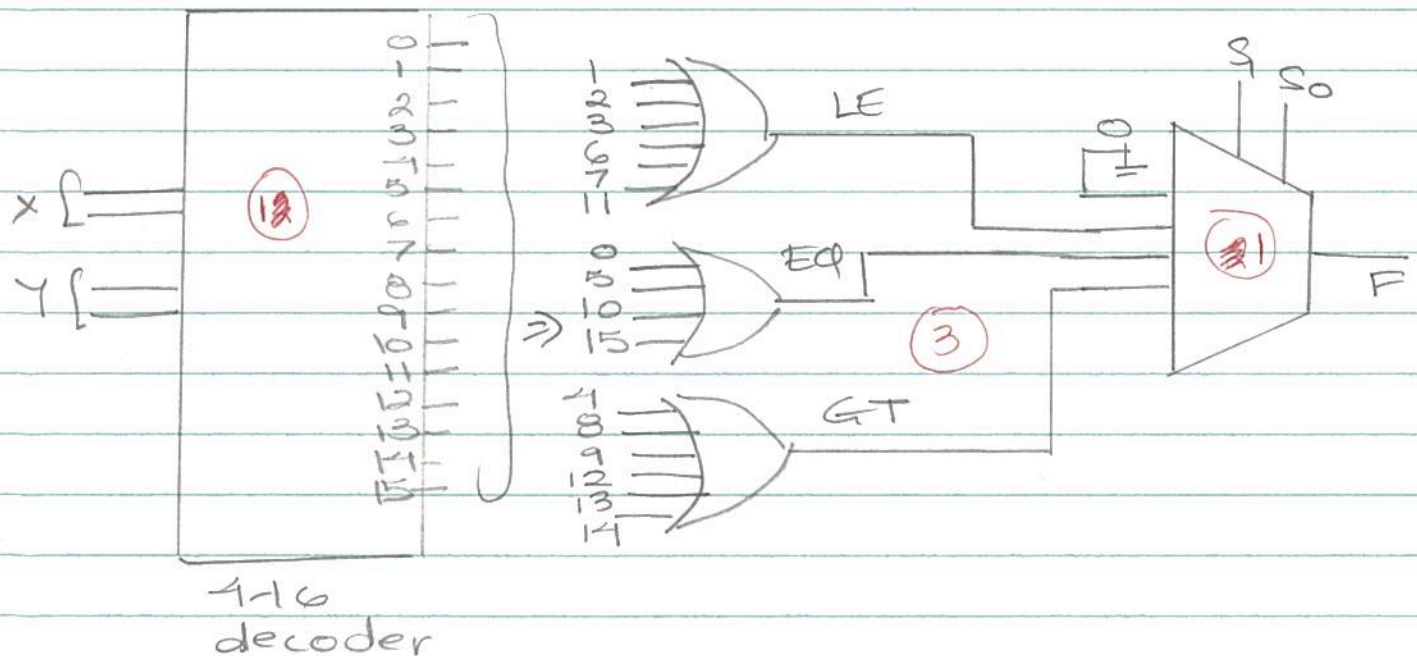


## 1b) 2-bit comparator


Solution 1:

$$X = Y \Rightarrow EQ = 1 ; X > Y \Rightarrow GT = 1$$

$$X < Y \Rightarrow LE = 1 ; X - Y = 0 \Rightarrow NULL = 1$$

$X_1, X_0$	$Y_1, Y_0$	$EQ$	$GT$	$LE$	$NULL$	
0 0	0 0	0	0	0	1	
0 0	0 1	0	0	1	0	
0 0	1 0	0	0	1	0	(2)
0 0	1 1	0	0	1	0	
0 1	0 0	0	1	0	0	$S_1, S_0, F$
0 1	0 1	1	0	0	0	0 0 NULL
0 1	1 0	0	0	1	0	0 1 LE
0 1	1 1	0	0	1	0	1 0 EQ
1 0	0 0	0	1	0	0	1 1 GT
1 0	0 1	0	1	0	0	(2)
1 0	1 0	1	0	0	0	$NULL = \sum m(1)$
1 0	1 1	0	0	1	0	$EQ = \sum m(5, 10, 15)$
1 1	0 0	0	1	0	0	$GT = \sum m(4, 8, 9,$
1 1	0 1	0	1	0	0	$12, 13, 14)$
1 1	1 0	0	1	0	0	$LE = \sum m(1, 2, 3,$
1 1	1 1	1	0	0	0	$6, 7, 11)$

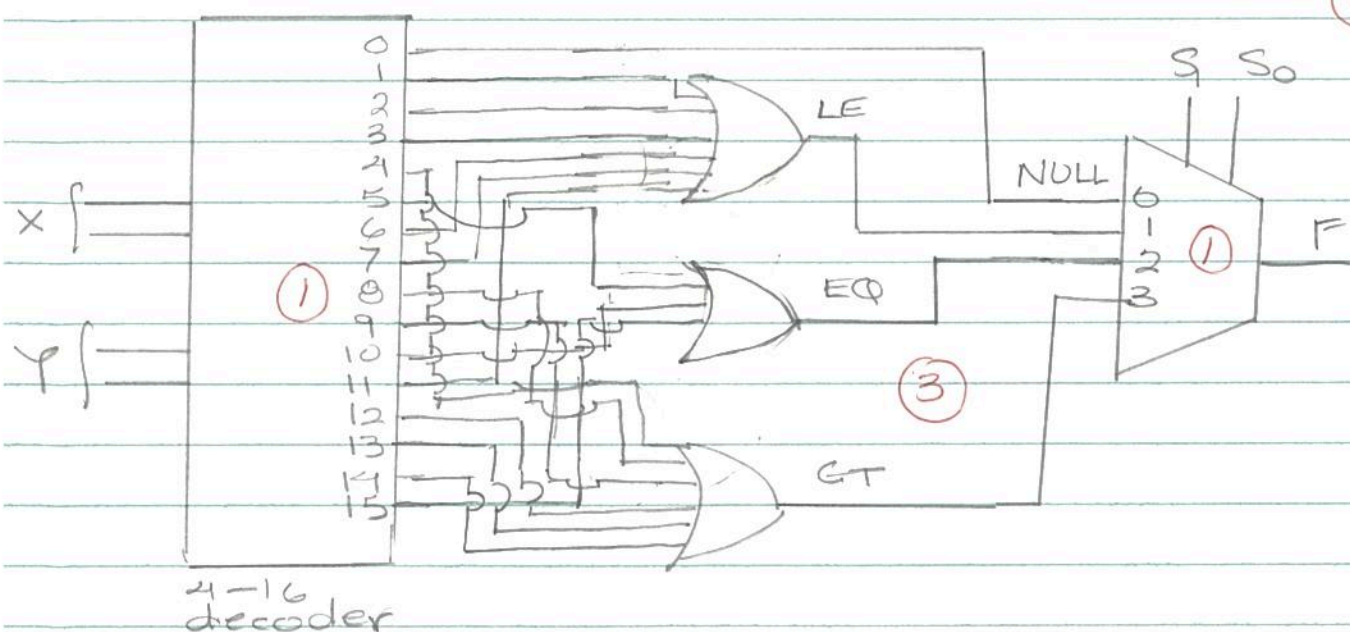

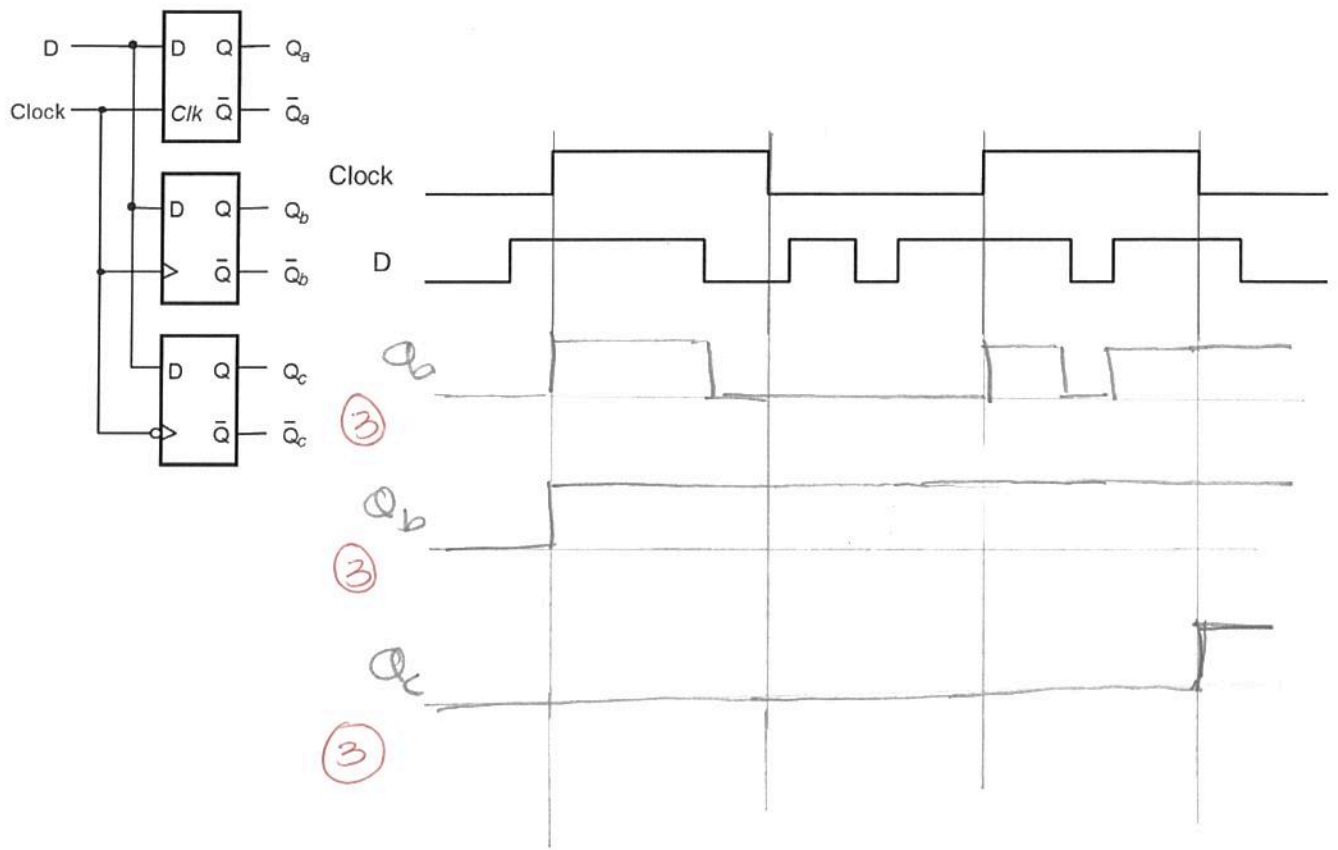



2a)

$453.25_8 \rightarrow \text{base } 10$  (1)

$$4 \times 8^2 + 5 \times 8^1 + 3 \times 8^0 + 2 \times 8^{-1} + 5 \times 8^{-2}$$

$$(5) = 299.3281_{10}$$

base 10  $\rightarrow$  base 7

7	299		$0.3281 \times 7 = 2.2967$	2
	42	5	$0.2967 \times 7 = 2.0769$	2
	6	0	$0.0769 \times 7 = 0.5383$	0
			$0.5383 \times 7 = 3.7681$	3

(5)

$$605.2203_7$$

$$453.25_8$$

Replacing each number with 3 bit binary

$$4 - 100, 5 - 101, 3 - 011, 2 - 010, 5 - 101$$

$$\Rightarrow \overbrace{100}^4 \overbrace{101}^5 \overbrace{011}^3 . \overbrace{010}^2 \overbrace{101}^5$$

(5)

b)

(i) From left side - moving right

AND gate:  $W\bar{X}Z$

OR gates:  $Y + W\bar{X}Z$  and  $W + X$

AND gate:  $(W + X)(Y + W\bar{X}Z)$

OR gate:  $F = \bar{Z} + (W + X)(Y + W\bar{X}Z)$

(4)

(ii)

$$F = \bar{Z} + [(W + X)(Y + W\bar{X}Z)]$$

$$= \bar{Z} + [WY + XY + WW\bar{X}Z + XW\bar{X}Z]$$

$$= \bar{Z} + WY + XY + W\bar{X}Z$$

$$= WY + XY + (\bar{Z} + W\bar{X}Z)$$

$$= Y(W + X) + \bar{Z} + W\bar{X}$$

$$= XY + \bar{X}W + \bar{Z}$$

consensus:  $XY + \bar{X}W + YW = XY + \bar{X}W$



$WW = 1$
$X\bar{X} = 0$

(7)

$$A + \bar{A}B = A + B$$

Q1

2b

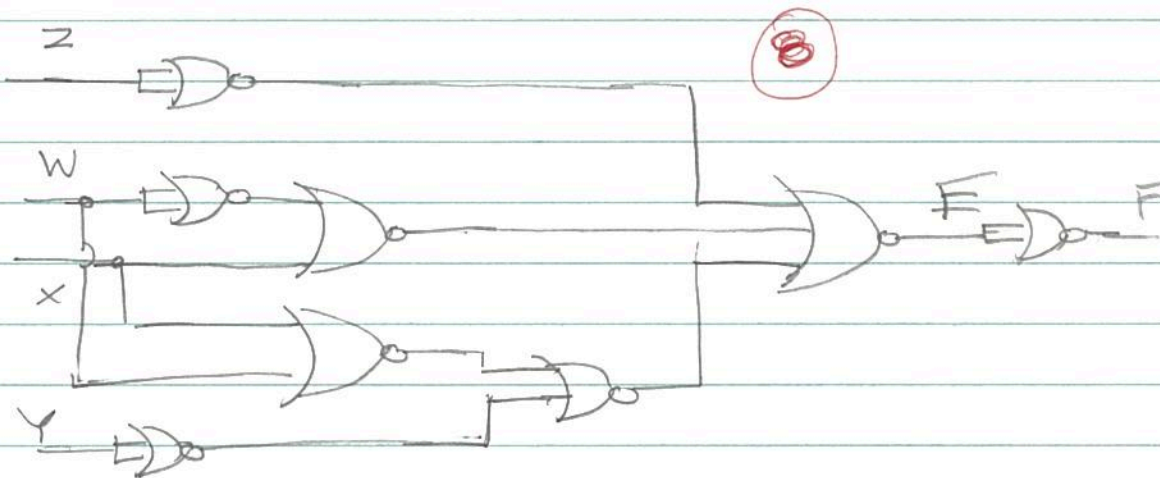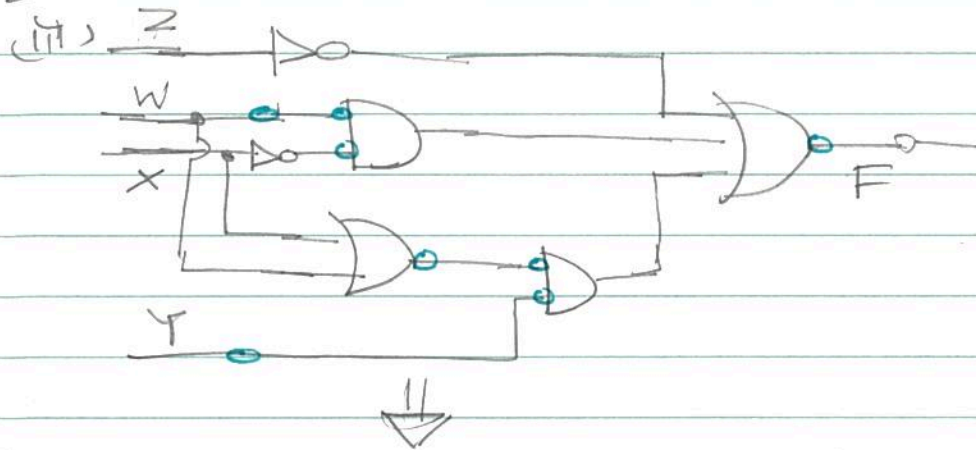

2c

Truth table

A	B	BR	D	BL	BL = $\sum m(1, 2, 3, 7)$
0	0	0	0	0	$D = \sum m(1, 2, 4, 7)$
0	0	1	1	1	$= \bar{A}\bar{B}BR + \bar{A}B\bar{B}R$
0	1	0	1	1	$+ \bar{A}B\bar{B}R + AB\bar{B}R$
0	1	1	0	1	$= BR(\bar{A}\bar{B} + AB)$
1	0	0	1	0	$+ \bar{B}R(\bar{A}\bar{B} + AB)$
1	0	1	0	0	$\bar{A}B + A\bar{B} = A \oplus B$
1	1	0	0	0	$\bar{A}\bar{B} + AB = \overline{A \oplus B}$
1	1	1	1	1	$\Rightarrow D = BR(\overline{A \oplus B}) + \bar{B}R(A \oplus B)$
					$= BR \oplus A \oplus B$ (2)

$$\begin{aligned}
 BL &= \bar{A}\bar{B}BR + \bar{A}B\bar{B}R + \bar{A}B\bar{B}R + AB\bar{B}R \\
 &= (\bar{A}\bar{B} + AB)BR + \bar{A}B(\bar{B}R + BR) \\
 &= (\overline{A \oplus B})BR + \bar{A}B = 1, \bar{B}R + BR = 1
 \end{aligned}$$




2c)


To get rid of OR need to do double complement

$$BL = \overline{(\overline{A+B})BR + \overline{AB}} = \overline{(\overline{A+B})BR} \overline{(\overline{AB})}$$


(3)

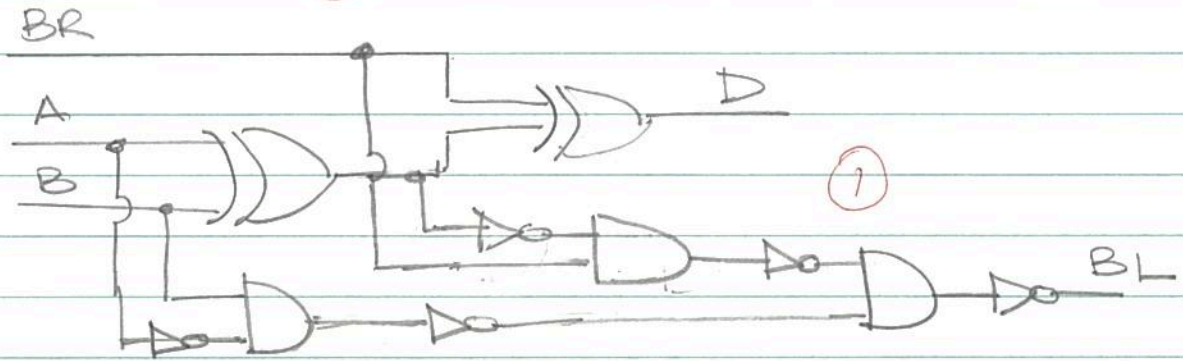

If OR gate kept - circuit will be

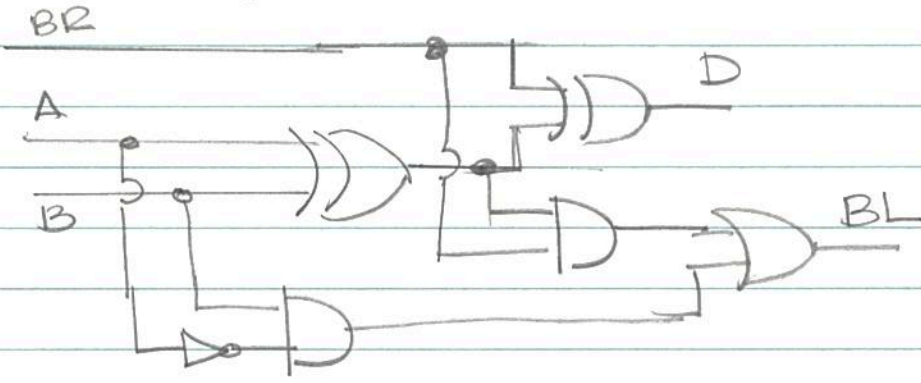

(II)

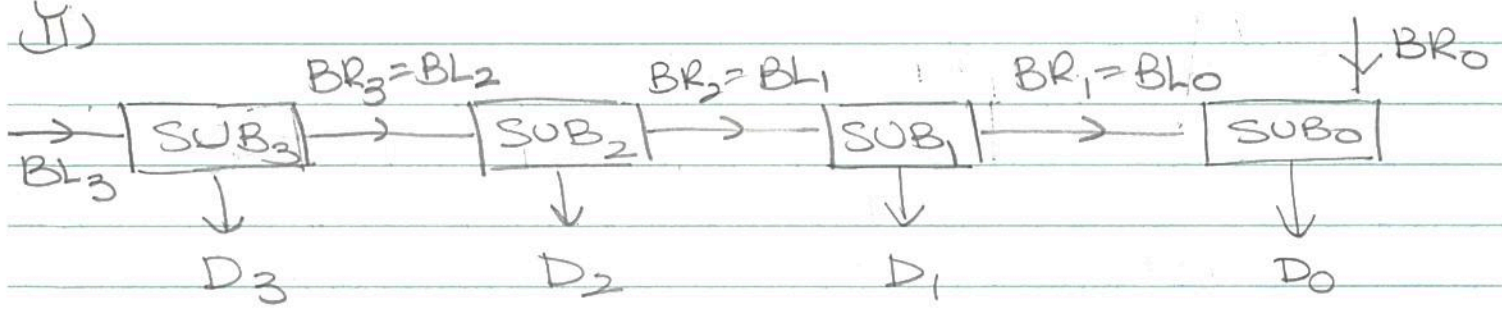

(5)