

1. Convert the numbers in the table below from the given base to the other bases.

Converting $3D5.E_{16}$ to decimal

$$3D5.E = 3 \times 16^2 + 13 \times 16 + 5 + 14 \times 16^{-1}$$

$$= 768 + 208 + 5 + 0.875$$

$$= 981.875_{10}$$

Converting 981.875_{10} to base-5

Integer part		Fraction part	
5	981	$0.875 \times 5 = 4.375$	4
	196	$0.375 \times 5 = 1.875$	1
	39	$0.875 \times 5 = 4.375$	4
	7	$0.375 \times 5 = 1.875$	1
	1		

$981.875_{10} = 12411.4141_5$

Converting $3D5.E_{16}$ to binary

3	D	5	.	E
0011	1101	0101	.	1110

$3D5.E_{16} = 1111010101.1110_2$

Converting 1111010101.1110_2 to octal

0011	1101	0101	.	1110
1	7	2	5	7

$3D5.E_{16} = 1725.7_8$

Converting 782.25_{10} to base-5

Integer		fraction	
5	782	$0.25 \times 5 = 1.25$	1
	156	$0.25 \times 5 = 1.25$	1
	31	$0.25 \times 5 = 1.25$	1
	6	$0.25 \times 5 = 1.25$	1
	1		

$782.25_{10} = 11112.1111$

Converting 782.25_{10} to hexadecimal

Integer		fraction	
16	782	$0.25 \times 16 = 4$	
	48		
	3		

$782.25_{10} = 30E.4_{16}$

Converting $30E.4_{16}$ to binary

3 0 E . 4
 0011 0000 1110 . 0100

$30E.4_{16} = 1100001110.01_2$

Converting 1100001110.01_2 to octal

001100001110 . 010
 1 4 1 6 . 4

$30E.4_{16} = 1416.4_8$

binary	decimal	base-5	hexadecimal	octal
1111010101.111	981.875	12411.4141	3D5.E	1725.7
1100001110.01	782.25	11112.1111	30E.4	1416.4

Where referenced, questions are taken from the textbook:

M. Mano, C. R. Kime and T. Martin, *Logic and Computer Design Fundamentals*, 5th Edition (Global Edition), Pearson, 2016

2. Simplify the following Boolean functions using algebraic manipulation to a minimum number of literals

i. $F(A, B, C) = A \oplus B \oplus C + \bar{A}\bar{B}\bar{C} + \bar{A}BC + A\bar{B}C + ABC$

ii. $G(A, B, C, D) = ABD + \bar{A}\bar{B}\bar{C} + \bar{A}\bar{B}C\bar{D}$

2.

(i) $F = A \oplus B \oplus C + \bar{A}\bar{B}\bar{C} + \bar{A}BC + A\bar{B}C + ABC$
 $= A \oplus B \oplus C + (\bar{A}\bar{B} + \bar{A}B)C + (A\bar{B} + AB)C$

$\bar{A}B + A\bar{B} = A \oplus B = X$
 $\overline{A \oplus B} = \overline{\bar{A}B + A\bar{B}} = \bar{A}\bar{B} + AB = \bar{X}$

$\Rightarrow F = A \oplus B \oplus C + (\bar{A \oplus B})C + (A \oplus B)C$
 $= A \oplus B \oplus C + \underbrace{\bar{X}C + XC}_{\overline{X \oplus C}}$
 $= A \oplus B \oplus C + (\overline{X \oplus C})$
 $= A \oplus B \oplus C + \overline{(A \oplus B \oplus C)}$
 $= 1$

(ii) $G = ABD + \bar{A}\bar{B}\bar{C} + \bar{A}\bar{B}C\bar{D}$
 $= ABD + \bar{A}\bar{B}(\bar{C} + C\bar{D})$

Note: $X + Y = X + \bar{X}Y$

$\Rightarrow G = ABD + \bar{A}\bar{B}(\bar{C} + \bar{D})$
 $= ABD + \bar{A}\bar{B}\bar{C} + \bar{A}\bar{B}\bar{D}$

3. Consider the following Boolean function F:

$$F(A, B, C, D) = (\bar{A} + \bar{B} + D)(\bar{A} + \bar{D}) + AC + BD$$

3.4) $F = (\bar{A} + \bar{B} + D)(\bar{A} + \bar{D}) + AC + BD$

GIC = 9 (literals) + 3 (inv) + 5 (terms)
= 17

1) Opening $\nearrow A$

$$F = \bar{A}\bar{A} + \bar{A}\bar{B} + \bar{A}D + \bar{A}\bar{D} + \bar{B}D + D\bar{D} + AC + BD$$

$$= \bar{A} + \bar{A}\bar{B} + \bar{A}D + \bar{A}\bar{D} + \bar{B}D + AC + BD$$

\bar{A} will include all minterms with \bar{A}

$$\bar{A} = \bar{A}\bar{B}\bar{C}\bar{D} + \bar{A}\bar{B}C\bar{D} + \bar{A}B\bar{C}\bar{D} + \bar{A}BC\bar{D}$$

$$+ \bar{A}\bar{B}CD + \bar{A}B\bar{C}D + \bar{A}BCD + \bar{A}\bar{B}CD$$

$\bar{A}\bar{B}, \bar{A}D, \bar{A}\bar{D}$ will be give minterms include in those obtained \bar{A} (0-7)

$AC = AC(B + \bar{B})(D + \bar{D})$

$$= AC(BD + \bar{B}D + B\bar{D} + \bar{B}\bar{D})$$

$$= ABCD + \bar{A}\bar{B}CD + A\bar{B}C\bar{D} + \bar{A}B\bar{C}\bar{D}$$

$BD = BD(A + \bar{A})(C + \bar{C})$

$$= BD(AC + \bar{A}C + A\bar{C} + \bar{A}\bar{C})$$

$$= ABCD + \bar{A}BCD + A\bar{B}C\bar{D} + \bar{A}\bar{B}C\bar{D}$$

$\bar{B}\bar{D} = \bar{B}\bar{D}(A + \bar{A})(C + \bar{C})$

$$= \bar{B}\bar{D}(AC + \bar{A}C + A\bar{C} + \bar{A}\bar{C})$$

$$= \bar{A}\bar{B}C\bar{D} + \bar{A}\bar{B}C\bar{D} + A\bar{B}C\bar{D} + \bar{A}\bar{B}C\bar{D}$$


$$F = \sum m(0, 1, 2, 3, 4, 5, 6, 7, 8, 10, 11, 13, 14, 15)$$

Where referenced, questions are taken from the textbook:

M. Mano, C. R. Kime and T. Martin, Logic and Computer Design Fundamentals, 5th Edition (Global Edition), Pearson, 2016

(M)

Simplifying using a K-map

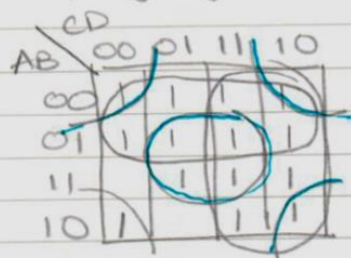

All prime implicants
are essential

$$\bar{A}, C, BD, \bar{B}\bar{D}$$

$$F = \bar{A} + C + BD + \bar{B}\bar{D}$$

(IV)



$$F = (\bar{A} + \bar{B} + C + D)(\bar{A} + B + C + \bar{D})$$

OR

$$F = \overline{AB\bar{C}\bar{D}} + \overline{A\bar{B}C\bar{D}}$$

$$= (\bar{A}\bar{B}\bar{C}\bar{D})(\bar{A}\bar{B}C\bar{D})$$


$$= (\bar{A} + \bar{B} + C + D)(\bar{A} + B + C + \bar{D})$$

$$(V) F = \bar{A} + C + BD + \bar{B}\bar{D}$$

$$GIC = 6(\text{no of literals}) + 2(\text{terms}) + 3(\text{inv})$$
$$= 11$$

$$\text{Reduction} = 17 - 11 = 6$$

(VI)

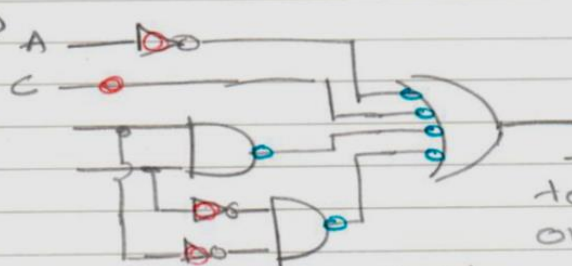


AND-OR imp

— Adding bubbles
to convert ANDs
OR to NAND

— Adding inverters where
no pairs

— Replacing inverters with NANDs too

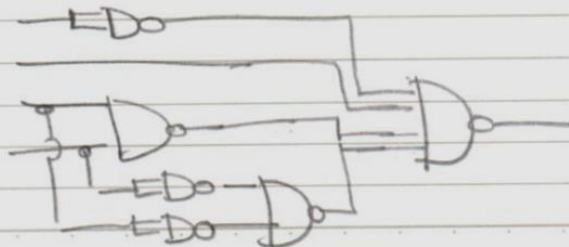

4. Design a combination circuit which can detect prime numbers from 0 to 15. There should be a single output line, which is 1 if the input is a prime number, otherwise the output line would be 0.

For numbers 0-15 will need 4 bits (A,B,C,D)
Output is single bit (Y)

$Y = 1$ when ABCD is prime
prime numbers are 2, 3, 5, 7, 11, 13

Drawing truth table

A	B	C	D	Y
0	0	0	0	0
0	0	0	1	0
0	0	1	0	1
0	0	1	1	1
0	1	0	0	0
0	1	0	1	1
0	1	1	0	0
0	1	1	1	1
1	0	0	0	0
1	0	0	1	0
1	0	1	0	0
1	0	1	1	1
1	1	0	0	0
1	1	0	1	1
1	1	1	0	0
1	1	1	1	0

$Y = C$

$Y = D$

$Y = CD$

$Y = \overline{C}D$

a)

b)

A, B are at select; C, D at input

5. Design a circuit to implement the following pair of Boolean equations, using factoring to simplify.

5. factoring both functions

$$X = ADF + AEF + BDF + BEF + CDF + CEF$$

$$= (AD + AE + BD + BE + CD + CE)F$$

$$= [(A+B+C)D + (A+B+C)E]F$$

$$= [(A+B+C)(D+E)]F$$

$$Y = A\bar{D}\bar{E} + B\bar{D}\bar{E} + C\bar{D}\bar{E}$$

$$= (A+B+C)\bar{D}\bar{E}$$

Let $T_1 = A+B+C$
 $T_2 = D+E \Rightarrow \bar{T}_2 = \bar{D}\bar{E} = \bar{DE}$

$$\Rightarrow X = T_1 T_2 F$$

$$Y = T_1 \bar{T}_2$$

Original GIC $X = 18(\text{litervols}) + 6(\text{Herms}) = 24$
 $GIC Y = 9(\text{litervols}) + 3(\text{Herms}) + 2(\text{inv}) = 14$
 Total GIC = $24 + 14 = 38$

Optimized GIC $T_1 = 3$ $T_2 = 2$ $\text{inv} = 1$
 $X = 3$ $Y = 2$
 Total GIC = $3 + 3 + 2 + 2 + 1 = 11$

GIC reduction = $38 - 11 = 27$

Where referenced, questions are taken from the textbook:

M. Mano, C. R. Kime and T. Martin, *Logic and Computer Design Fundamentals*, 5th Edition (Global Edition), Pearson, 2016

6. Implement the function below using XOR and AND gates only. Then construct the circuit using interconnecting three-state buffers and inverters.

$$H = \overline{A}\overline{B}C\overline{D} + \overline{A}B\overline{C}\overline{D} + A\overline{B}C\overline{D} + A\overline{B}C\overline{D}$$

Factoring H

$$H = \overline{A}B(C\overline{D} + \overline{C}D) + A\overline{B}(C\overline{D} + \overline{C}D)$$


$$= (\overline{A}B + A\overline{B})(C\overline{D} + \overline{C}D)$$

$$= (A \oplus B)(C \oplus D)$$


To implement using 3-state buffers, will implement each XOR separately and bring together in final 3-state buffer

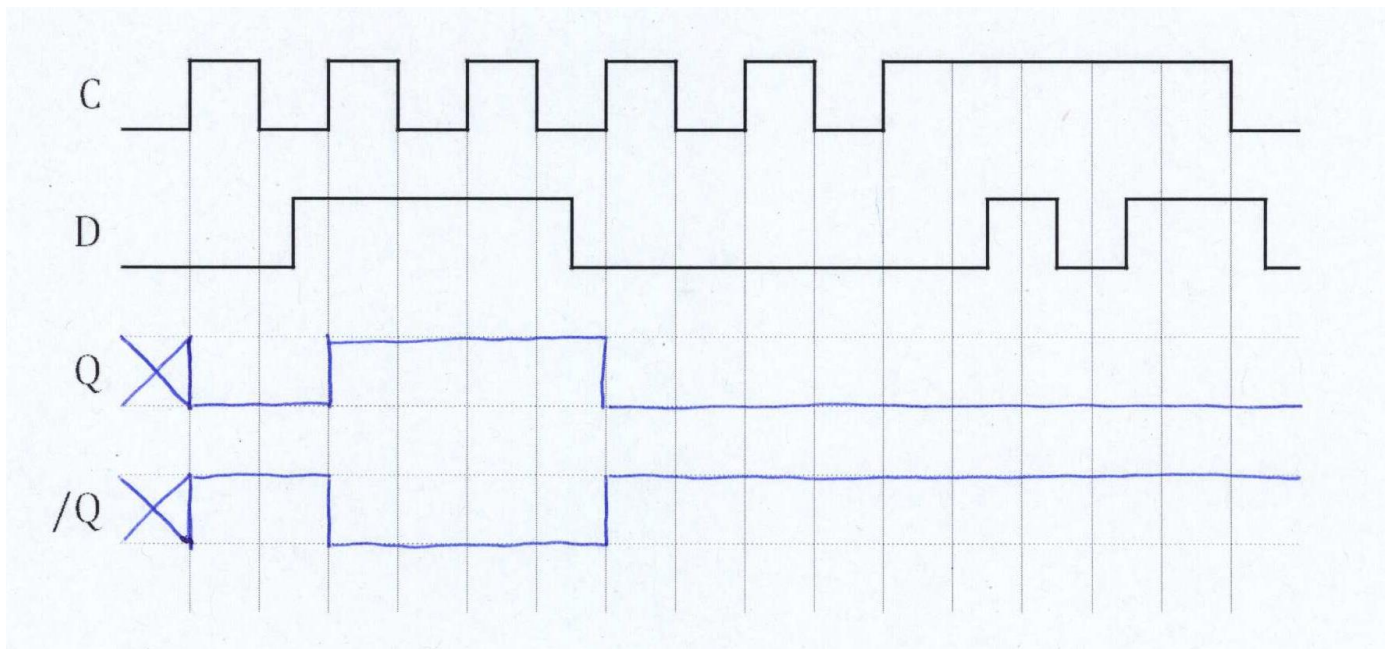7. Simulate the circuit to determine whether its functional behavior is identical to that of the D flip-flop circuit presented in lectures

Manually tracking the circuit can see that circuit behave like a D flip-flop circuit.



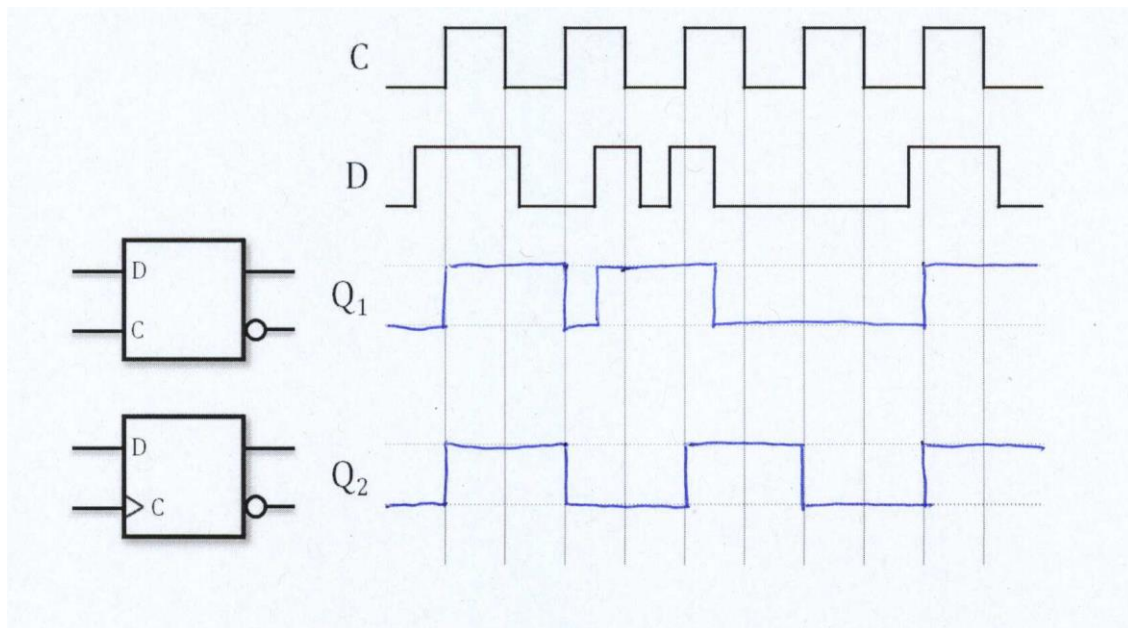8. Clock and D waveforms, one latch, and one flip-flop are shown in the figure below. For the latch and the flip-flop, carefully sketch the output waveform, Q_i , obtained in response to the input waveforms.




Where referenced, questions are taken from the textbook:

M. Mano, C. R. Kime and T. Martin, *Logic and Computer Design Fundamentals, 5th Edition (Global Edition)*, Pearson, 2016

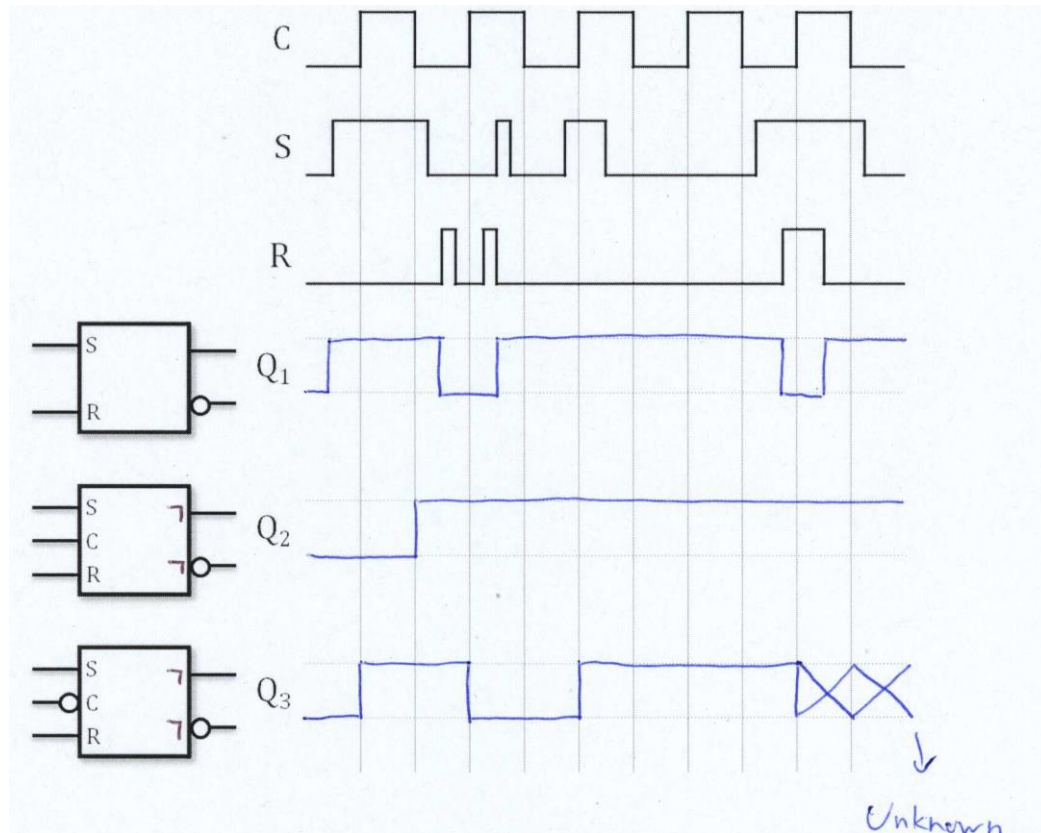
9. *Clock, S and R* waveforms, one latch and two flip-flops are shown in the figure below. For the latch and the flip-flops, carefully sketch the output waveform, Q_i , obtained in response to the input waveforms.

The last bit is unknown due to a race condition in the master slave condition. Can settle at $Q_3 = 0$ or $Q_3 = 1$



10. Draw the timing sequence of the circuit below with three T flip-flops. What is the circuit doing?

The circuit is a three bit counter

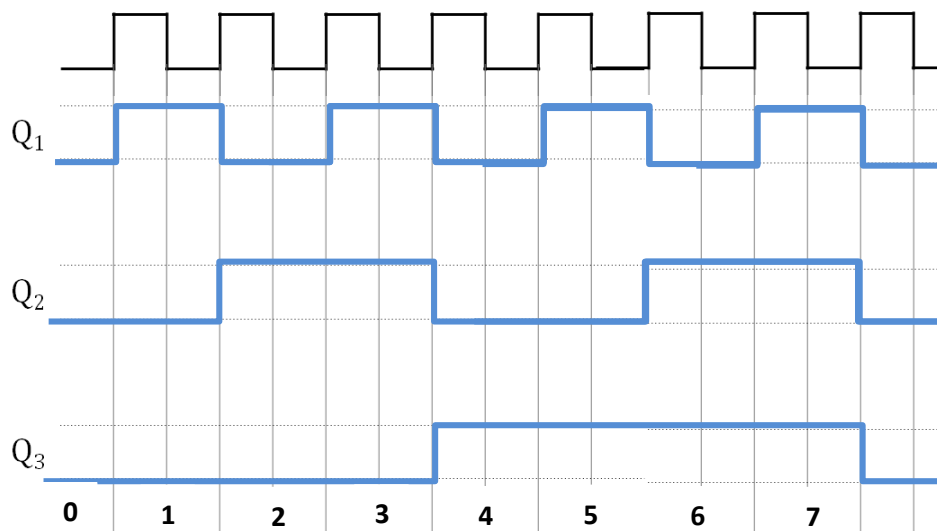

Where referenced, questions are taken from the textbook:

M. Mano, C. R. Kime and T. Martin, *Logic and Computer Design Fundamentals, 5th Edition (Global Edition)*, Pearson, 2016