

Week 10 - T1 2020

# Computer Design Fundamentals

ELEC2141: Digital Circuit Design

# Overview

Registers

Shift registers

Computer design fundamentals

Arithmetic logic units

Datapath representation

**Reading: Mano - Chapter 6, 6.1-6.6**

**Chapter 8, 8.1-8.5**

# Registers

An *n-bit register* consists of  $n$  flip-flops and is capable of storing  $n$ -bits of binary information.




The flip-flops are connected to a common clock

May also have a combinational circuit that implements state transitions of the flip-flops.

The flip-flops hold data and the combinational circuit determine the new or transformed data that will transfer to the flip-flops.

It is useful for storing and manipulating information in digital computers.

# 4-bit register

   

# Clock skew

Inserting additional logic in the clock path introduces a delay

Clock signals arrive at different flip-flops and registers at different times depending on the logic in their clock path

This is known as *clock skew*


In truly synchronous system, we must insure that all clock pulses arrive simultaneously throughout the system so that all flip-flops trigger at the same time

Therefore, control operation without clock gating is advisable
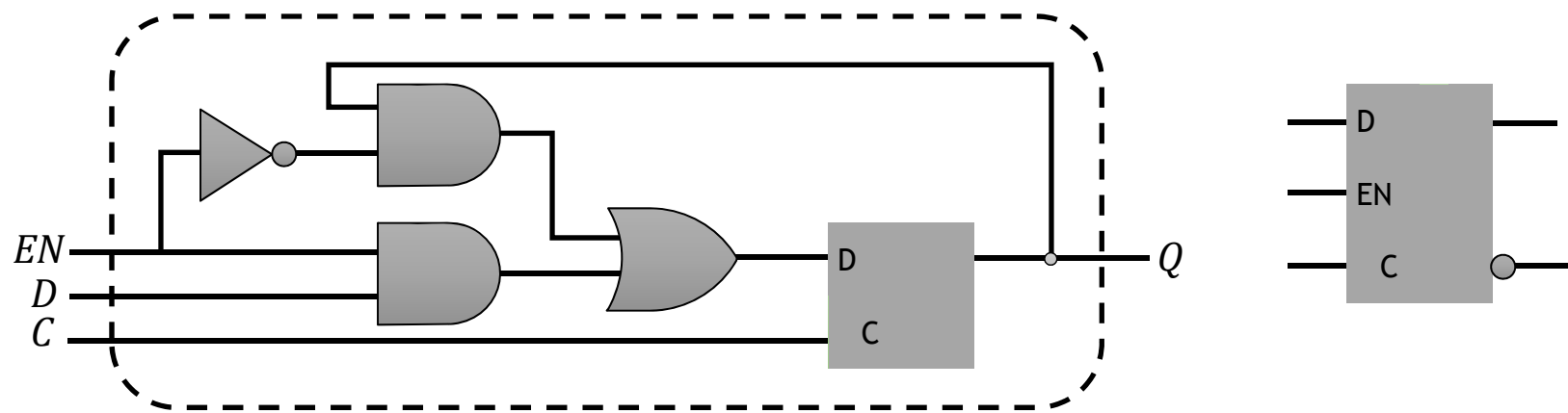
# D Flip-flops with enable

A D flip-flop with enable, with no clock gate, is a better option

It consists of a 2-to-1 multiplexer and a D flip-flop




Feedback connection necessary at D flip-flop does not have a 'no change' input condition

# 4 bit Register: D flip-flop with enable

Here the D flip-flop with enable is used as the building block for the register

A common *load* signal is connected to the EN inputs of the flip-flops

 When load is 1, data from the inputs is transferred into the register with the next positive clock edge; otherwise, the current value in the register remains the same



# Shift register

*Shift registers* are capable of moving information upon the occurrence of a clock-signal either uni-directionally or bi-directionally

Information can be entered into registers either in

Parallel: All 0/1 bits are handled simultaneously; requires as many lines as symbols being transferred

Serial: Involves the bit-by-bit transfer of information in a time sequence

Four possible ways registers can transfer information:

Serial-in/serial-out

Serial-in/parallel-out



Parallel-in/parallel-out

Parallel-in/serial-out


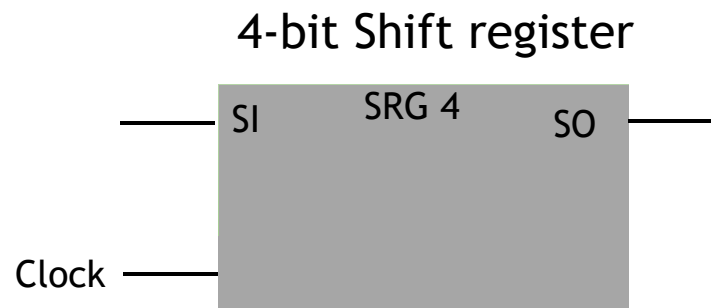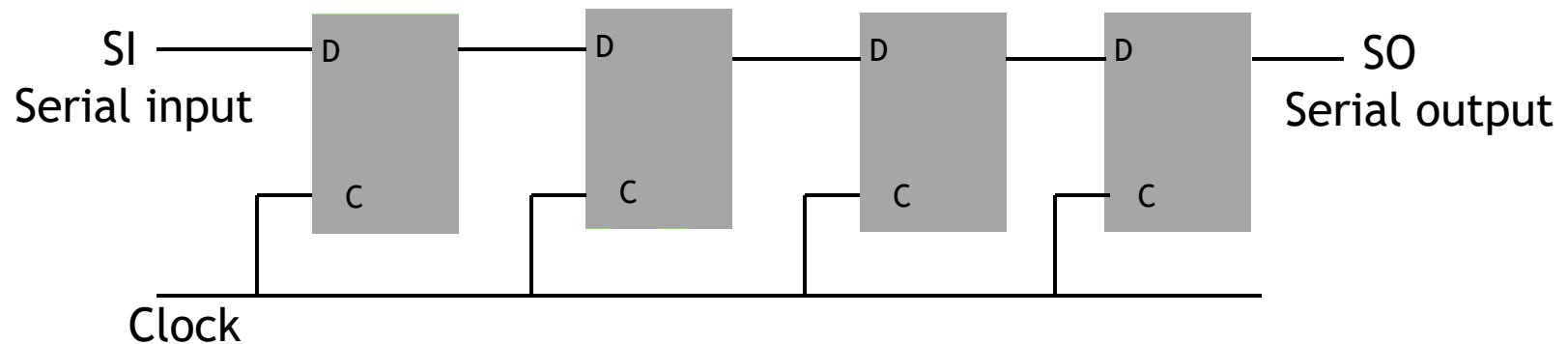
# Shift register

Simplest possible shift register is a serial in - serial out shift register




Bidirectional shift register with parallel loading provides versatile operation
 
# Shift register with parallel load

If all flip-flop outputs are accessible, output bits can be in parallel

An  $n$ -bit register can be created by interconnecting  $n$  of these units




Shift	Load	Register Operation
0	0	No change (Hold)
0	1	Parallel load
1	x	Serial input

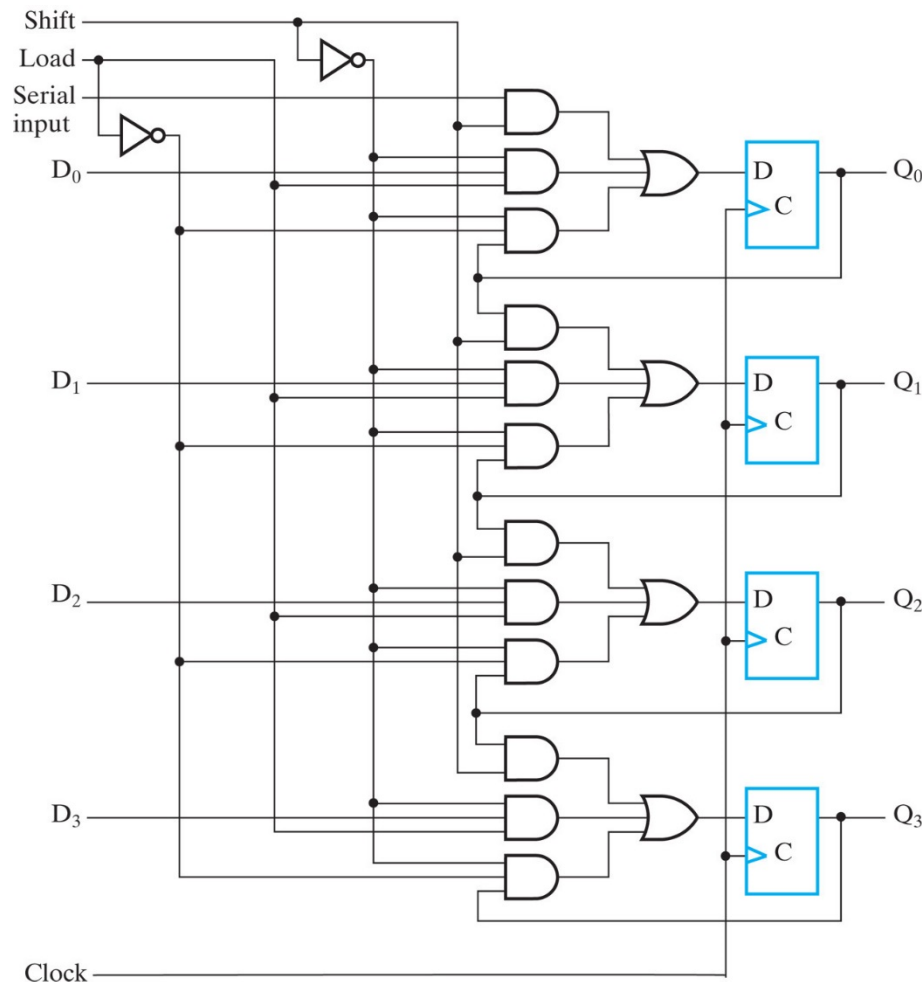
# Shift register with parallel load

Adding a parallel load, allows parallel to serial shifting and vice-versa

Shift registers are used to interface digital system far from each other




Shift	Load	Register Operation
0	0	No change (Hold)
0	1	Parallel load
1	x	Shift left ( $Q_0$ to $Q_3$ )

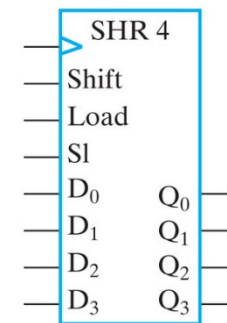

UNSW  
SYDNEY
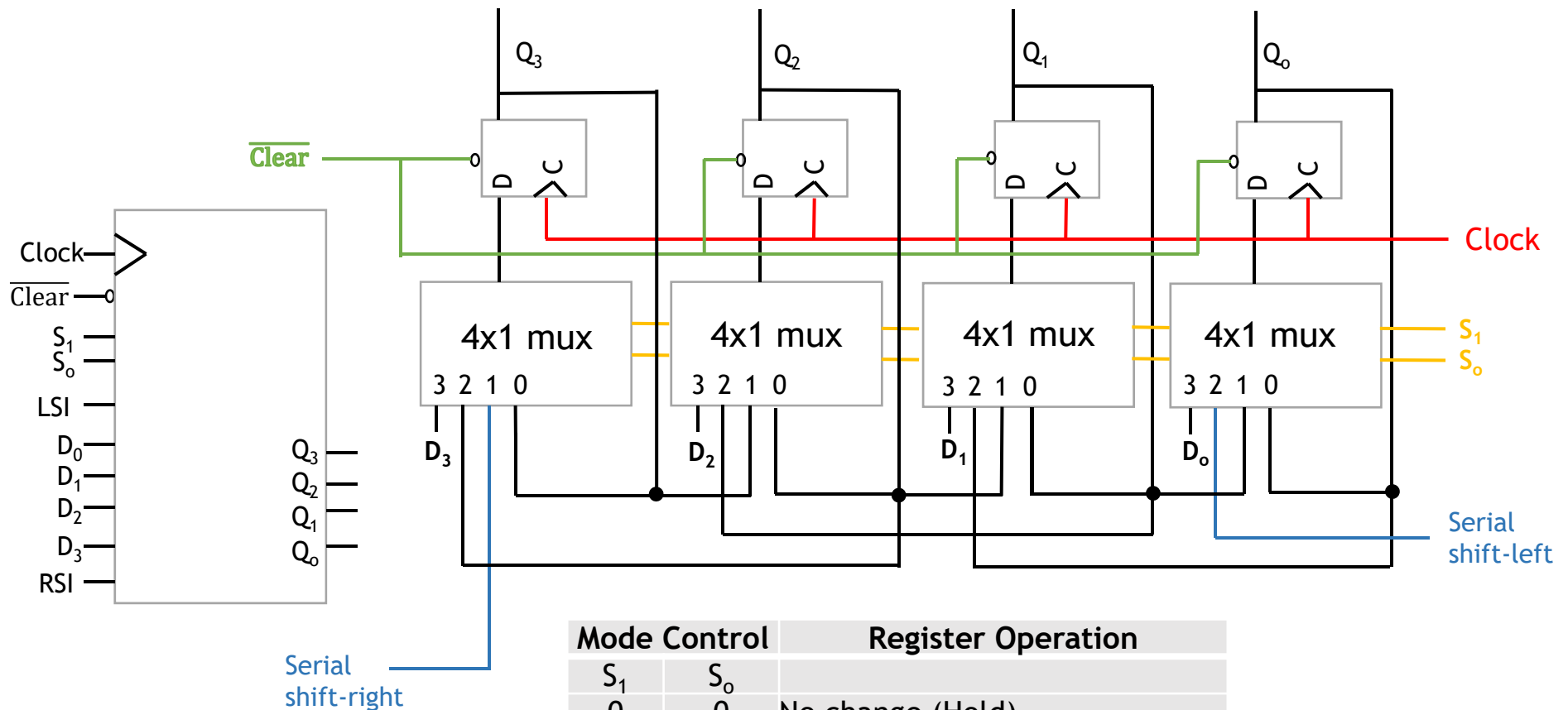
# Bidirectional shift register

A bidirectional shift register is capable of left and right serial shifts, parallel loading, and holding data




Mode Control		Register Operation
$S_1$	$S_0$	
0	0	No change (Hold)
0	1	Shift right (RSI)
1	0	Serial Shift left (LSI)
1	1	Parallel load



UNSW  
SYDNEY
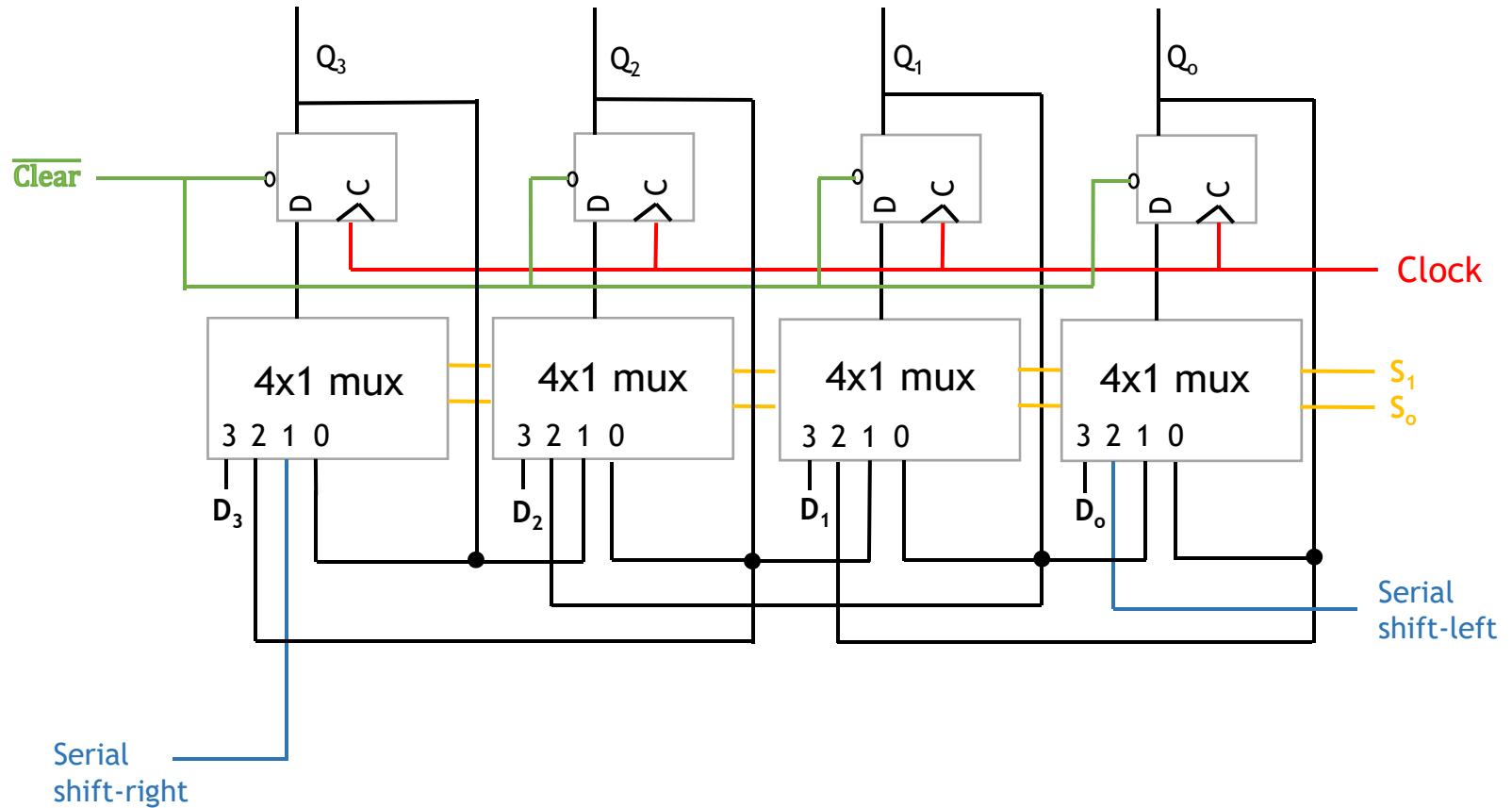
# Bidirectional shift register in Verilog



Mode Control		Register Operation
$S_1$	$S_0$	
0	0	No change (Hold)
0	1	Shift right (RSI)
1	0	Serial Shift left (LSI)
1	1	Parallel load

# Verilog HDL for shift register

// Behavioral description of a 4-bit universal shift register

```
module Shift_Register_4_beh(
    output reg    [3:0] Q;           // Register output
    input         [3:0] D;           // Parallel input
    input         [1:0] S;           // Select inputs
    input         LSI, RSI,          // Serial inputs
                CLK, Clear_b );     // Clock and Clear
always @ (posedge CLK, negedge Clear_b)
    if (Clear_b == 0) Q <= 4'b0000;
    else
        case (S)
            2'b00: Q <= Q;           // no change
            2'b01: Q <= {RSI, Q[3:1]}; // Shift right
            2'b10: Q <= {Q[2:0], LSI}; // Shift left
            2'b11: Q <= D;           // Parallel load of input
        endcase
endmodule
```

# HDL for the top level module

// Structural description of a 4-bit universal shift register

```
module Shift_Register_4_str(  
    output    [3:0] Q;           // Register output  
    input     [3:0] D;           // Parallel input  
    input     [1:0] S;           // Select inputs  
    input     LSI, RSI,          // Serial inputs  
             CLK, Clear_b );    // Clock and Clear  
  
    // instantiate the four stages  
  
    stage ST0 (Q[0], Q[1], LSI, D[0], Q[0], S, CLK, Clear_b);  
    stage ST1 (Q[1], Q[2], Q[0], D[1], Q[1], S, CLK, Clear_b);  
    stage ST2 (Q[2], Q[3], Q[1], D[2], Q[2], S, CLK, Clear_b);  
    stage ST3 (Q[3], RSI, Q[2], D[3], Q[3], S, CLK, Clear_b);  
  
endmodule
```

# HDL for the next top level module

```
// Declaring one stage of shift register
```

```
module stage(i0,i1,i2,i3,Q,select, CLK, Clr_b);
```

```
    input    i0, i1, i2, i3;           // Register output
    output    Q;                       //Parallel output
    input [1:0] select;                //Select inputs
    input     CLK,Clr_b;               //Serial inputs
    wire      mux_out;                //Clock and Clear
```

```
// instantiate mux and flip-flop
```

```
mux_4_x_1 M0 (mux_out, i0, i1, i2, i3, select);
DFF  M1 (Q,mux_out,CLK, Clr_b);
```

```
endmodule
```



# Declaring the low level modules

// Declaring 4x1 multiplexer

```
module
Mux_4_x_1(mux_out,i0,i1,i2,i3,select);

    input    i0, i1, i2, i3;
    output reg    mux_out;
    input [1:0] select;

    Always @ (select, i0,i1,i2,i3)
        case (select)
            2'b00: mux_out = i0;
            2'b01: mux_out = i1;
            2'b10: mux_out = i2;
            2'b11: mux_out = i3;
        endcase

endmodule
```

// Declaring DFF

```
module DFF(Q,D,CLK, Clr_b);

    output reg Q;
    input    D, CLK, Clr_b;

    always @ (posedge CLK, negedge Clr_b)
        if (Clr_b == 0) Q<= 1'b0;
        else
            Q <= D;
endmodule
```

# Counters

*Counters* are a specific kind of register that goes through a prescribed sequence of distinct states

Also called a pattern generator

Each stored 0/1 combination is called the state of the counter

The total number of states is called its *modulus*


If a counter has  $m$  distinct states then it is called a *mod- $m$*  counter

Two categories: *ripple* and *synchronous* counters
 
# State diagram of a counter

The order in which states appear is referred to as its *counting sequence* and depicted with a state diagram

$S_i$  denotes one of the states of the counter



# Ripple counters

In *ripple counters*, the flip-flop output transitions cause changes in other flip-flops, i.e. the effect of a count pulse ripples through the counter

Also referred to as asynchronous counters

In *binary ripple counters*, the counting sequence corresponds to that of the binary numbers

Modulus is  $2^n$ , where  $n$  is the number of flip-flops in the counter


Can have a *binary up-counter*, *binary down-counter*

# 4-bit binary ripple counter

The least significant flip-flop receives the incoming clock pulse



The complemented output of each flip-flop is connected to the clock of the next most significant flip-flop

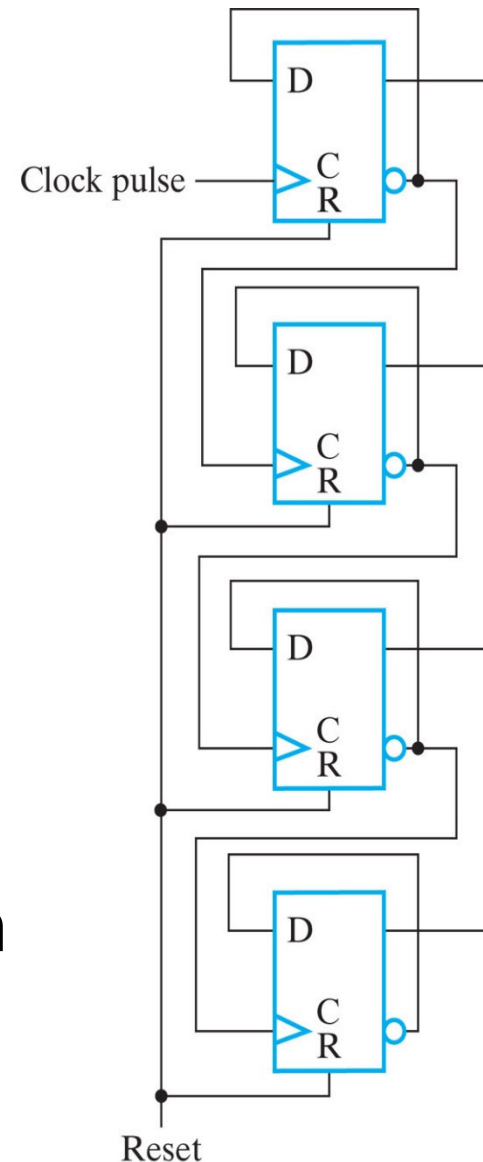Each positive transition of the clock pulse causes each flip-flop to toggle





UNSW  
SYDNEY

# 4-bit binary ripple counter

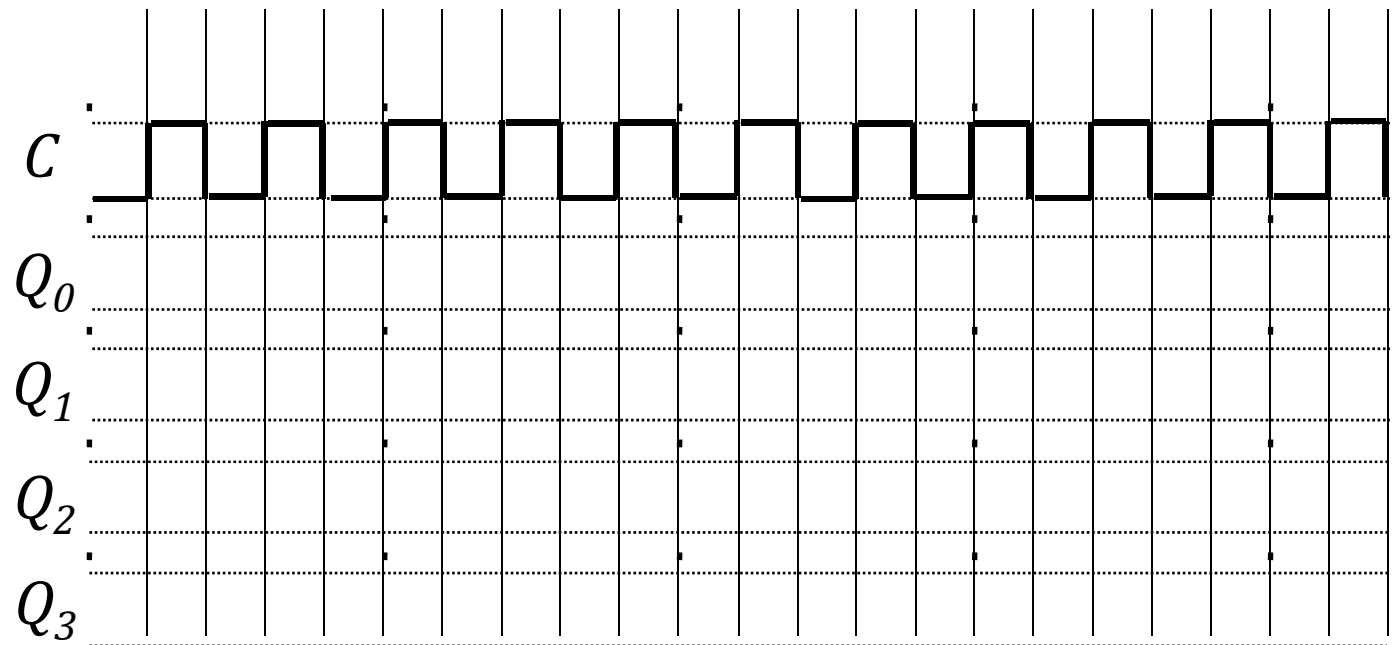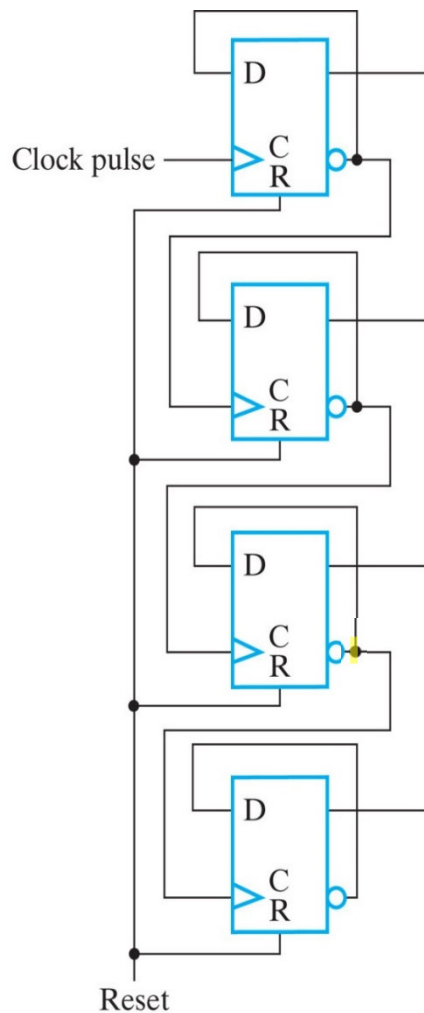

 
 
# Binary ripple counter

Counters built with T flip-flops are the simplest as the toggle feature is naturally suited to the counting operation


  
# Binary ripple counter

Counters built with T flip-flops are the simplest as the toggle feature is naturally suited to the counting operation





# Delays in ripple counters

There is a propagation delay between the input and output of a flip-flop

Rippling behavior affects the overall time delay between the occurrence of a count pulse and when the stabilized count appears at the output


When going from  $111 \dots 111$  to  $000 \dots 000$ , toggle signals must propagate through the entire length of the counter

For  $n$ -stage binary ripple counter, the worst case time is  $n \cdot t_{pd}$ , where  $t_{pd}$  is the propagation delay time associated with each flip-flop
 
# Synchronous binary counters



In *synchronous counters*, all flip-flops change simultaneously after the propagation delay associated with a single flip-flop

Count pulses are applied directly to the control inputs, C, of all the clocked flip-flops



4-bit synchronous up counter with T flip-flops

# Synchronous binary counters

  


# Synchronous binary counters

A *synchronous counter* can also be made by combining an adder with D flip-flop


All the flip-flops trigger on the positive edge of the clock (can also use negative edge)

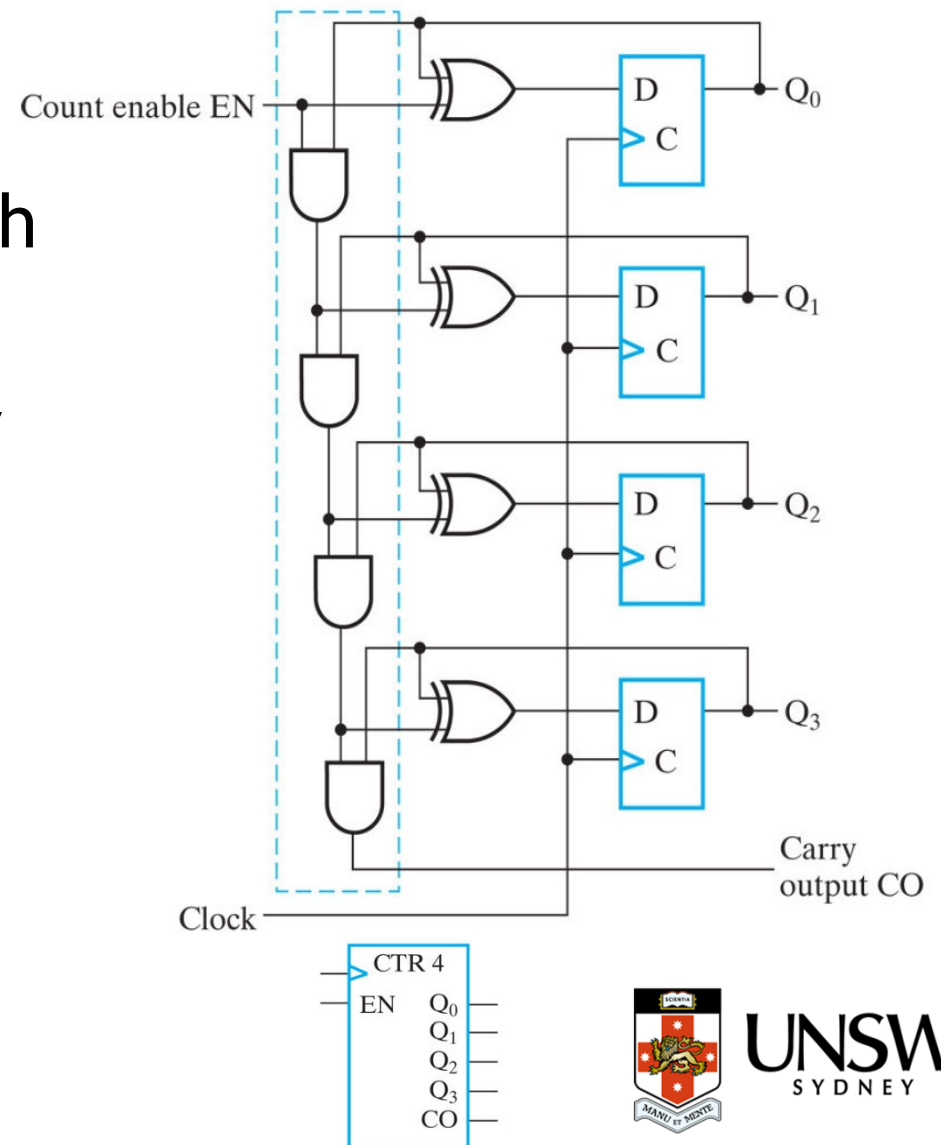The carry output CO is used to extend the counter to more stages



UNSW  
SYDNEY

# Binary counter with parallel load

 


Parallel load added to input an initial binary number into counter prior to count operation


Load	Count	Operation
1	0	Parallel load
0	1	Count enabled
0	0	Hold
 
# Cascaded counters

Larger counters can be built by combining smaller counters together



3 digit BCD counter

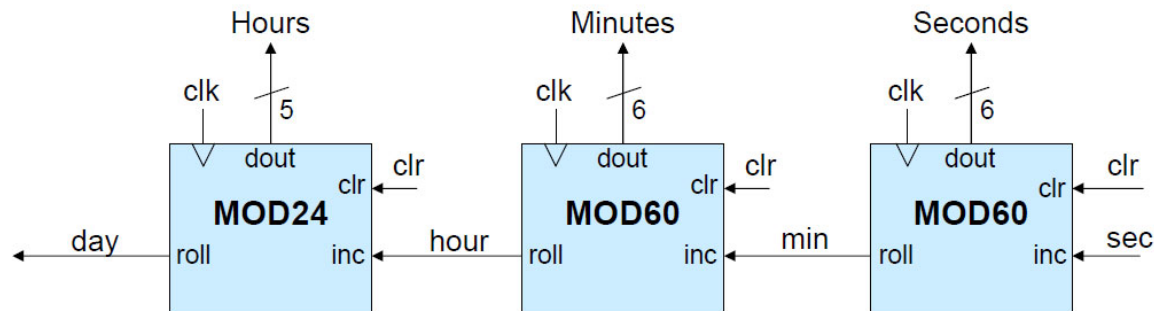

Hour:minute:second clock

# Computer design fundamentals

A simple computer architecture can be divided into

1. *Datapath*, which consists of:

- A set of registers

- The micro-operations performed on data stored in the registers

- The control interface


2. *Control Unit*, which provides signals that control micro-operations performed in the datapath and other components

*Micro-operations* are elementary operations performed on data stored in registers (arithmetic/logic/shift/transfer)

In computer systems, a shared *arithmetic/logic unit (ALU)* is used to perform micro-operations

The contents of registers are transferred to the ALU, which performs the operation and then transfers them to the destination

# Datapath

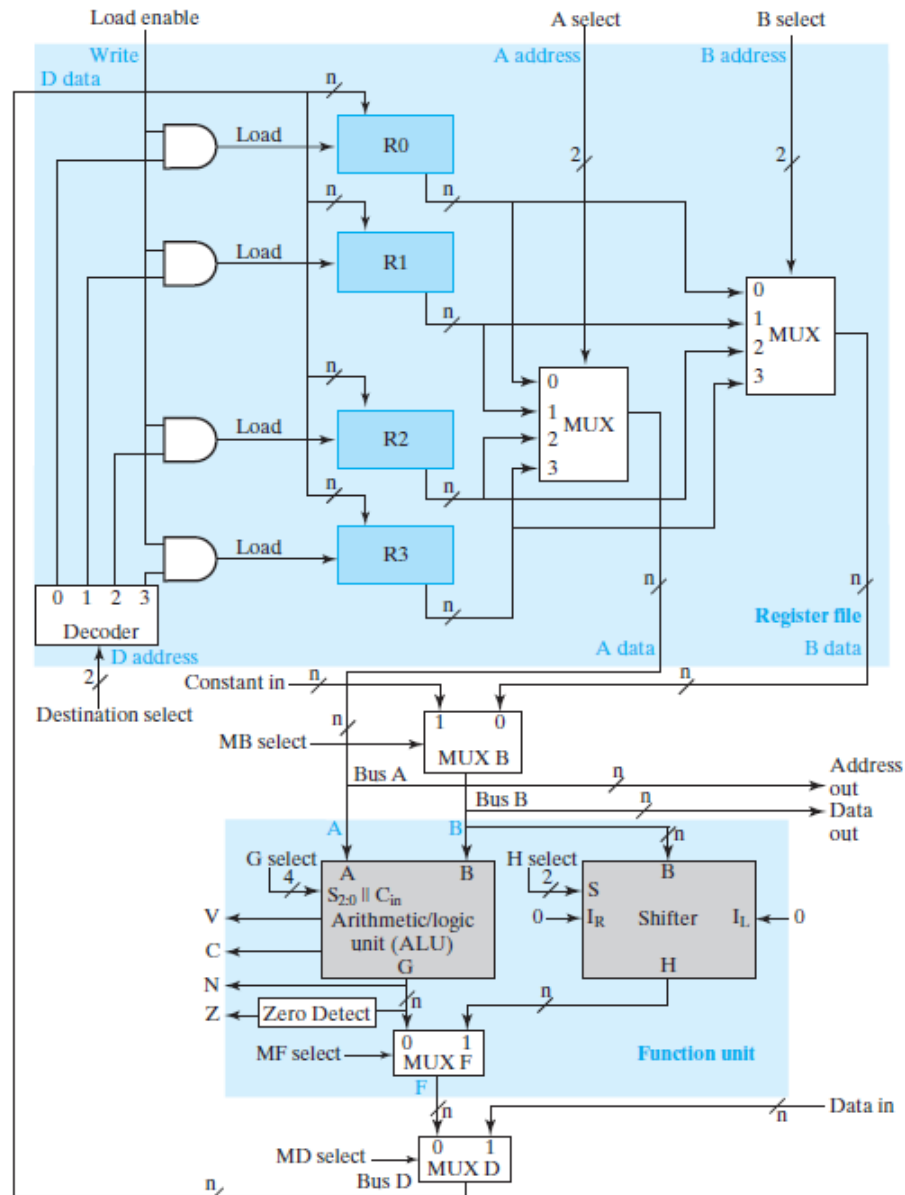




# Datapath

Registers are denoted by uppercase letters (followed by numbers)

*AR* - address register, *PC* - program counter, *R2* - register 2

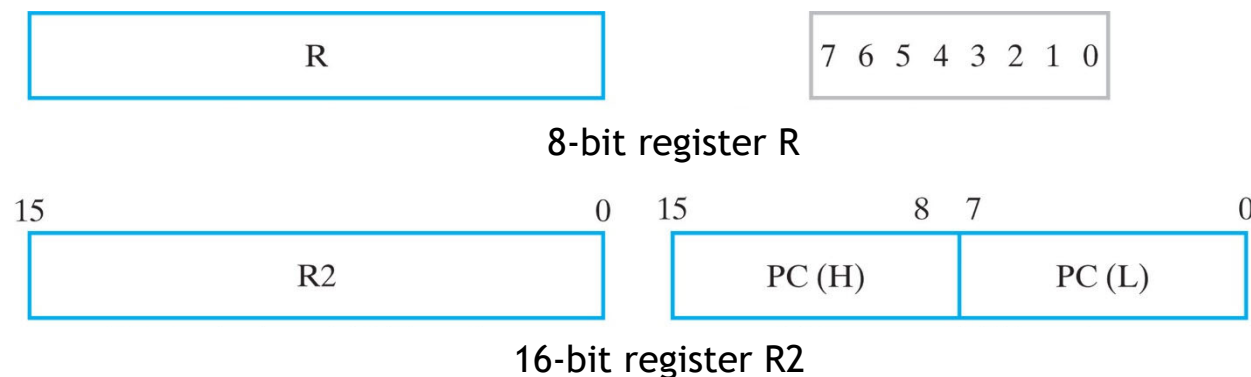The individual flip-flops in a  $n$  bit register are numbered from 0 to  $n-1$  with 0 the LSB



# Datapath

Data transfer from one register to another is denoted using the  $\leftarrow$  operator

$$R2 \leftarrow R1$$

$R1$  is the source of transfer and  $R2$  the destination


Conditional statements used when data transfer occurs only on receiving a control signal

$$K_1: R2 \leftarrow R1$$

$K_1$  can be any Boolean function or variable that evaluates to 0 or 1

$$K_3: R2 \leftarrow R1, R1 \leftarrow R2$$

# Datapath

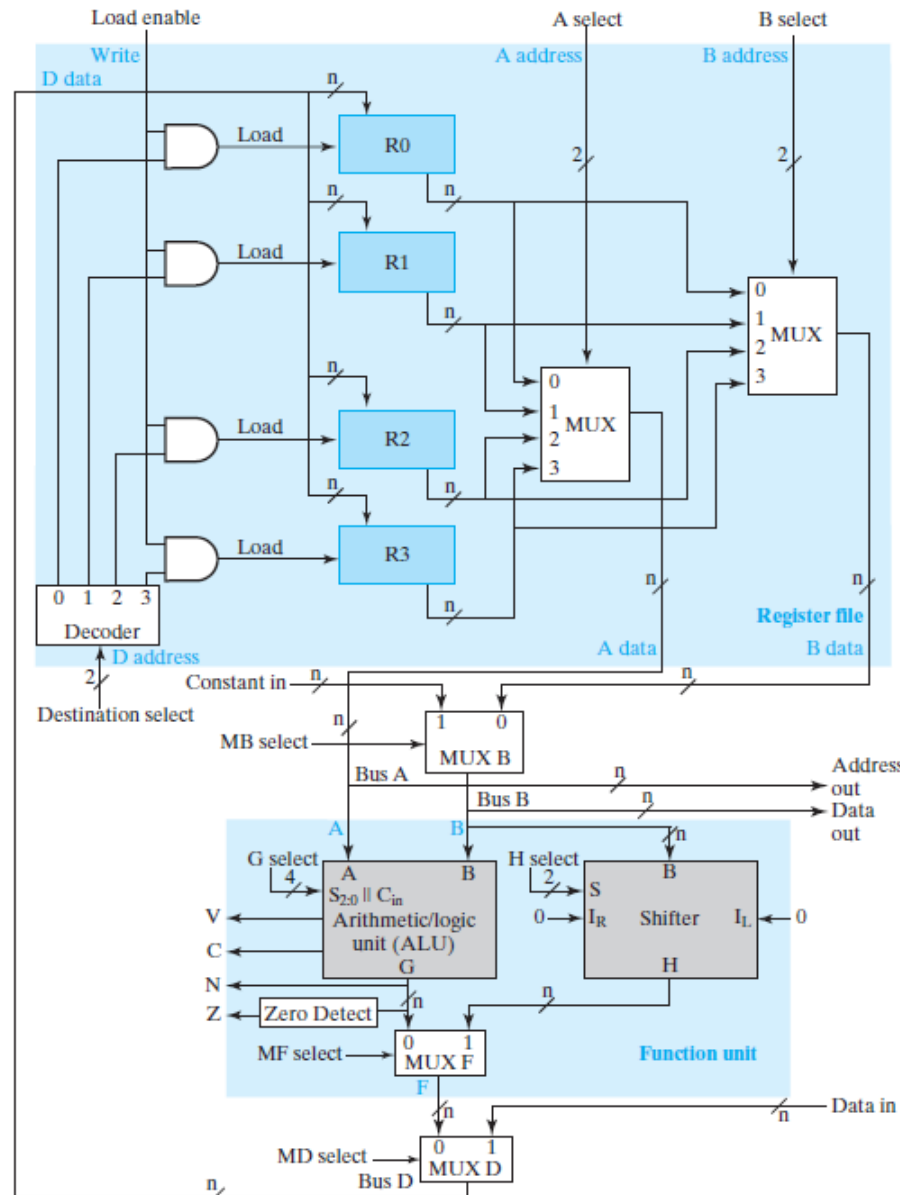

To perform  $R1 \leftarrow R2 + R3$

The control unit must provide the following control inputs:


1. **A select**, to place contents of  $R2$  onto  $A$  data and Bus A
2. **B select** to place contents of  $R3$  onto 0 input of MUX B; and **MB select** to put 0 input of MUX B onto Bus B
3. **G select**, to complete  $A+B$
4. **MF select**, to place the ALU output on the MUX F output
5. **MD select**, to place the MUX F output onto Bus D
6. **Destination select**, to select  $R1$  as the destination of the data on Bus D
7. **Load enable**, to enable  $R1$  to be loaded



UNSW  
SYDNEY
 
# Arithmetic/logic unit

An *arithmetic/logic unit (ALU)* is a combinational circuit that performs basic arithmetic and logic operations



# Arithmetic/logic unit

Performs a set of basic arithmetic and logic micro-operations


The  $n$ -bit result is output on vector  $G$  with carry-out on  $C_{out}$

$S_2$  selects between arithmetic or logic operations

$S_1$  and  $S_0$  select one of 4 operations within the arithmetic or logic operations

Can be extended to 8 operations by using the  $C_{in}$  (carry-in) input

# Arithmetic/logic unit

 

# Arithmetic unit

The arithmetic circuit is based on the  $n$ -bit parallel adder  
By controlling the inputs to the adder, different types of arithmetic operations can be obtained

Connect the  $X$  input of the adder directly to operand  $A$

Make the input  $Y$  some function of operand  $B$

Select		Input	$G = A + Y + C_{in}$	
$S_1$	$S_0$	$Y$	$C_{in} = 0$	$C_{in} = 1$
0	0	All 0s	$G = A$ (transfer)	$G = A + 1$ (increment)
0	1	$B$	$G = A + B$ (add)	$G = A + B + 1$
1	0	$\bar{B}$	$G = A + \bar{B}$	$G = A + \bar{B} + 1$ (subtract)
1	1	All 1s	$G = A - 1$ (decrement)	$G = A$ (transfer)

# Arithmetic unit

Use a truth table and k-maps to implement the select logic on input  $B$


Inputs			Output	Function
$S_1$	$S_0$	$B_i$	$Y_i$	
0	0	0	0	$Y_i = 0$
0	0	1	0	
0	1	0	0	$Y_i = B_i$
0	1	1	1	
1	0	0	1	$Y_i = \bar{B}_i$
1	0	1	0	
1	1	0	1	$Y_i = 1$
1	1	1	1	

		$S_1 S_0$		
		00	01	$S_1$
$B_i$	0	0	0	11
	1	0	1	10
		$S_0$		

$$Y_i = B_i S_0 + \bar{B}_i S_1$$



# Arithmetic unit

 


# Logic unit

Performs bitwise logical operations on the bits of the operands


There are four commonly used logic operations- AND, OR, XOR, and NOT

 One stage logic unit: (as many as n-bit are required)



$S_1$	$S_0$	Output	Operation
0	0	$G = A \& B$	AND
0	1	$G = A   B$	OR
1	0	$G = A \oplus B$	XOR
1	1	$G = \bar{A}$	NOT

# Arithmetic/logic unit

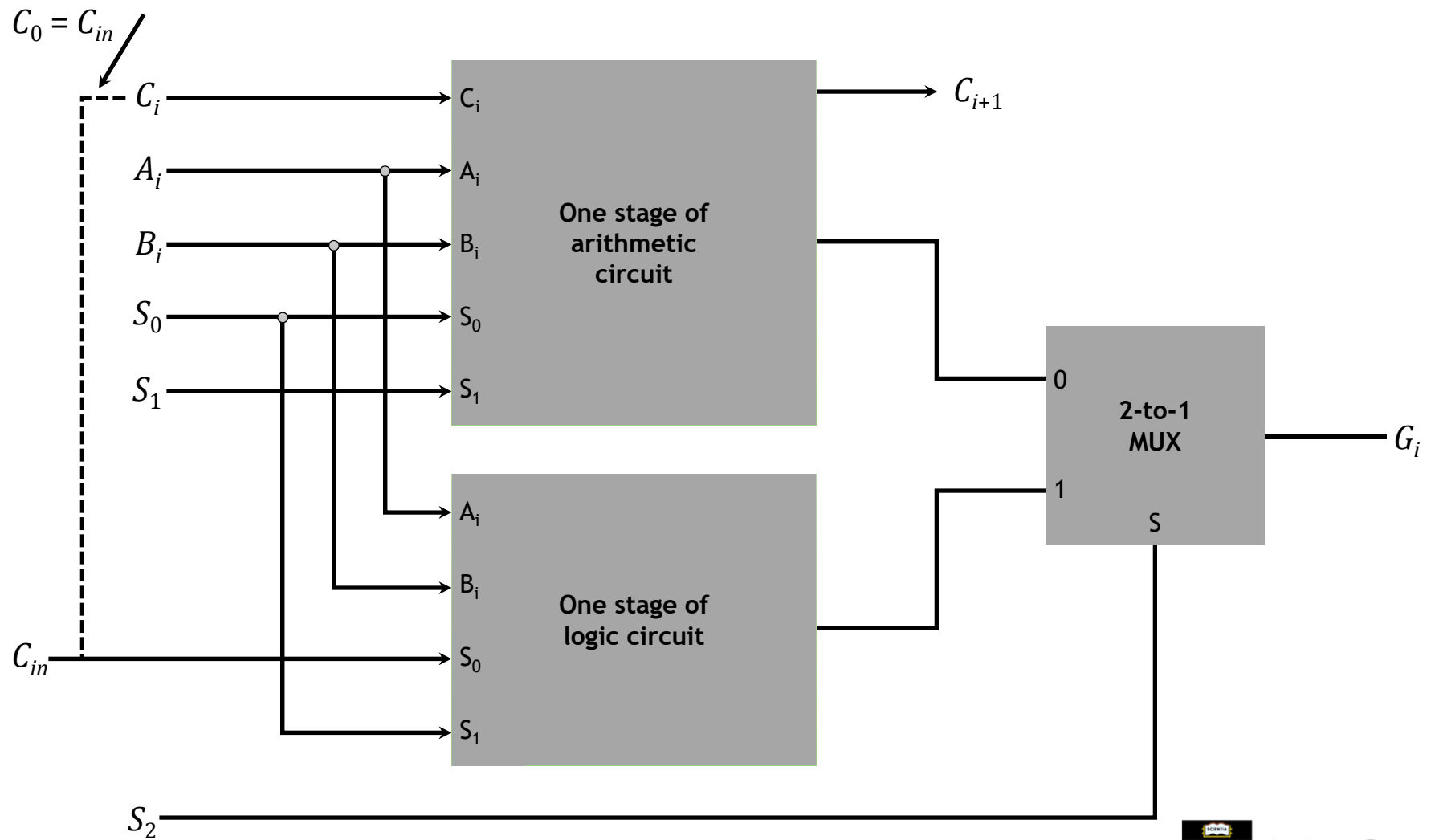

# Arithmetic/logic unit

Operation Select				Operation	Function
$S_2$	$S_1$	$S_0$	$C_{in}$		
0	0	0	0	$G = A$	Transfer $A$
0	0	0	1	$G = A + 1$	Increment $A$
0	0	1	0	$G = A + B$	Addition
0	0	1	1	$G = A + B + 1$	Add with carry input of 1
0	1	0	0	$G = A + \bar{B}$	$A$ plus 1's complement of $B$
0	1	0	1	$G = A + \bar{B} + 1$	Subtraction
0	1	1	0	$G = A - 1$	Decrement $A$
0	1	1	1	$G = A$	Transfer $A$
1	X	0	0	$G = A \& B$	AND
1	X	0	1	$G = A   B$	OR
1	X	1	0	$G = A \oplus B$	XOR
1	X	1	1	$G = \bar{A}$	NOT (1's complement)



# The Shifter

The *shifter* shifts the value on Bus  $B$  by one bit to the left or by one bit to the right

Constructed using a combinational circuit so not dependent on the system clock

The shifter can be designed using  $n$  multiplexers with two select lines:

$S = 00$  - no shift


$S = 01$  - right shift

$S = 10$  - left shift



UNSW  
SYDNEY

# 4-bit shifter

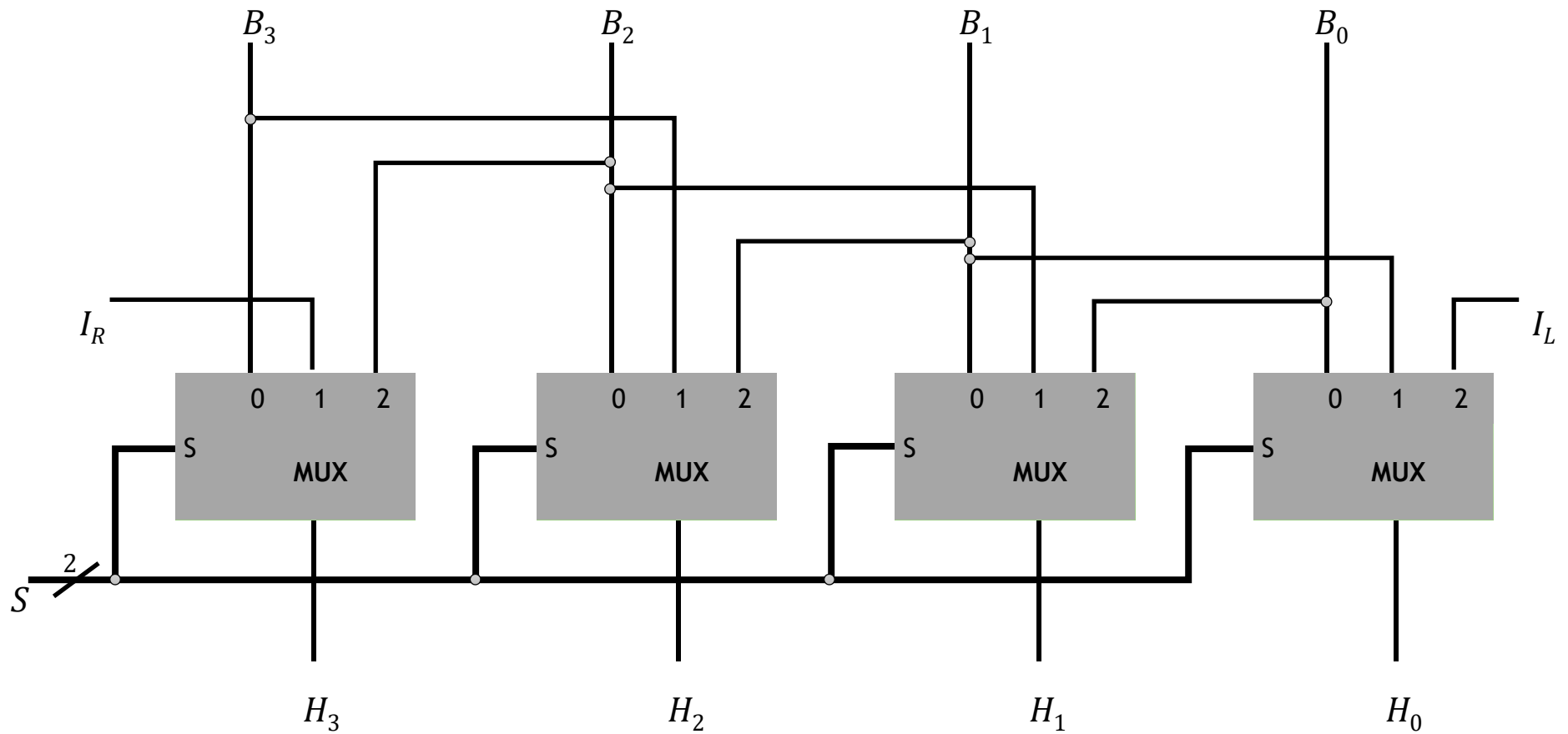

# Datapath representation


We can reduce the apparent complexity of the datapath by enclosing different functions into modules

Different implementations of the modules can then be interchanged without redesigning the entire datapath

All registers with common micro-operations are organised into a *register file*

Since the ALU and shifter are shared processing units, they are grouped together with the MUX into a shared *function unit*

# Datapath representation

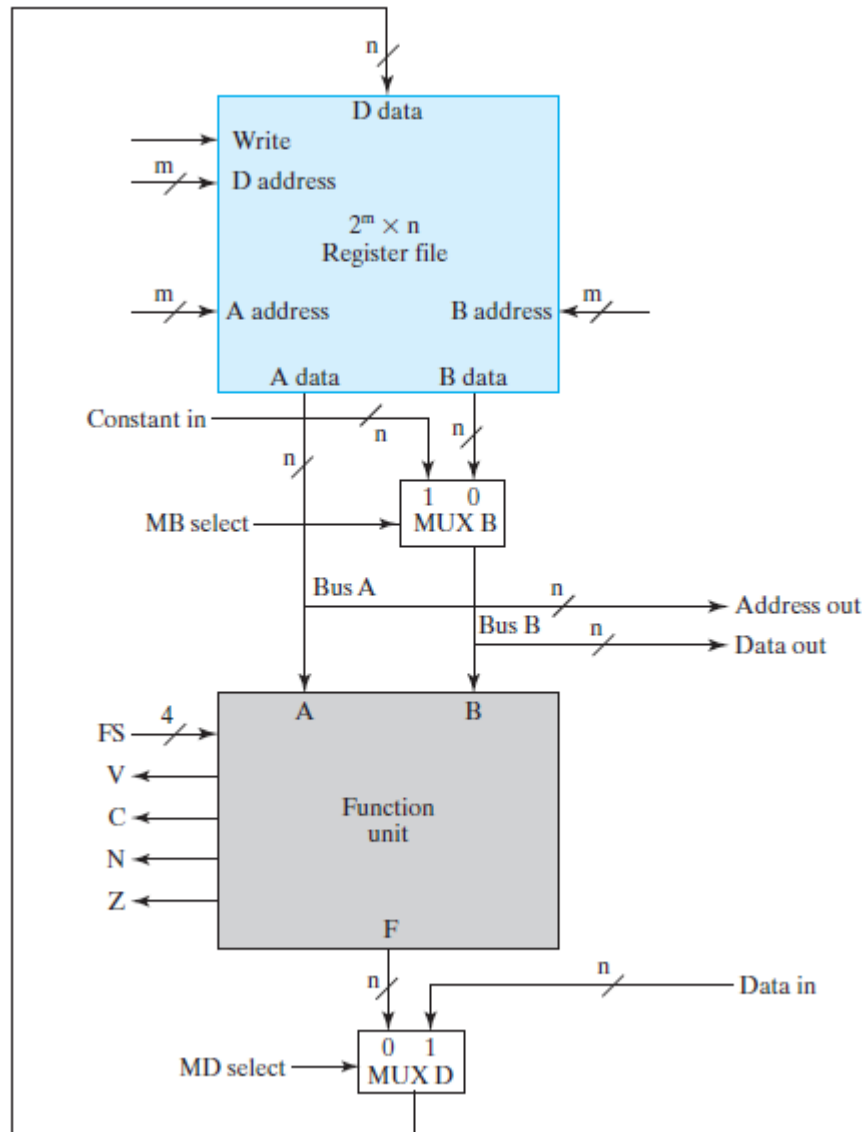

The size of the *register file* is  $2^m \times n$  where  $m$  is the number of register address bits and  $n$  is the number of bits per register

The operation of the *function unit* is selected using a 4-bit *FS* (function select)



# Datapath representation

FS[3:0]	MF Select	G[3:0] Select	H[1:0] Select	Operation
0000	0	0000	XX	$F = A$
0001	0	0001	XX	$F = A + 1$
0010	0	0010	XX	$F = A + B$
0011	0	0011	XX	$F = A + B + 1$
0100	0	0100	XX	$F = A + \bar{B}$
0101	0	0101	XX	$F = A + \bar{B} + 1$
0110	0	0110	XX	$F = A - 1$
0111	0	0111	XX	$F = A$
1000	0	1X00	XX	$F = A \& B$
1001	0	1X01	XX	$F = A   B$
1010	0	1X10	XX	$F = A \oplus B$
1011	0	1X11	XX	$F = \bar{A}$
1100	1	XXXX	00	$F = B$
1101	1	XXXX	01	$F = B \gg 1$
1110	1	XXXX	10	$F = B \ll 1$



# Datapath representation

To fully specify the function unit, all the codes for *MF select*, *G select* and *H select* must be defined in terms of *FS*.

From the function table, can derive the internal inputs in the function unit in terms of the *FS* external input:

$$MF = FS[3]FS[2]$$

$$G[3:0] = FS[3:0]$$

$$H[1:0] = FS[1:0]$$

# Final exam format

2 hours

4 questions - 25 marks each

Similar to mid semester exam

Topics covered

- Combinational circuits

- Sequential circuits

- Verilog

- Arithmetic circuits

- Digital integrated circuits

- Computer design fundamentals

# Combinational circuits

$$\overline{W}\overline{X}Y + \overline{W}\overline{Y} + \overline{X}YZ + \overline{W}\overline{X}Y$$

Algebraic simplification

Simplification via K-maps

SOP, POS form

NAND, NOR implementation

Implementation using decoders/MUXs

GIC

# Sequential circuits

*Serial sequence detector, e.g. three consecutive bits*

State diagram

Mealy, Moore state machines

State table

State minimisation

Implementation via flip-flops (JK/D/T)

# Verilog

```
module
mux_case(out,cntrl,in1,in2);
input cntrl,in1,in2;
output out;
reg out;

always @ *
case (cntrl)
1'b0:
out = in1;
1'b1 :
out = in2;
endcase
endmodule
```

Describe what code does

Explain specific parts of code

Identify errors in code

Add/modify lines of code



# Arithmetic circuits

$$67 + 23$$

$$-57 + 110$$

$$23 - 49$$

Half and full adder

Binary ripple carry and look carry-ahead adder

1's and 2's complement

Unsigned and signed binary addition and subtraction

Overflow and Status flags

# Digital integrated circuits

$$F(w, x, y, z) = \sum m(0,1,2,4,5)$$

BJT logic families - understanding how they operate

Fan-out, power dissipation, propagation delay, noise margin, cost

CMOS implementation of logic functions



# Computer design fundamentals

Registers

Shifters - serial, parallel, bidirectional

Datapaths

Arithmetic Unit

Logic Unit

Shifter Unit

Datapath representation